
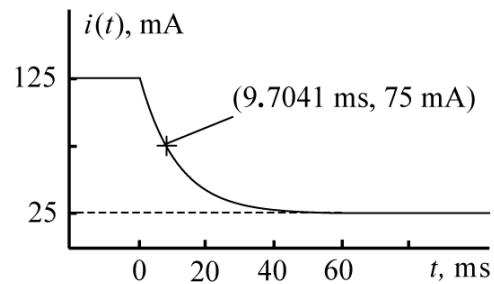


# EE221 1<sup>st</sup> Midterm Exam - Spring 2010

Name \_\_\_\_\_

Student # \_\_\_\_\_

1.

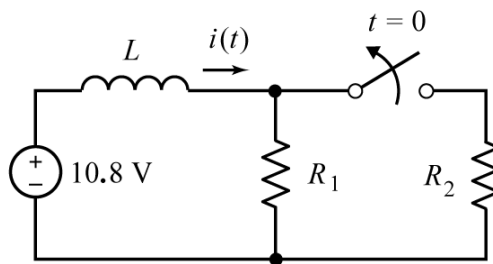

a. Determine the values of  $R_1$  and  $R_2$ .

$$R_1 = \underline{\quad 432 \quad} \Omega \text{ and } R_2 = \underline{\quad 108 \quad} \Omega.$$

b. Determine the value of the time constant,  $\tau$ , of this circuit after the switch opens.

$$\tau = \underline{\quad 14 \quad} \text{ ms.}$$

a.  $0.025 = \frac{10.8}{R_1} \Rightarrow R_1 = 432 \Omega$  and  $0.125 = \frac{10.8}{R_1 \parallel R_2} \Rightarrow 432 \parallel R_2 = 86.4 \Omega \Rightarrow R_2 = 108 \Omega$


b. After the switch closes, the plot can be represented by the equation  $i(t) = 25 + 100e^{-at}$  mA so

$$75 = 25 + 100e^{-a(0.0097041)} \Rightarrow a(0.0097041) = -\ln\left(\frac{75-25}{100}\right) \Rightarrow a = 71.4286 \frac{1}{\text{s}}$$

$$\tau = \frac{1}{a} = 0.0140 \text{ s} = 14 \text{ ms}$$

Also, after the switch closes, the Thevenin resistance of the part of the circuit connected to the inductor is  $R_1 = 432 \Omega$ . Consequently, the inductance is  $L = \tau R_1 = 0.014(432) = 6.048 \text{ H}$ .

2. An AC source is connected to a load:

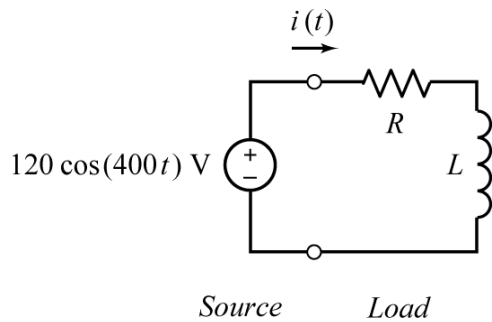

a) Suppose that the voltage source supplies

$$\mathbf{S} = 11.686 \angle 35.75^\circ = 9.4837 + j6.8282 \text{ VA}$$

And the current is represented as

$$i(t) = B \cos(400t + \theta) \text{ mA}$$

Determine values of  $B$  and  $\theta$ .

$$B = \underline{\underline{194.8}} \text{ mA} \quad \text{and} \quad \theta = \underline{\underline{-35.75}}^\circ$$

b) Suppose **instead** that

$$i(t) = 274.54 \cos(400t - 29.6^\circ) \text{ mA}$$

Determine values of the resistance and inductance.

$$R = \underline{\underline{380}} \Omega \quad \text{and} \quad L = \underline{\underline{540}} \text{ mH}$$

c) Suppose **instead** that  $i(t) = 332.8 \cos(400t - 33.7^\circ) \text{ mA}$ . Determine the values of the real and reactive powers supplied by the source to the load.

$$P = \underline{\underline{16.61}} \text{ W} \quad \text{and} \quad Q = \underline{\underline{11.08}} \text{ VAR}$$

d) Suppose **instead** that the voltage source supplies 20.43 W at a power factor of 0.8423 lagging. Determine the values of the apparent and reactive powers supplied by the source to the load.

$$|\mathbf{S}| = \underline{\underline{24.255}} \text{ VA} \quad \text{and} \quad Q = \underline{\underline{13.074}} \text{ VAR}$$

**Solution:**

$$\text{a) } \mathbf{I} = \left( \frac{2\mathbf{S}}{\mathbf{V}} \right)^* = \left( \frac{2(11.686 \angle 35.75^\circ)}{120 \angle 0^\circ} \right)^* = 0.19477 \angle -35.75^\circ \text{ A}$$

$$\text{b) } \mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{120 \angle 0^\circ}{0.27454 \angle -29.6^\circ} = 437.095 \angle 29.6^\circ = 420 + j90.04 = 380 + j(400)(0.5400) \Omega$$

$$\text{c) } \mathbf{S} = \frac{(120 \angle 0^\circ)(0.3328 \angle -33.7^\circ)^*}{2} = 19.968 \angle 33.7^\circ = 16.61 + j11.08 \text{ VA}$$

$$\text{d) } 20.43 = P = |\mathbf{S}| \text{ pf} = |\mathbf{S}| 0.8423 \Rightarrow |\mathbf{S}| = 24.255 \text{ VA}$$


$$Q = |\mathbf{S}| \sin(\cos^{-1}(\text{pf})) = 24.255 \sin(\cos^{-1}(0.8423)) = 13.074 \text{ VAR}$$

3. The input to this circuit shown is

$$v_s(t) = 12 \cos(8t) \text{ V}$$

The impedance of the load is  $12 + j16 \Omega$ .

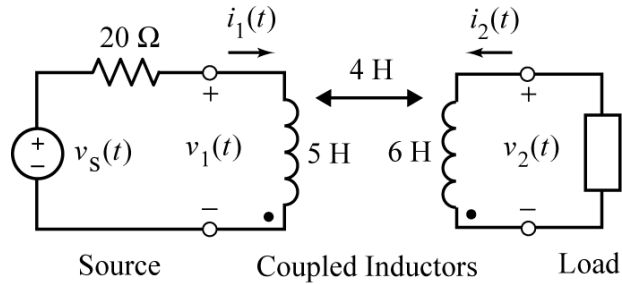Noticing that  $i_1(t)$  and  $i_2(t)$  are mesh currents, we can represent this circuit by the mesh equations




$$\begin{bmatrix} 20 + ja & jb \\ jc & 12 + jd \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 12 \angle 0^\circ \\ 0 \end{bmatrix}$$

where  $a$ ,  $b$ ,  $c$ , and  $d$  are real constants. Determine the values of  $a$ ,  $b$ ,  $c$ , and  $d$ .

$$a = \underline{\quad 40 \quad} \Omega, \quad b = \underline{\quad 32 \quad} \Omega, \quad c = \underline{\quad 32 \quad} \Omega, \quad \text{and} \quad d = \underline{\quad 64 \quad} \Omega$$

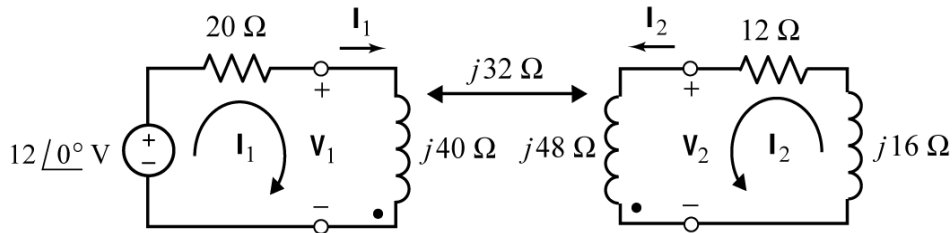Represent the circuit in the frequency domain as



The coil voltages are given by

$$\mathbf{V}_1 = j40\mathbf{I}_1 + j32\mathbf{I}_2 \quad \text{and} \quad \mathbf{V}_2 = j48\mathbf{I}_2 + j32\mathbf{I}_1$$

Using KVL

$$20\mathbf{I}_1 + \mathbf{V}_1 - 12 \angle 0^\circ = 0 \quad \text{and} \quad 12\mathbf{I}_2 + j16\mathbf{I}_2 + \mathbf{V}_2 = 0$$

Substituting the coil voltages:

$$20\mathbf{I}_1 + j40\mathbf{I}_1 + j32\mathbf{I}_2 = 12 \angle 0^\circ$$

$$12\mathbf{I}_2 + j16\mathbf{I}_2 + j48\mathbf{I}_2 + j32\mathbf{I}_1 = 0$$


Solving gives

$$\mathbf{I}_1 = 0.3575 \angle -47^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_2 = 0.1757 \angle 143.6^\circ \text{ A}$$

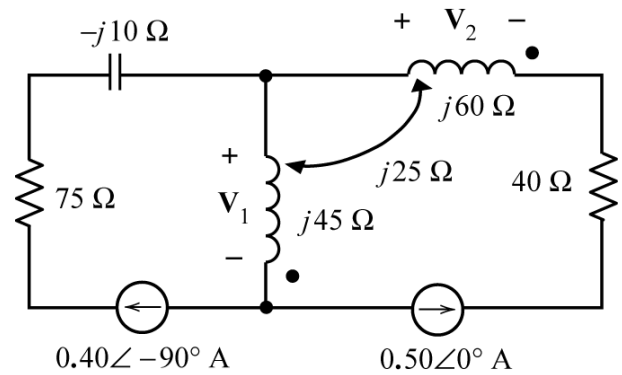4. Here is an AC circuit represented in the frequency domain. This circuit contains a pair of coupled coils.

Represent the coil voltages as  $\mathbf{V}_1 = A \angle \theta$  V and  $\mathbf{V}_2 = B \angle \phi$  V. Determine the values of the amplitude and angle of  $\mathbf{V}_1$ .

$$A = \underline{20.6} \text{ V}, \theta = \underline{29.1}^\circ$$




**Solution:**

$$\mathbf{V}_1 = j45(0.5 - j0.4) + j25(-0.5) = 18 + j10 = 20.59 \angle 29.1^\circ \text{ V},$$

$$\mathbf{V}_2 = j60(-0.5) + j25(0.5 - j0.4) = 10 - j17.5 = 20.16 \angle -60.26^\circ \text{ V}$$

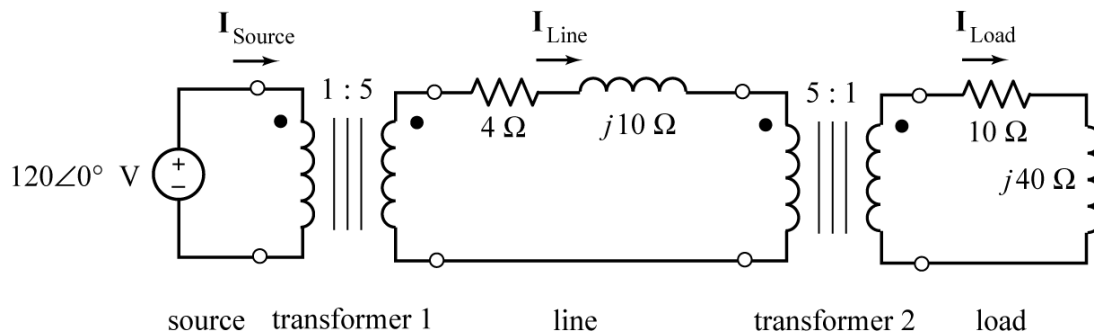5. Consider this circuit, represented in the frequency domain.



Given that the line current is  $\mathbf{I}_{\text{Line}} = 0.5761 \angle -75.88^\circ$  A, determine  $P_{\text{Source}}$ , the average power supplied by the source,  $P_{\text{Line}}$ , the average power delivered to the line and  $P_{\text{Load}}$ , the average power delivered to the load.

$$P_{\text{Source}} = \underline{42.15} \text{ W}, P_{\text{Line}} = \underline{0.6638} \text{ W} \text{ and } P_{\text{Load}} = \underline{41.49} \text{ W}$$

(**Hint:** Use conservation of (average) power to check your answers.)

$$\mathbf{I}_{\text{Source}} = \left(\frac{5}{1}\right) \mathbf{I}_{\text{Line}} = 2.8805 \angle -75.88^\circ \text{ A} \text{ so } P_{\text{Source}} = \frac{(120)(2.8805)}{2} \cos(0 - (-75.88^\circ)) = 42.16 \text{ W}$$

$$P_{\text{Line}} = \frac{0.5761^2}{2} (4) = 0.6638 \text{ W}$$


$$\mathbf{I}_{\text{Load}} = \left(\frac{5}{1}\right) \mathbf{I}_{\text{Line}} = 2.8805 \angle -75.88^\circ \text{ A} \text{ so } P_{\text{Load}} = \frac{2.8805^2}{2} (10) = 41.49 \text{ W}$$

6. In this circuit

$$i(t) = 0.135 \cos(5t - 81.16^\circ) \text{ A}$$

and
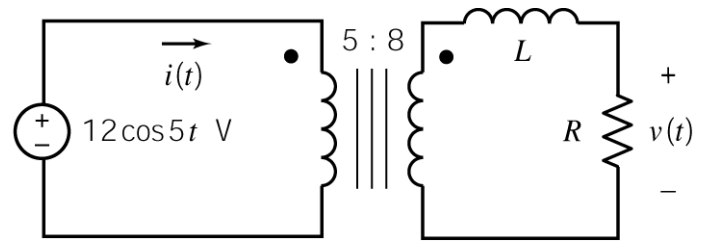
$$v(t) = 2.951 \cos(5t - 81.16^\circ) \text{ V}$$




Determine the resistance and inductance values:

$$R = \underline{\quad 35 \quad} \Omega \text{ and } L = \underline{\quad 45 \quad} \text{ H}$$

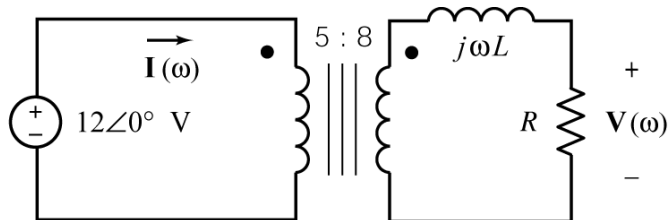**Solution:**

Represent the circuit in the frequency domain as



The impedance seen by the voltage source is

$$\left(\frac{5}{8}\right)^2 (R + j5L) = \frac{12 \angle 0^\circ}{\mathbf{I}} = \frac{12 \angle 0^\circ}{0.135 \angle -81.16^\circ} = 88.889 \angle 81.16^\circ$$

so


$$R + j5L = 227.556 \angle 81.16^\circ = 34.970 + j224.853 = 34.970 + j(5)44.971$$

Consequently  $L = 44.971 \cong 45 \text{ H}$  and  $R = 34.970 \cong 35 \Omega$ .

Notice also that

$$R = \frac{\mathbf{V}(\omega)}{\frac{5}{8}\mathbf{I}(\omega)} = \frac{2.951 \angle -81.16^\circ}{\left(\frac{5}{8}\right)0.135 \angle -81.16^\circ} = 34.975 \cong 35 \Omega$$

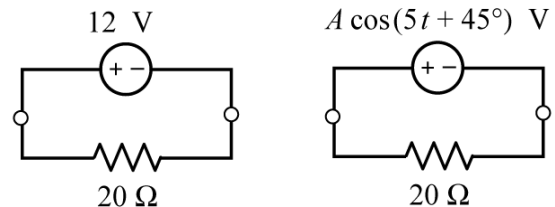7. The sources in these two circuits supply equal values of average power,  $P_{\text{ave}}$ . Determine the values of  $A$ , the amplitude of the sinusoidal voltage, and  $P_{\text{ave}}$ .



$$A = \underline{\quad 16.97 \quad} \text{ V and } P_{\text{ave}} = \underline{\quad 7.2 \quad} \text{ W}$$

$$\frac{A}{\sqrt{2}} = 12 \Rightarrow A = 16.97 \approx 17 \text{ V and } P_{\text{ave}} = 12 \left( \frac{12}{20} \right) = 7.2 \text{ W}$$