
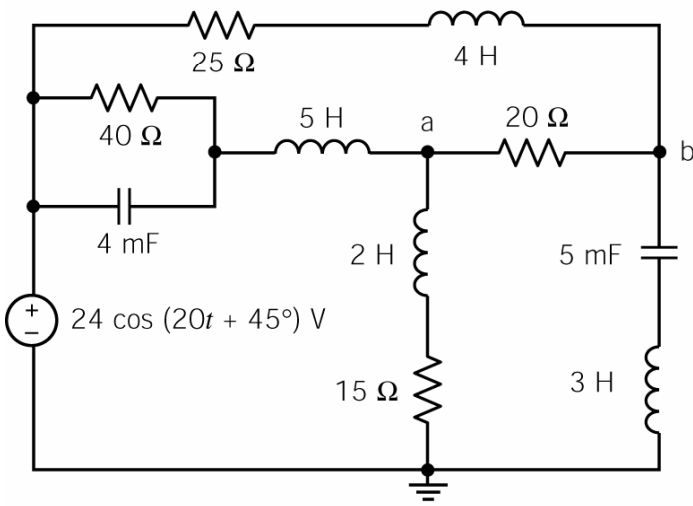


(a)

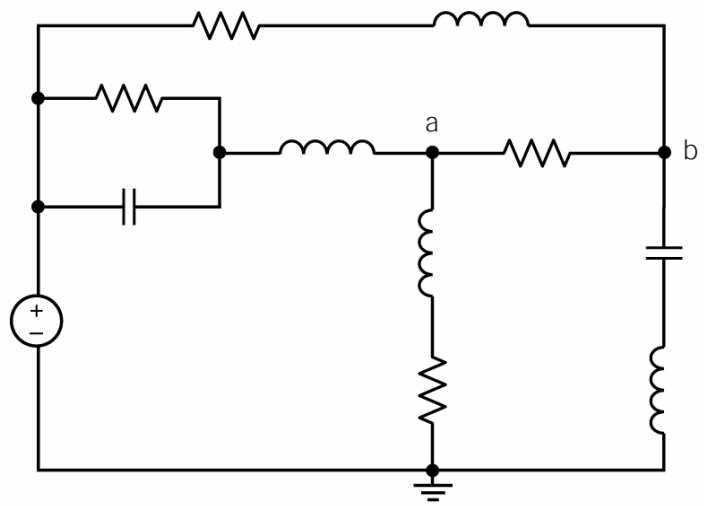


time domain











frequency domain

(b)

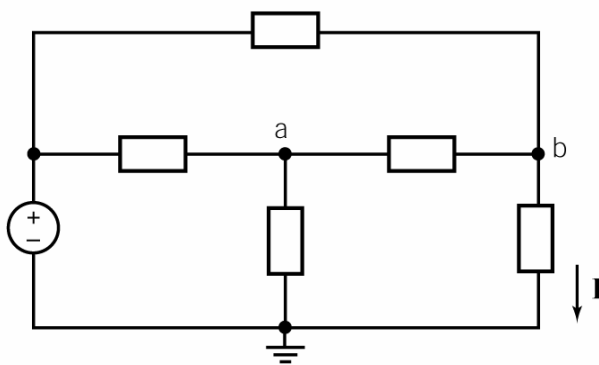

(c)

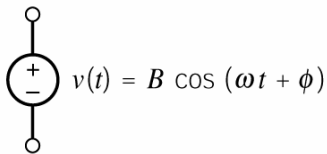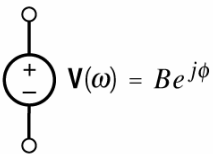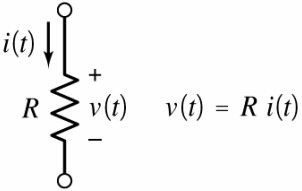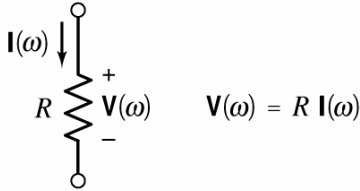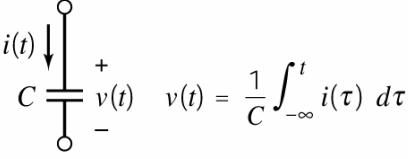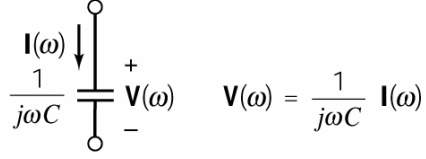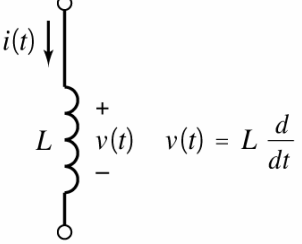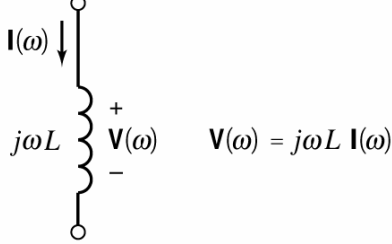ELEMENT	TIME DOMAIN	FREQUENCY DOMAIN
Voltage source	 $v(t) = B \cos(\omega t + \phi)$	 $\mathbf{V}(\omega) = B e^{j\phi}$
Resistor	 $v(t) = R i(t)$	 $\mathbf{V}(\omega) = R \mathbf{I}(\omega)$
Capacitor	 $v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$	 $\mathbf{V}(\omega) = \frac{1}{j\omega C} \mathbf{I}(\omega)$
Inductor	 $v(t) = L \frac{d}{dt} i(t)$	 $\mathbf{V}(\omega) = j\omega L \mathbf{I}(\omega)$

Complex Numbers

$$A\angle\theta = a + jb$$

where $A\angle\theta$ is the complex number in polar form and $a + jb$ is the complex number in rectangular form. The conversion from polar form to rectangular form and visa versa is described by

$$a = \text{the real part of } A\angle\theta = A \cos(\theta)$$

$$b = \text{the imaginary part of } A\angle\theta = A \sin(\theta)$$

$$A = \text{the magnitude of } a + jb = \sqrt{a^2 + b^2}$$

$$\theta = \text{the angle of } a + jb = \begin{cases} \tan^{-1}\left(\frac{b}{a}\right) & \text{when } a > 0 \\ 180^\circ - \tan^{-1}\left(\frac{b}{-a}\right) & \text{when } a < 0 \end{cases}$$

Solution

(a) The node equations are

$$\frac{24 - v_a}{40} = \frac{v_a - v_b}{20} + \frac{v_a}{15}$$

$$\frac{24 - v_b}{25} + \frac{v_a - v_b}{20} = \frac{v_b}{50}$$


or

$$\begin{bmatrix} \frac{1}{40} + \frac{1}{20} + \frac{1}{15} & -\frac{1}{20} \\ -\frac{1}{20} & \frac{1}{25} + \frac{1}{20} + \frac{1}{50} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} \frac{24}{40} \\ \frac{24}{25} \end{bmatrix}$$

Solving using MATLAB gives

$$v_a = 8.713 \text{ V} \quad \text{and} \quad v_b = 12.69 \text{ V}$$

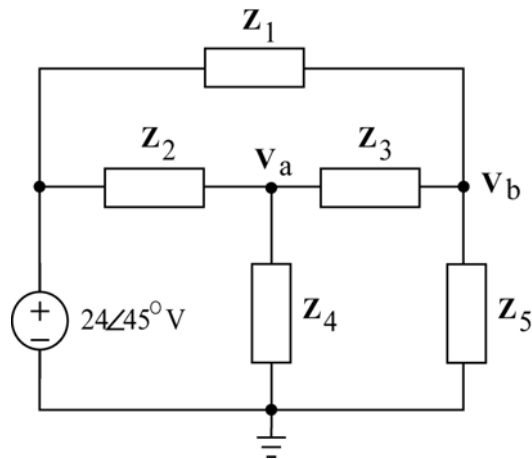(b, c) Use phasors and impedances to represent the circuit in the frequency domain as



where

$$\mathbf{Z}_1 = 25 + j(20)4 = 25 + j80 = 83.82 \angle 72.7^\circ \Omega$$

$$\mathbf{Z}_2 = \left(40 \parallel \frac{1}{j(20)(0.004)} \right) + j(20)5 = 3.56 + j88.6 = 88.68 \angle 87.7^\circ \Omega$$

$$\mathbf{Z}_3 = 20 \Omega$$

$$\mathbf{Z}_4 = 15 + j(20)2 = 15 + j40 = 42.72 \angle 69.4^\circ$$

$$\mathbf{Z}_5 = j(20)3 + \frac{1}{j(20)(0.005)} = j50 = 50 \angle 90^\circ \Omega$$

The node equations are

$$\frac{24\angle 45^\circ - \mathbf{V}_a}{\mathbf{Z}_2} = \frac{\mathbf{V}_a}{\mathbf{Z}_4} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3}$$

$$\frac{24\angle 45^\circ - \mathbf{V}_b}{\mathbf{Z}_1} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3} = \frac{\mathbf{V}_b}{\mathbf{Z}_5}$$

$$\begin{bmatrix} \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} + \frac{1}{\mathbf{Z}_4} & -\frac{1}{\mathbf{Z}_3} \\ -\frac{1}{\mathbf{Z}_3} & \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_3} + \frac{1}{\mathbf{Z}_5} \end{bmatrix} \begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \end{bmatrix} = \begin{bmatrix} \frac{24\angle 45^\circ}{\mathbf{Z}_2} \\ \frac{24\angle 45^\circ}{\mathbf{Z}_1} \end{bmatrix}$$

Solving using MATLAB gives

$$\mathbf{V}_a = 7.89\angle 44.0^\circ$$

$$\mathbf{V}_b = 8.45\angle 45.1^\circ$$

so

$$v_a(t) = 7.89 \cos(20t + 44^\circ) \text{ V}$$

$$v_b(t) = 8.45 \cos(20t + 45.1^\circ) \text{ V}$$