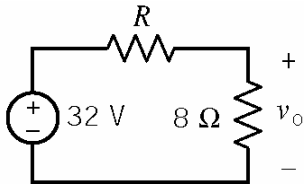


ES 250 First Midterm Practice Exam 1

1. a. To cause $v_o = 17.07$ V choose $R = \underline{\quad 7 \quad} \Omega$.




- b. To cause $v_o = 9.143$ V choose $R = \underline{\quad 20 \quad} \Omega$.

- c. If $R = 14 \Omega$ then $v_o = \underline{\quad 11.6 \quad} \text{V}$


- d. If $v_o = 14.22$ V the voltage source supplies $\underline{\quad 56.9 \quad} \text{W}$ of power.

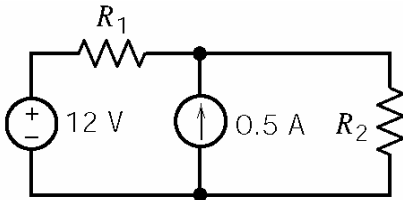2. The voltage source supplies 4.8 W of power and the current source supplies 3.6 W of power.



$$R_1 = \underline{\quad 12 \quad} \Omega \quad \text{and} \quad R_2 = \underline{\quad 8 \quad} \Omega$$

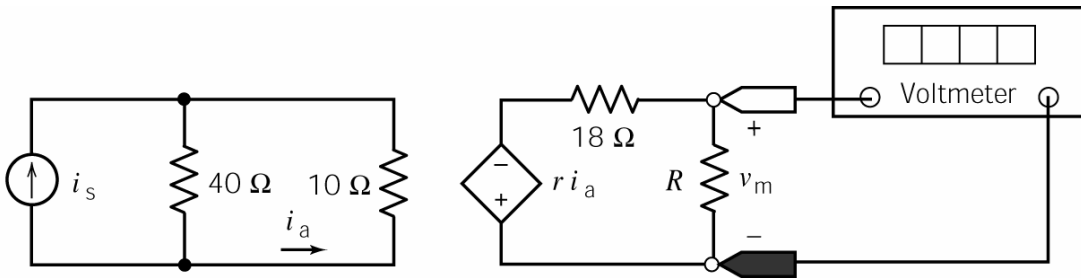3. The input to this circuit is the current of the current source, i_s . The output is the voltage measured by the meter, v_m . The output is proportional to the input, that is $v_m = k i_s$, where k is the constant of proportionality.




- a. When $i_s = 3$ A, $R = 12 \Omega$ and $r = 10$ V/A, then $i_a = \underline{\quad 2.4 \quad} \text{A}$ and $v_m = \underline{\quad 9.6 \quad} \text{V}$.

- b. When $R = 12 \Omega$, then $r = \underline{\quad 6.25 \quad} \text{V/A}$ is required to cause $v_m = 2 i_s$.

- c. When $r = 10$ V/A then $R = \underline{\quad 6 \quad} \Omega$ is required to cause $v_m = 2 i_s$.

- d. When $R = 12 \Omega$ and $i_s = 5$ A, then $r = \underline{\quad 7.5 \quad} \text{V/A}$ is required to cause $v_m = 12$ V.

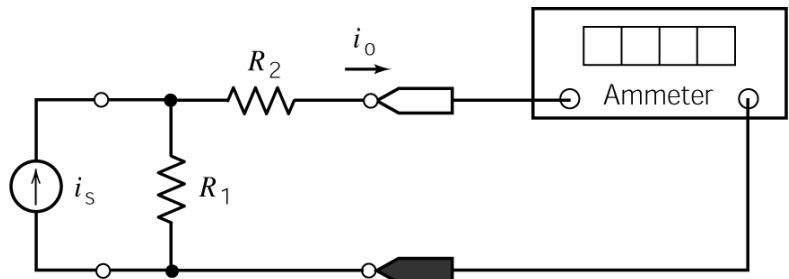4. The input to this circuit is the source current, i_s . The output is the current measured by the meter, i_o . A current divider connects the source to the meter.



Given these observations:

- A. The input $i_s = 5$ A causes the output to be $i_o = 2$ A.

B. When $i_s = 2$ A the source supplies 48 W.

The values of the resistances are $R_1 = \underline{20} \Omega$ and $R_2 = \underline{30} \Omega$.


5. In this circuit $v_2 = \frac{2}{3}v_s$, and $i_3 = \frac{1}{5}i_1$ and $v_4 = \frac{3}{8}v_2$.

Determine the values of R_1 , R_2 and R_4 .

$R_1 = \underline{8} \Omega$, $R_2 = \underline{20} \Omega$

and

$R_4 = \underline{30} \Omega$

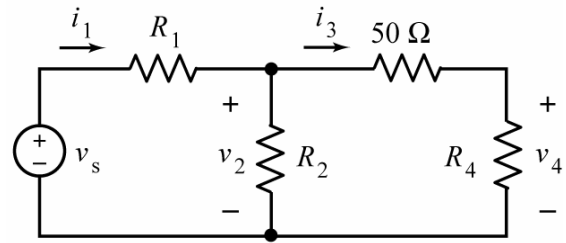

6. Given that


$v_a = 8$ V,

Determine the values of R_1 and v_o :


$R_1 = \underline{10} \Omega$,

and

$v_o = \underline{-3.2}$ V

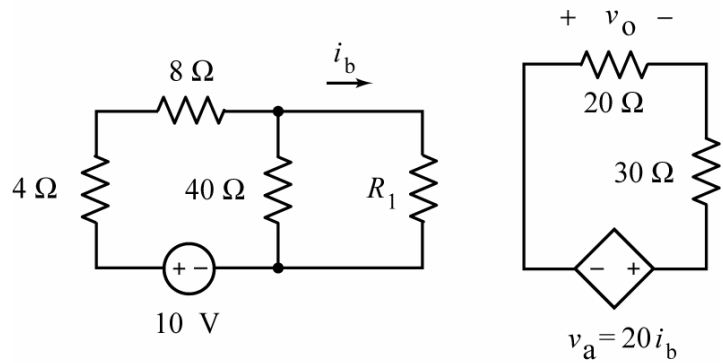

7.

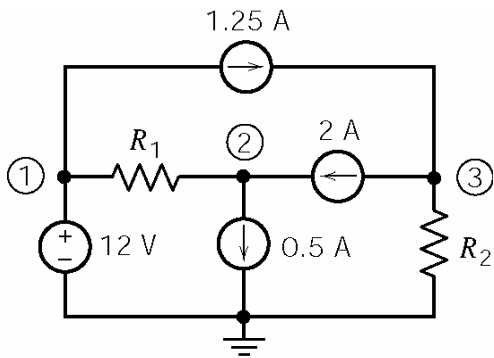

The encircled numbers are node numbers. The corresponding node voltages are

$v_1 = 12$ V, $v_2 = 21$ V and $v_3 = -3$ V,

- The 0.5 A current source **supplies** $\underline{-10.5}$ W of power.
- The 2 A current source **supplies** $\underline{48}$ W of power.
- $R_1 = \underline{6} \Omega$ and $R_2 = \underline{4} \Omega$
- The voltage source **supplies** $\underline{-3}$ W of power.