 


* Delays in a CMOS transmission gate 2-1_MUX circuit

```
.model ndev nmos(level=2,vto=1.0,tox=150e-10,kp=40e-6,gamma=0.0)
.model pdev pmos(level=2,vto=-1.0,tox=150e-10,kp=20e-6,gamma=0.0)
```

* This is a subcircuit of an inverter ($W_n=3\text{um}$, $W_p=6\text{um}$ and $L=1\text{um}$)

```
.subckt inv 1 2 ; input , output
mn1 2 1 0 0 ndev w=3um l=1um
mp1 2 1 3 3 pdev w=6um l=1um
c_lumped 2 0 0.01p
Vdd 3 0 5.0
.ends
```




* This is a subcircuit of another inverter

```
.subckt invwl 1 2 ; input , output
mn1 2 1 0 0 ndev w=3um l=1um
mp1 2 1 3 3 pdev w=6um l=1um
c_lumped 2 0 0.01p
Vdd 3 0 5.0
.ends invwl
```





* This is a subcircuit of a Transmission Gate
 
```
.subckt trg 1 2 3 4 ;input, output, contrl_sig on NMOS, contrl_sig on PMOS
mn1 1 3 2 0 ndev w=3um l=1um
mp1 1 4 2 5 pdev w=6um l=1um
Vdd 5 0 5.0
.ends trg
```



*This is for a 2-1 MUX
  
```
.subckt mux2tol 1 2 3 4 ; input1, input2, output, address
xtrg1 1 3 4 5 trg
xinv 4 5 inv
xtrg2 2 3 5 4 trg
.ends
```



* Main Input file

xmux1 1 2 8 10 mux2to1

xinv1 11 1 invw1

xinv2 22 2 invw1

c_load 8 0 0.5pf

r_shunt 8 0 100MEG

vin1 11 0 pulse(0 5 0ns 1ns 1ns 3ns 8ns)

vin2 22 0 pulse(5 0 0ns 1ns 1ns 7ns 16ns)

v_add 10 0 pulse(0 5 25ns 1ns 1ns 24ns 50ns)

.option itl5=0

.tran .1ns 60ns 0.0ns 0.1ns

.probe

.end

