

HW8

1. You may submit your results using EE446 memos having at most 3 authors.
2. Consider two inverting amplifiers, each having an ideal gain of 100. One inverting amplifier uses a compensated op amp ($R_i = 2 \text{ M}\Omega$, $R_o = 75 \text{ }\Omega$, $a_o = 200,000 \text{ V/V}$, $f_T = 1 \text{ MHz}$) and the other uses an uncompensated op amp ($R_i = 2 \text{ M}\Omega$, $R_o = 75 \text{ }\Omega$, $a_o = 200,000 \text{ V/V}$, $f_T = 1 \text{ MHz}$). (EE446 Lecture 3/25/09)
 - a. Simulate both amplifiers using PSpice to obtain gain Bode plots. (See EE446 lectures on 3/4/09 and 3/25/09 for op amp models.)
 - b. Argue that the results of these simulations show that the gain Bode plots of the inverting amplifiers consist of
 - i. a low frequency asymptote showing the ideal gain of 100 and
 - ii. the high frequency asymptote of the op amp gain Bode plot.
 - c. The introduction needs to ...
 - i. introduce and distinguish the various gains (inverting amplifiers, compensated and uncompensated op amps)
 - ii. describe the expected results, including the identifying characteristics of the low and high frequency asymptotes.
3. Due Friday, 4/3. Only “real reports” submitted Friday can be revised.