

HW9

1. You may submit your results using EE446 memos having at most 3 authors.
2. Consider two inverting amplifiers, each having an ideal gain of 100. One inverting amplifier uses a compensated op amp ($R_i = 2 \text{ M}\Omega$, $R_o = 75 \text{ }\Omega$, $a_o = 200,000 \text{ V/V}$, $f_T = 1 \text{ MHz}$) and the other uses an uncompensated op amp ($R_i = 2 \text{ M}\Omega$, $R_o = 75 \text{ }\Omega$, $a_o = 200,000 \text{ V/V}$, $f_T = 1 \text{ MHz}$). (EE446 Lecture 3/25/09)
 - a. Simulate both amplifiers using PSpice to obtain the Bode plots for the loop gain.
 - b. Use those Bode to determine the bandwidth and phase margins of both amplifiers.
 - c. Evaluate the suitability of both amplifiers for amplifying speech signals (e.g. signals having components in the frequency range 200-8000 Hz.)
 - d. The introduction needs to ...
 - i. introduce loop gain, phase margin and bandwidth. (In particular, make certain that the reader will not confuse “gain” and “loop gain”.)
 - ii. describe the criteria for evaluating the suitability of amplifiers for amplifying speech signals.
3. Due Monday, 4/6.