

Circuit A\* is obtained from Circuit A by



- replacing all independent voltage sources by short circuits
- and
- replacing all independent current sources by open circuits.

### Problem 5.4-5


We want to find the Thevenin equivalent circuit for this circuit:

There is a dependent source in this circuit so we will not be able to reduce this circuit to its Thevenin equivalent circuit using source transformations and equivalent resistance.

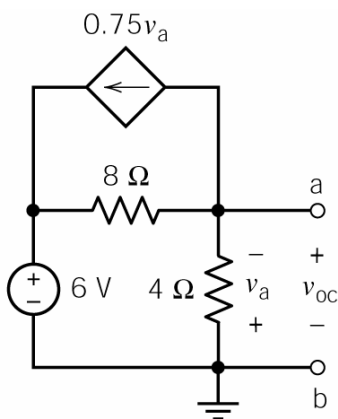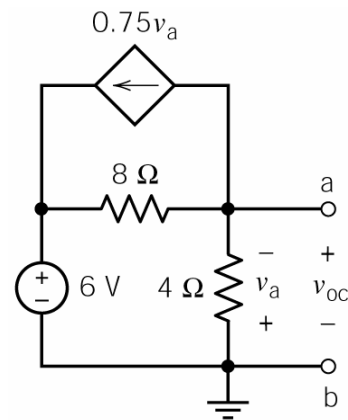
We will need to find  $v_{oc}$ ,  $i_{sc}$  and  $R_t$ . Figure 5.4-3 shows this is done. Replace “Circuit A” in Figure 5.4-3 with the circuit in this problem to get



(a)

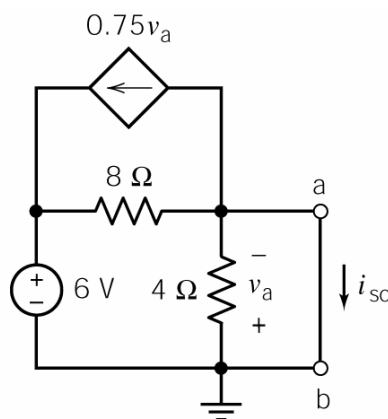


(b)

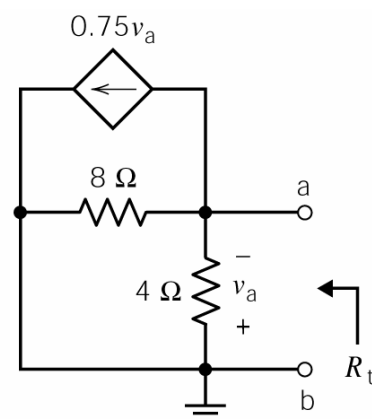

(c)

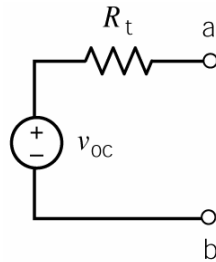After we have determined the value of  $v_{oc}$ ,  $i_{sc}$  and  $R_t$ , we can draw the Thevenin equivalent circuit as



Let's find  $v_{oc}$  using the circuit shown above in (a):

Notice that  $v_{oc}$  is the node voltage at node a. Express the controlling voltage of the dependent source as a function of the node voltage:

$$v_a = -v_{oc}$$

Apply KCL at node a:

$$-\left(\frac{6-v_{oc}}{8}\right) + \frac{v_{oc}}{4} + \left(-\frac{3}{4}v_{oc}\right) = 0$$

so

$$-6 + v_{oc} + 2v_{oc} - 6v_{oc} = 0 \Rightarrow v_{oc} = -2 \text{ V}$$

Let's find  $i_{sc}$  using the circuit shown above in (b):

Notice that the short circuit forces

$$v_a = 0$$



Apply KCL at node a:


$$-\left(\frac{6-0}{8}\right) + \frac{0}{4} + \left(-\frac{3}{4}(0)\right) + i_{sc} = 0$$

Solving this equation gives

$$i_{sc} = \frac{6}{8} = \frac{3}{4} \text{ A}$$

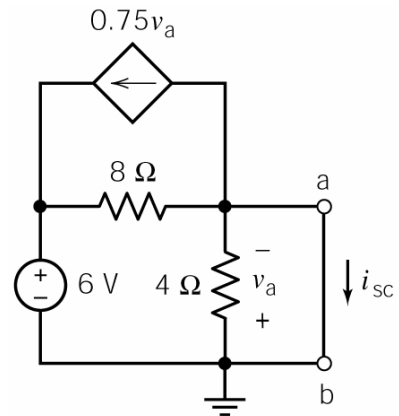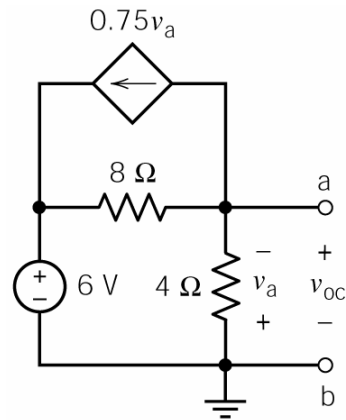Once we have found  $v_{oc}$  and  $i_{sc}$  we can calculate  $R_t$  using  $R_t = \frac{v_{oc}}{i_{sc}} = \frac{-2}{\frac{3}{4}} = -\frac{8}{3} \Omega$ . Then the Thevenin equivalent can be drawn as



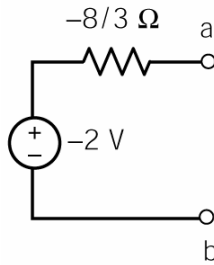


**Alternate derivation of  $R_t$ :**

Figure 5.4-4 illustrates a procedure for calculating  $R_t$  by connecting a current source across the terminals of Circuit A\* and then calculating the voltage across that current source.

Notice that Figure 5.4-3(c) and Figure 5.4-4 refer to Circuit A\* instead of Circuit A. Circuit A\* is obtained from Circuit A by setting all of the *independent* sources to zero.

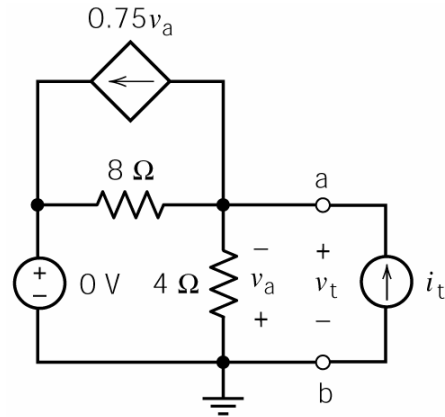There is only one independent source in our circuit, the 6 V voltage source. A zero voltage source is equivalent to a short circuit. First we set that source to zero and we replaced it with the equivalent short circuit.



We use this circuit to calculate the Thevenin resistance as the ratio

$$R_t = \frac{v_t}{i_t}$$

Let's do that calculation:

First, notice that  $v_a = -v_t$ . Next apply KCL at node a:


$$0.75v_a + \frac{v_t}{8} = \frac{v_a}{4} + i_t$$

so

$$i_t = \frac{v_t}{8} + \frac{v_t}{4} - 0.75v_t = -\frac{3}{8}v_t$$

Then
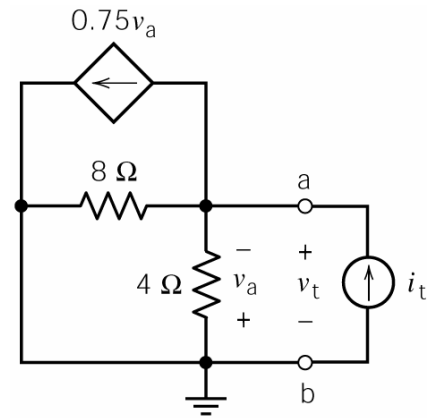
$$\frac{v_t}{i_t} = -\frac{8}{3} \Rightarrow R_t = -\frac{8}{3} \Omega$$




**Remark:** We may be bothered by the negative Thevenin resistance. A negative Thevenin resistance may not be desirable, but it is a possibility when the circuit contains a dependent source.

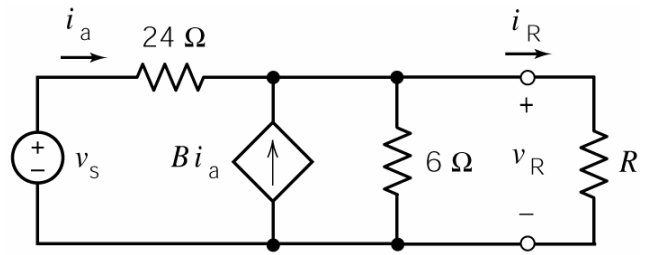2. Given that  $0 \leq R \leq \infty$  in this circuit, consider these two observations:

When  $R = 2 \Omega$  then  $v_R = 4 \text{ V}$  and  $i_R = 2 \text{ A}$ .


When  $R = 6 \Omega$  then  $v_R = 6 \text{ V}$  and  $i_R = 1 \text{ A}$ .



Fill in the blanks in the following statements:

- The maximum value of  $i_R$  is 4 A.
- The maximum value of  $v_R$  is 8 V.
- The maximum value of  $p_R = i_R v_R$  occurs when  $R =$  2  $\Omega$ .
- The maximum value of  $p_R = i_R v_R$  is 16 W.
- When  $R = 5 \Omega$  then  $v_R =$  5.714 V.
- When  $R =$  8  $\Omega$  then  $v_R = 6.4 \text{ V}$ .
- When  $R =$  14  $\Omega$  then  $i_R = 500 \text{ mA}$ .

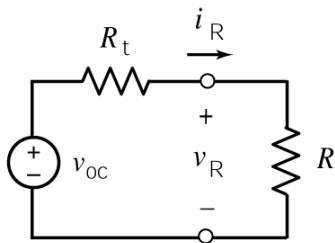We can replace the part of the circuit to the left of the terminals by its Thevenin equivalent circuit:



Using voltage division  $v_R = \frac{R}{R + R_t} v_{oc}$  and using Ohm's law  $i_R = \frac{v_{oc}}{R + R_t}$ .

By inspection,  $v_R = \frac{R}{R + R_t} v_{oc} = \frac{v_{oc}}{1 + \frac{R_t}{R}}$  will be maximum when  $R = 0$ . The

maximum value of  $v_R$  will be  $v_{oc}$ . Similarly,  $i_R = \frac{v_{oc}}{R + R_t}$  will be

maximum when  $R = 0$ . The maximum value of  $i_R$  will be  $\frac{v_{oc}}{R_t} = i_{sc}$ .

The maximum power transfer theorem tells us that  $p_R = i_R v_R$  will be maximum when  $R = R_t$ . Then

$$p_R = i_R v_R = \left( \frac{v_{oc}}{R + R_t} \right) \left( \frac{R}{R + R_t} v_{oc} \right) = R \left( \frac{v_{oc}}{R + R_t} \right)^2.$$

Let's substitute the given data into the equation  $i_R = \frac{v_{oc}}{R + R_t}$ .

When  $R = 2 \Omega$  we get  $2 = \frac{v_{oc}}{2 + R_t} \Rightarrow 4 + 2R_t = v_{oc}$ . When  $R = 6 \Omega$  we get  $1 = \frac{v_{oc}}{6 + R_t} \Rightarrow 6 + R_t = v_{oc}$ .

So  $6 + R_t = 4 + 2R_t \Rightarrow R_t = 2 \Omega$  and  $v_{oc} = 4 + 2R_t = 8 \text{ V}$ . Also  $i_{sc} = \frac{v_{oc}}{R_t} = \frac{8}{2} = 4 \text{ A}$ .

Now the blanks can be easily filled-in.