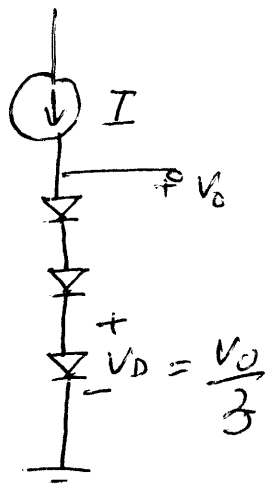


Solution to Hour Exam I

1.



$$I_S = 10^{-14} \quad n = 1$$

$$I_D = I = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$\approx 10^{-14} e^{\frac{0.667}{1 \times 0.025}}$$

$$= 3.86 \text{ mA}$$

if current increases by 1 mA

$$(V_D + \Delta V_D) (\text{per diode}) = 0.667 + 1 \times 0.025 \times 2.3 \log_{10} \frac{4.86}{3.86}$$

$$= (0.667 + 0.0575) \text{ V}$$

$$\Delta V_D (\text{per diode}) = 0.0575 \text{ V} \quad \overline{V_D = \frac{nV_T}{I} \text{ (small sig. model)}}$$

$$\Delta V_0 = 3 \times 0.0575 = 17.25 \text{ mV} \quad \left| \begin{array}{l} \Delta V_0 = 3V_D \times 1 \text{ mA} \\ = \frac{25}{3.86} \times 3 = 19.4 \text{ mV} \end{array} \right.$$

2. $V_Z = 10 \text{ V} \quad I_Z = 25 \text{ mA} \quad r_Z = 10 \Omega$ $\frac{19.4}{3} = 6.47 \text{ V}$
not much less than nV_T

$$V_{Z0} = V_Z - I_Z r_Z = 10 - 25(\text{mA}) \times 0.01 \text{ k}\Omega$$

$$= 10 - 0.25 = 9.75 \text{ V}$$

$$\text{Line regulation} = 0.05 = \frac{10}{R + 10}$$

$$R + 10 = \frac{10}{0.05} \Rightarrow R = 190 \Omega$$

Now $R = \frac{V_{S\text{min}} - V_{Z0} - r_Z I_{Z\text{min}}}{I_{Z\text{min}} + I_{L\text{max}}}$

$$190 = \frac{V_{S\text{min}} - 9.75 - 0.01 \times 5}{(5 + 20) \times 10^{-3}} = \frac{V_{S\text{min}} - 9.8}{25 \times 10^{-3}}$$

$$V_{S\text{min}} = 190 \times 25 \times 10^{-3} + 9.8 = 4.75 + 9.8 = 14.55 \text{ V}$$

Max power $P_{\max} = 1 \text{ W}$

$$1 = (V_{z0} + I_{z\max} r_z) I_{z\max}$$
$$= 9.75 I_{z\max} + 10 I_{z\max}^2$$

$$10 I_{z\max}^2 + 9.75 I_{z\max} - 1 = 0$$

$$I_{z\max} = \frac{-9.75 \pm \sqrt{9.75^2 + 40}}{20} = 93.58 \text{ mA}$$

$$\therefore V_{s\max} = I_{z\max} (R + r_z) + 9.75$$

$$= 93.58 (0.2 \text{ k}) + 9.75 = 28.46 \text{ V}$$

3.

