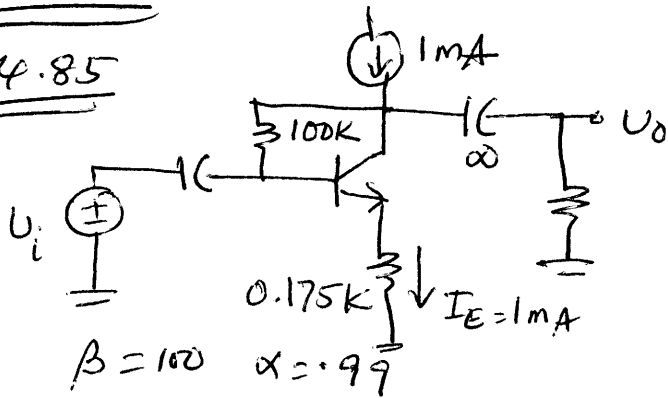


EE341

Solution to Take Home Exam

P4.85



$\beta = 100 \quad \alpha = 0.99$

$r_e = \frac{V_T}{I_E} \approx 0.025k$


(a) $I_E = 1mA \quad I_B =$

$\therefore I_E = \alpha I_C \approx 0.99mA$

$V_C = I_C R_C + 0.7 + I_B R_B$

$= 1 \times 0.175 + 0.7 + \frac{1}{101} \times 100k$
 $= 1.875V$

(b)

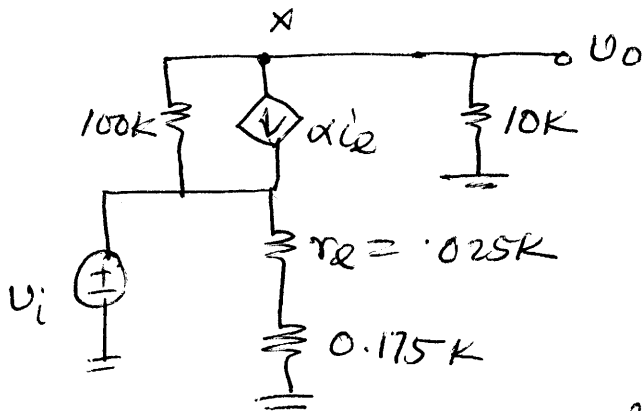

$i_e = \frac{U_i}{r_e + R_E} = \frac{U_i}{(0.025 + 0.175)k}$
 $= \frac{U_i}{0.2k}$


Let us write a node equation at x

$\frac{U_o - U_i}{100k} + \alpha i_e + \frac{U_o}{10k} = 0$

$0.01U_o - 0.01U_i + \frac{0.99U_i}{0.2} + 0.1U_o = 0$

$0.11U_o = -4.94U_i \Rightarrow \frac{U_o}{U_i} = A_V = -44.9V/V$

P4.92

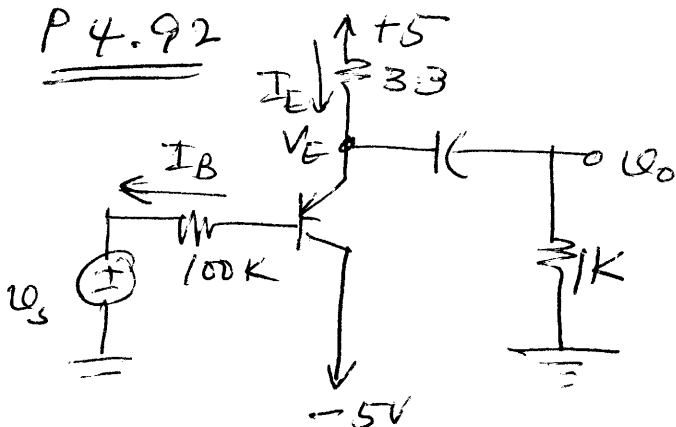

$\beta = 120$


$5 = I_E R_E + 0.7 + I_B R_B$

$\Rightarrow I_E = \frac{5 - 0.7}{3.3 + \frac{100}{121}} \approx 1.042mA$

$r_e = \frac{V_T}{I_E} \approx 24\Omega$

$V_E = 5 - 3.3 \times 1.042 = 1.56V$

Small signal equivalent ckt

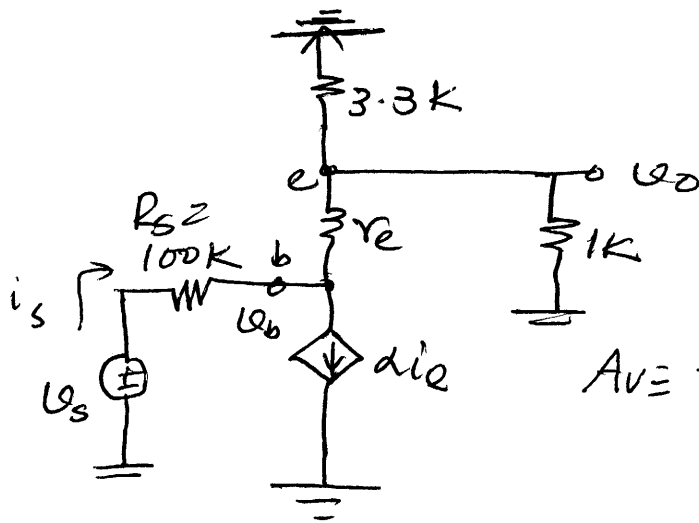

$$R_{in} \cong \frac{v_b}{i_b} = (1+\beta)(r_e + 3.3\text{k}\Omega) = 95.8\text{k}\Omega$$

$$A_v \equiv \frac{v_o}{v_s} = \frac{v_o}{v_b} \cdot \frac{v_b}{v_s} = \frac{(3.3\text{k}\Omega)}{r_e + (3.3\text{k}\Omega)} \cdot \frac{R_{in}}{R_{in} + 100\text{k}\Omega} = 0.474\text{ V/V}$$

$$\frac{i_o}{i_s} = \frac{v_o/R_L}{v_s/(R_s + R_{in})} = \frac{v_o}{v_s} \cdot \left(\frac{R_s + R_{in}}{R_L} \right) = 0.474 \cdot \frac{(195.8)}{1\text{k}} = 92.9\text{ A/A}$$

$$R_o = 3.3\text{k}\Omega \parallel \left(r_e + \frac{100}{1+\beta} \right) = 0.676\text{k}\Omega$$

Max input amplitude:

If we want to limit $\hat{v}_{be} \cong 5\text{mV}$ then

$$\hat{v}_{be} = \frac{(1+\beta)r_e \hat{v}_s}{R_s + R_{in}} = \frac{2.9}{195.8} \hat{v}_s$$

$$\therefore \hat{v}_s = \frac{195.8}{2.9} \times 5\text{mV} = 0.338\text{V}$$

However if we allow \hat{v}_o to be such that the transistor turns off: ($i_E = 0$):

$$v_E = v_B + \hat{v}_o \quad \text{when } v_o = +\hat{v}_o$$

$$\therefore \frac{5 - (v_E + \hat{v}_o)}{3.3\text{k}\Omega} = \frac{+\hat{v}_o}{1\text{k}\Omega} \Rightarrow \hat{v}_o = \frac{5 - 1.56}{4.3} = 0.8\text{V}$$


$$\therefore \hat{v}_s = \hat{v}_o / A_v = 1.68\text{V}$$

So the max allowable input voltage
 $\rightarrow \hat{V}_s = 0.338 \text{ V}$

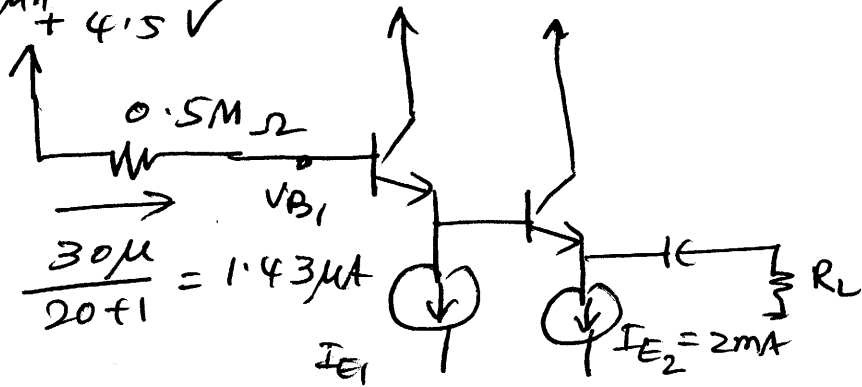
4.96 $I_{E2} = 2 \text{ mA}$ $I_{E1} = 20 \mu\text{A} + I_{B2}$
 (a) $= 20 + \frac{2000 \mu\text{A}}{201} \approx 30 \mu\text{A}$

$V_{B1} = 4.5 - 0.5 \text{ M}\Omega \times 1.43 \mu\text{A} + 4.5 \text{ V}$
 $= 3.79 \text{ V}$

$V_{B2} = 3.79 - 0.7$
 $= 3.09 \text{ V}$



Small signal equivalent ckt

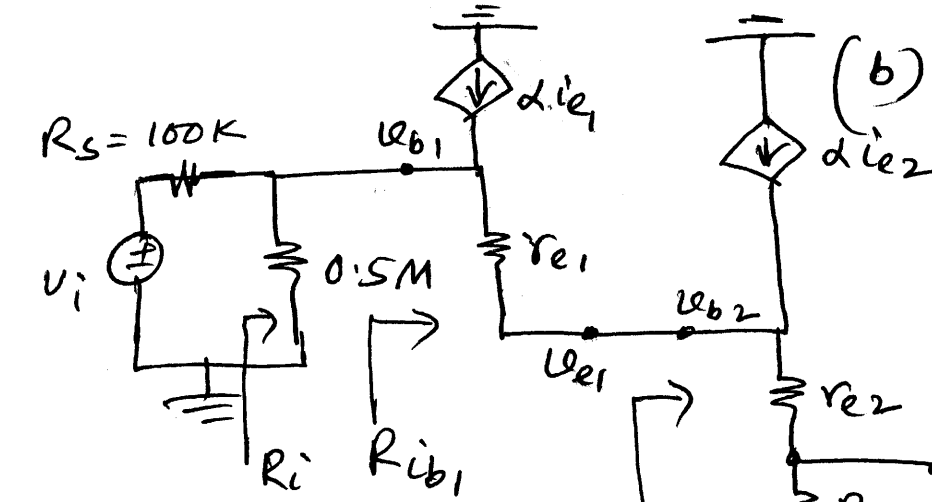

(b) $\frac{v_o}{v_{b2}} = \frac{R_L}{r_{e2} + R_L}$
 $r_{e2} = \frac{25}{2} = 12.5 \Omega$
 $R_L = 1 \text{ k}\Omega$

$R_{ib2} = (1 + \beta_2)(r_{e2} + R_L)$
 $= 201 \times (1.0125)$
 $= 203.5 \text{ k}\Omega$

$\therefore \frac{v_o}{v_{b2}} = 0.988 \text{ V/V}$
 $r_{e1} = \frac{25 \text{ mV}}{30 \mu\text{A}} = 0.83 \text{ k}\Omega$

(c) $\frac{v_{e1}}{v_{b1}} = \frac{v_{b2}}{v_{b1}} = \frac{R_{ib2}}{r_{e1} + R_{ib2}} = \frac{203.5}{203.5 + 0.83} = 0.996 \text{ V/V}$

$$\begin{aligned}
 R_i &= 0.5M \parallel (1+\beta_1)(r_{e1} + R_{i'b2}) \\
 &= 0.5M \parallel (21)(0.83 + 203.5) \\
 &= (0.5 \parallel 4.29)M = 0.448M\Omega \\
 &= 448k\Omega
 \end{aligned}$$

$$(d) \frac{V_{b1}}{V_s} = \frac{R_i}{R_i + R_s} = \frac{448}{448 + 100} = 0.818 \text{ V/V}$$

$$\begin{aligned}
 (e) \frac{V_o}{V_s} &= \frac{V_{b1}}{V_s} \cdot \frac{V_{e1}}{V_{b1}} \cdot \frac{V_o}{V_{e1}} = 0.818 * 0.996 * 0.988 \\
 &= 0.805 \text{ V/V}
 \end{aligned}$$

Max input amplitude

$$\begin{aligned}
 \underline{\text{Note}} \quad V_{be1} &= \frac{(1+\beta_1)r_{e1} V_{b1}}{R_{i'b1}} = \frac{(1+\beta_1)r_{e1} V_{b1}}{(1+\beta_1)r_{e1} + \underbrace{(1+\beta_1)(1+\beta_2)}_{(r_{e2} + R_L)} * (1+\beta_1)R_{i'b2}} \\
 &= \frac{21(0.81)V_{b1}}{21(0.81 + 203.5)}
 \end{aligned}$$

$$* V_{be2} = \frac{(1+\beta_1)(1+\beta_2)r_{e2} V_{b1}}{21(0.81 + 203.5)} = \frac{21 * 2.51 * V_{b1}}{21(0.81 + 203.5)}$$

$$\therefore V_{be2} > V_{be1}$$

$$\begin{aligned}
 \therefore \frac{V_{be2}}{V_s} &= \frac{V_{be2}}{V_{b1}} \cdot \frac{V_{b1}}{V_s} = \frac{21 * 2.51}{21(0.81 + 203.5)} * 0.818 \\
 &= 10^{-2} \text{ V/V}
 \end{aligned}$$

$$\text{if } \hat{V}_{be} = 5 \text{ mV} \Rightarrow \hat{V}_s = \frac{5 \text{ mV}}{10^{-2}} = 0.5 \text{ V}$$

5

when $i_{E2} = 0$ $I_{RL} = -2\text{mA}$

$$| \hat{V}_0 | = (2 \times 1) = 2\text{V}$$

$$\therefore \hat{V}_S = \frac{2\text{V}}{0.805} = 2.48\text{V}$$

\therefore the max input amplitude
is 0.5V .