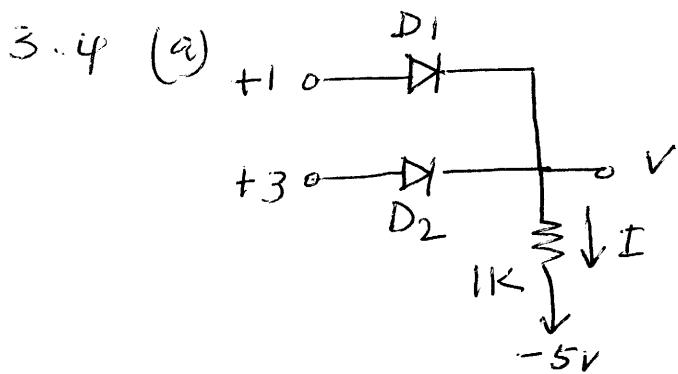


Assignment #1

Assume $D_1 \& D_2$ both ON.


Then $V = 1$ & $V = 3V$
Not possible.

Assume D_1 is on & D_2 is off
then $V = 1V$ & D_2 cannot
be off.

Thus D_2 must be ON & D_1 must be off
 $\therefore V = 3V$ which makes D_1 reverse biased

$$\therefore I = \frac{3 - (-5)}{1K} = 8mA$$

(b)

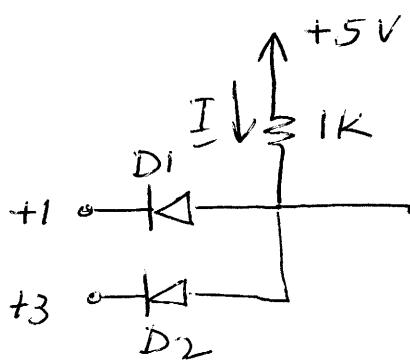

$D_1 \& D_2$ cannot both be ON.

Else $V = 1V$ & $V = 3V$ which
is impossible

If we assume D_2 is ON & D_1 is off $\Rightarrow V = 3V$
which means D_1 will be forward biased
& will have to be ON.


So D_2 must be off & D_1 is ON

$$\therefore V = 1V \quad \& \quad I = \frac{4V}{1K} = 4mA$$

3.23 If a second diode is added the current per diode will be $I/2$

$$\therefore \Delta V = 2 \cdot 3nV_T \log \frac{I/2}{I} = -2 \cdot 3nV_T \ln 2 \approx -18mV$$

Assignment # 4

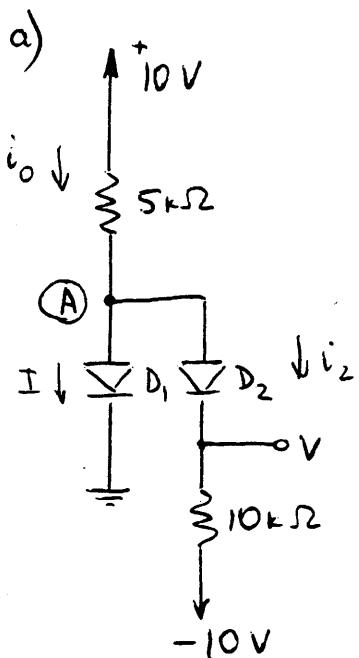Problem P 3.9

The diodes D_1 and D_2 are ideal, but have voltage drop 0.7 V across them.

Suppose, D_1 is not conducting (cut off), and D_2 is conducting.

Then the current through D_2 will be:

$$i_2 = \frac{10\text{ V} - (-10\text{ V}) - 0.7\text{ V}}{5\text{k}\Omega + 10\text{k}\Omega} = 1.28\text{ mA}$$

$V_A = 1.28\text{ mA} \cdot 10\text{k}\Omega + 0.7\text{ V} - 10\text{ V} = 3.56\text{ V} \Rightarrow$ diode D_1 is conducting and our assumption is wrong. By the same reason we can prove that the case when D_1 is conducting and D_2 is cut off is also wrong. So, both diodes are conducting.

Then $V_A = 0.7\text{ V}$. We need to find $I = i_0 - i_2$

$$i_0 = \frac{10\text{ V} - 0.7\text{ V}}{5\text{k}\Omega} = 1.86\text{ mA}$$

$$i_2 = \frac{V_A - 0.7\text{ V} + 10\text{ V}}{10\text{k}\Omega} = \frac{10\text{ V}}{10\text{k}\Omega} = 1\text{ mA}$$


$$V = 0.7\text{ V} - 0.7\text{ V} = 0$$

$$I = i_0 - i_2 = 1.86\text{ mA} - 1\text{ mA} = 0.86\text{ mA}$$

Answer: $I = 0.86\text{ mA}$; $V = 0$

Problem P3.9

b)

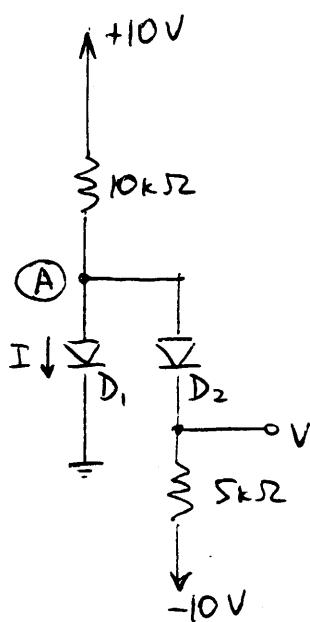

Similar to P3.9(a) we assume that D_1 is not conducting (cut off)

The current through D_2 will be:

$$i_2 = \frac{10V - (-10V) - 0.7V}{10k\Omega + 5k\Omega} \approx 1.28 \mu A$$

$$V_A = 1.28 \mu A \cdot 5k\Omega + 0.7V - 10V \approx -2.9V < 0.7V$$

So, the assumption was correct and D_1 is cut off
and $I = 0$



$$V = V_A - 0.7V = -2.9V - 0.7V = -3.6V$$

Answers: $I = 0$; $V \approx -3.6V$

P.S. Actually, one should check the case when both diodes are conducting and prove that it's wrong. If both diodes are conducting, then the resulting current through D_1 will be in opposite direction than it's shown in the figure. This means that D_1 is cut-off, and the assumption that both D_1 and D_2 are conducting is wrong.

Problem 3.13

Applied voltage :

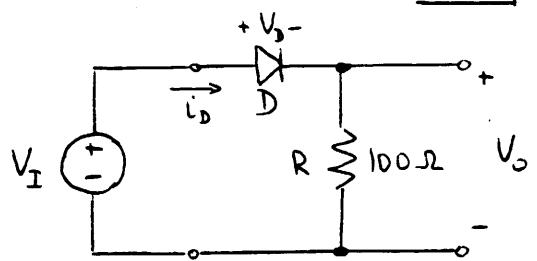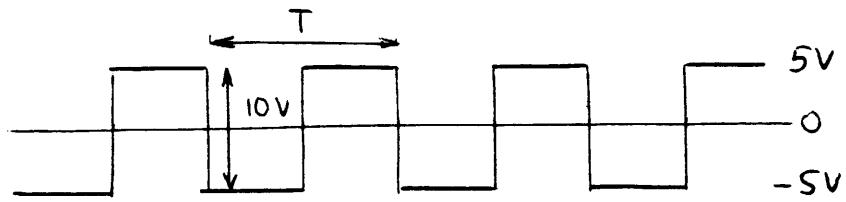

Diode conducting for half the cycle ($T/2$)

$$V_D = 0, V_O = V_{I_{max}} = 5V$$

$$i_D = \frac{5V}{100\Omega} = 50\text{ mA}$$

$$V_O \text{ average} = \frac{V_O}{2} = 2.5V \quad i_D \text{ average} = 25\text{ mA}$$

$$V_{I_{max\ reverse}} = -5V$$


Problem 3.14

The average voltage $V_{I_{average}}$ should be 2V

$$\text{Then } 2V = \frac{1}{T} \left(\frac{V_{I_{max}} \cdot T}{2} + \frac{(V_{I_{max}} - 10V) \cdot T}{2} \right)$$

$$\text{It follows } V_{I_{max}} = 7V$$

Applied voltage :

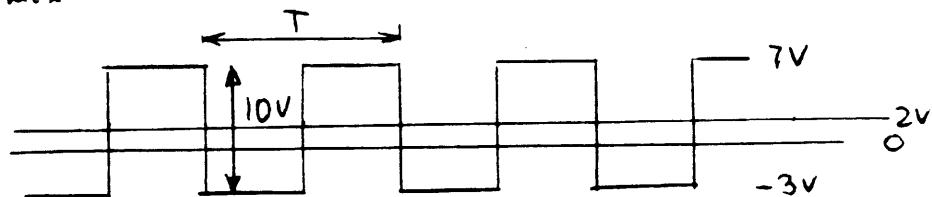

Diode still conducting for half the cycle ($T/2$)


$$V_D = 0, V_O = V_{I_{max}} = 7V$$

$$i_D = \frac{7V}{100\Omega} = 70\text{ mA}$$

$$V_O \text{ average} = \frac{V_O}{2} = 3.5V \quad i_D \text{ average} = 35\text{ mA}$$

$$V_{I_{max\ reverse}} = -3V$$

Problem P3.26

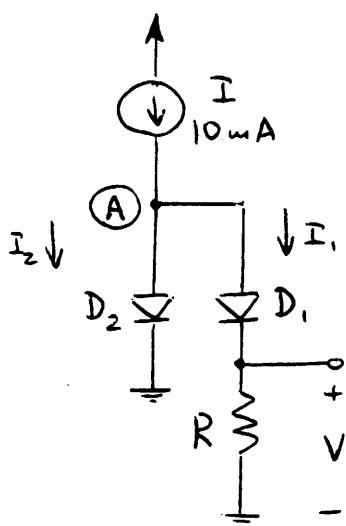

D_1 and D_2 are identical.

From their i-V characteristics: $10\text{mA} @ 0.7\text{V}$
 $100\text{mA} @ 0.8\text{V}$

First, let's find n and I_s of the diodes

For any two operating points of a diode:

$$n = \frac{V_2 - V_1}{2.3 V_T \log_{10} \frac{i_2}{i_1}}$$

$$\text{let } V_1 = 0.7\text{V} \quad i_1 = 10\text{mA}$$

$$V_2 = 0.8\text{V} \quad i_2 = 100\text{mA}$$

$$\text{Then } n = \frac{0.8\text{V} - 0.7\text{V}}{2.3 \cdot 0.025\text{V} \log_{10} \left(\frac{100\text{mA}}{10\text{mA}} \right)} = \frac{0.1\text{V}}{23 \cdot 0.025\text{V} \cdot 1} = \underline{\underline{1.739}}$$

$$I_s = i_1 \exp \left(-\frac{V_1}{n V_T} \right) = 10\text{mA} \cdot \exp \left(-\frac{0.7\text{V}}{1.739 \cdot 0.025\text{V}} \right) = \\ = 10^{-2}\text{A} \cdot 10^{-\frac{0.7\text{V}}{2.3 \cdot 1.739 \cdot 0.025}} = 10^{-2}\text{A} \cdot 10^{-7} = \underline{\underline{10^{-9}\text{A}}}$$

$$\boxed{n = 1.739; I_s = 10^{-9}\text{A}}$$

Now, most of the students approximated $n = 1.739$ by $n = 2$. You cannot do this since it changes the characteristics drastically. If $n = 1.739$, then for $V = 0.7\text{V}$ $I = 10\text{mA}$ (as given). If $n = 2$, then for $V = 0.7\text{V}$ $I = 10^{-9}\text{A} \cdot \exp \left(\frac{0.7\text{V}}{2.0075\text{V}} \right) = 1.22\text{mA}$, more than 8 times smaller. Most of the students ~~were~~ could not find the solution just because of this approximation.

Second, to find the value of R for given V , you need to find I through D_1 and R .

$$\text{From circuit theory, } I = I_1 + I_2; \quad V_{D_2} = V_{D_1} + V_R = V_{D_1} + 0.05\text{V}$$

$$I_1 = I_{D_1} = I_R$$

We can write the equation for currents, substituting $V_{D_1} + 0.05V$ instead of V_{D_2} into that equation.

$$\underbrace{I_s \exp\left(\frac{V_{D_1} + 0.05V}{n \cdot V_T}\right)}_{I_2} + \underbrace{I_s \exp\left(\frac{V_{D_1}}{n \cdot V_T}\right)}_{I_1} = I$$

$$\text{or } 10^{-9}A \cdot \exp\left(\frac{V_{D_1} + 0.05V}{1.739 \cdot 0.025V}\right) + 10^{-9}A \cdot \exp\left(\frac{V_{D_1}}{1.739 \cdot 0.025V}\right) = 10^{-2}A$$

and we are able to solve for V_{D_1} :

$$\exp\left(\frac{V_{D_1}}{1.739 \cdot 0.025V}\right) \cdot \left(1 + \exp\left(\frac{0.05V}{1.739 \cdot 0.025V}\right)\right) = 10^7 \quad \text{or}$$

$$\exp\left(\frac{V_{D_1}}{1.739 \cdot 0.025V}\right) = \frac{10^7}{4.158} \Rightarrow V_{D_1} = 2.3 n V_T (7 - \log_{10} 4.158) = \underline{\underline{0.638 \text{ V}}}$$

If you solve for V_{D_2} , substituting $V_{D_1} = V_{D_2} - 0.05V$, you should get $\underline{\underline{0.688 \text{ V}}}$.

Now, we are able to find the current I_1 :

$$I_1 = I_s \exp\left(\frac{V_{D_1}}{n \cdot V_T}\right) = 10^{-9}A \cdot \exp\left(\frac{0.638V}{1.739 \cdot 0.025V}\right) = 10^{-9}A \cdot \exp(14.67) =$$

$$\approx 10^{-9}A \cdot 10^{6.38} = \underline{\underline{2.4 \mu\text{A}}}$$

$$R = \frac{V_R}{I_1} = \frac{0.05V}{2.4 \cdot 10^{-3}A} = \underline{\underline{20.82 \Omega}}$$

Answers : $n = 1.739$; $I_s = 10^{-9}A$, $R = 20.82 \Omega$
