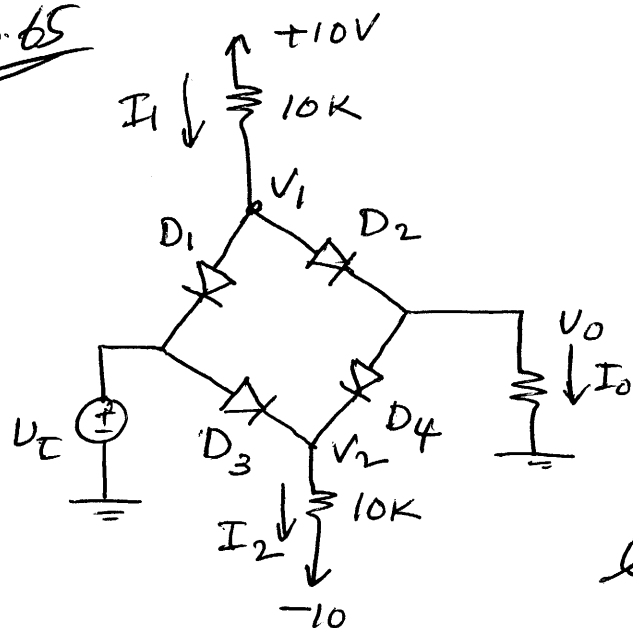


Assignment #2

EE 341

3.65



Consider first $V_i > 0$

Assume $V_i \leq 4.65V$

All the diodes will conduct.

$$V_1 = V_i + 0.7$$

$$V_o = V_1 - 0.7 = V_i$$

Note: as V_i increases from zero, I_1 will decrease but both I_0 & I_2 will increase.

When $V_i = 4.65V$, $V_1 = 4.65 + 0.7 = 5.35V$

$$\therefore I_1 = \frac{10 - 5.35}{10K} = 0.465mA$$

Since $V_o = V_i$ $I_0 = \frac{4.65}{10K} = 0.465mA$

Thus all the current I_1 will be diverted toward the output. Beyond that D_1 & D_4 will turn off & V_o will remain fixed at $4.65V$.


Since the circuit is symmetrical, the same argument can be used to show that when $V_i < 0$ $V_o = V_i$ as long as $V_i > -4.65V$. If $V_i < -4.65V$, D_2 & D_3 will be off & V_o will remain fixed as $-4.65V$.

3.77 $V_z = V_{z0} + I_z r_z \therefore V_{z0} = V_z - r_z I_z = 9.1 - 0.005 \times 28 = 8.96$

$$V_z (I_z = 10mA) = V_{z0} + I_z r_z = 9.101V$$

$$V_z (I_z = 100mA) = V_{z0} + I_z r_z = 9.46V$$

Problem P 370

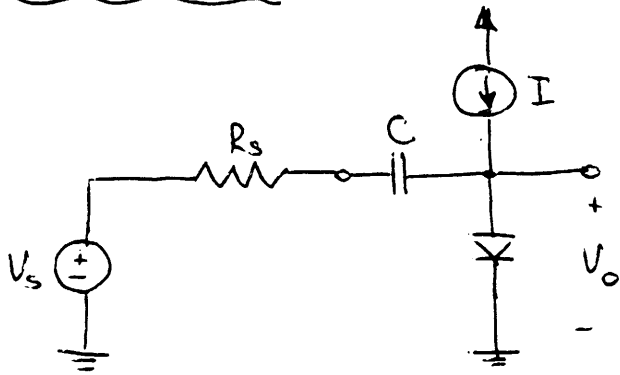

Small signal model requires that @ the operating point $I-V_D$, where diode is conducting,

$$V_s \ll V_D, \quad V_s \ll nV_T,$$

a small change in a signal V_s gives rise to a change in V_o

$$\text{Let } V_o = \tilde{V}_o(\text{const } I) + V_o'(\text{signal})$$

Using the voltage-divider rule for a small signal

$$\frac{V_o'}{V_s} = \frac{r_D}{R + r_D} \quad r_D = \frac{nV_T}{I} \quad \text{Substituting, } \frac{V_o'}{V_s} = \frac{\frac{nV_T}{I}}{R + \frac{nV_T}{I}}$$

$$\text{It follows that } V_o' = V_s \cdot \frac{nV_T}{RI + nV_T}$$

$$\text{Now } R_s = 1k\Omega, \quad n = 2, \quad V_s = 10 \mu V$$

$$\text{a) } I = 1 \text{ mA} \quad V_o' = 10 \mu V \cdot \frac{2 \cdot 0.025 \text{ V}}{1k\Omega \cdot 1 \text{ mA} + 2 \cdot 0.025 \text{ V}} = 0.0476 \cdot 10 \mu V = \underline{\underline{0.476 \mu V}}$$

$$\text{b) } I = 0.1 \text{ mA} \quad V_o' = 10 \mu V \cdot \frac{2 \cdot 0.025 \text{ V}}{1k\Omega \cdot 0.1 \text{ mA} + 2 \cdot 0.025 \text{ V}} = 0.333 \cdot 10 \mu V = \underline{\underline{3.33 \mu V}}$$

$$\text{c) } I = 1 \mu A \quad V_o' = 10 \mu V \cdot \frac{2 \cdot 0.025 \text{ V}}{1k\Omega \cdot 0.001 \text{ mA} + 2 \cdot 0.025 \text{ V}} = 0.98 \cdot 10 \mu V = \underline{\underline{9.8 \mu V}}$$

Even for the case c) $V_o' = 9.8 \mu V \ll nV_T = 50 \mu V$, but it's close to the limit where a small-signal model is valid.

$$V_o' = \frac{1}{2} V_s \Rightarrow (RI + nV_T)^{\frac{1}{2}} = nV_T \Rightarrow RI = nV_T \Rightarrow I = \frac{nV_T}{R}$$

$$I = \frac{2 \cdot 0.025 \text{ V}}{1k\Omega} = \underline{\underline{0.05 \mu A}}$$