
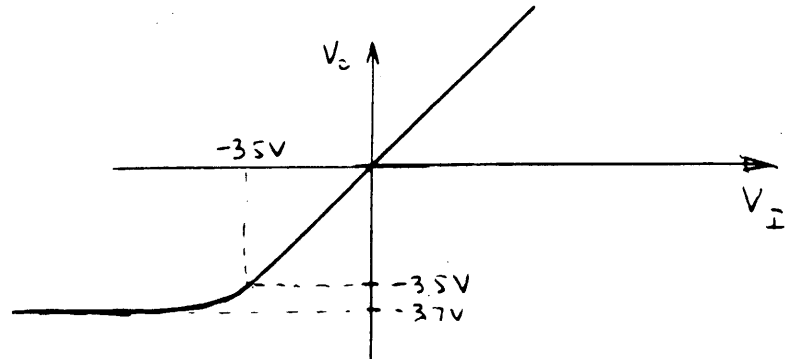
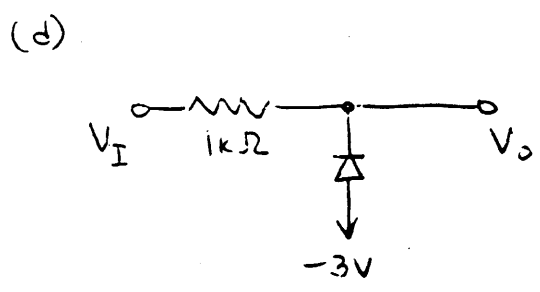
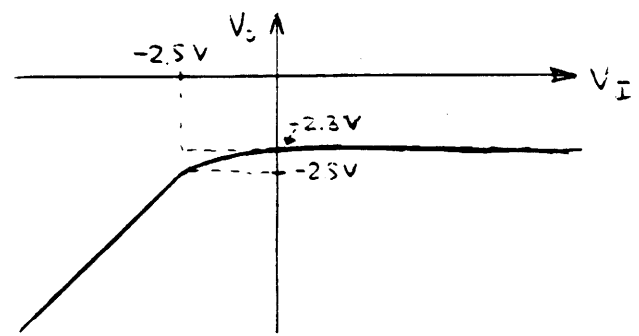
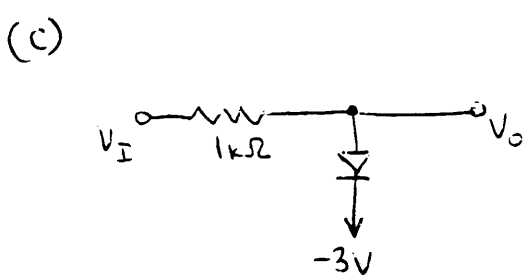
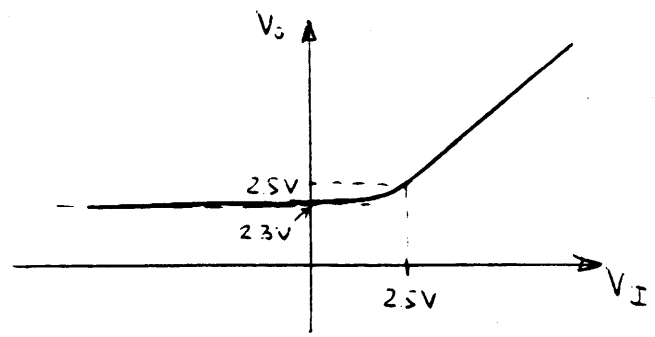
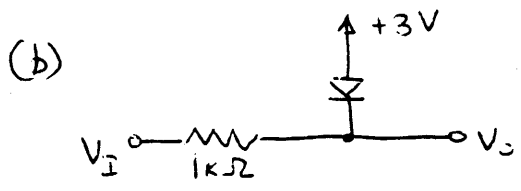
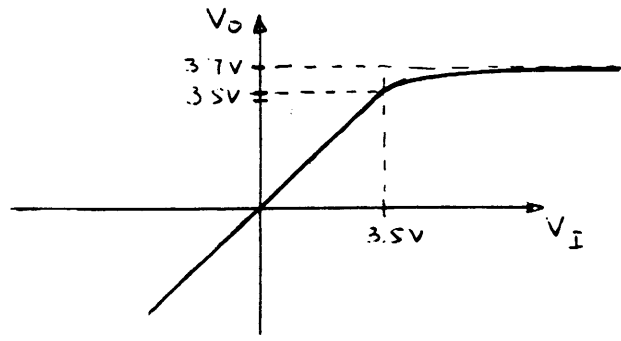



Assignment # 3

EE341



Problem 3.100

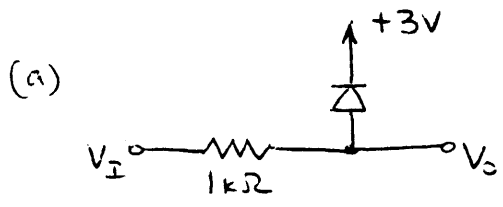

Problem 3.104

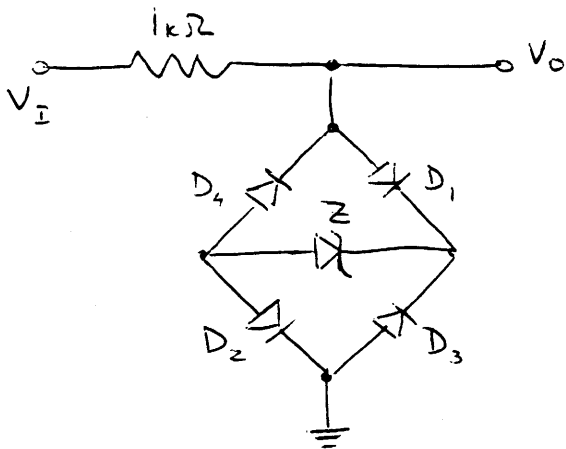

$$-20V \leq V_I \leq 20V$$

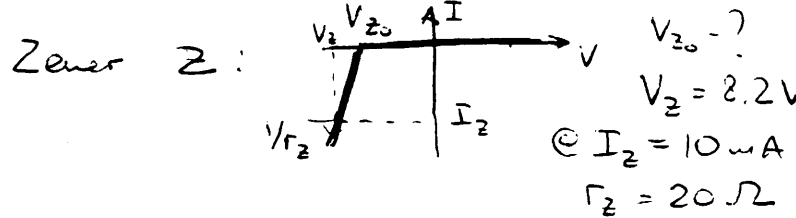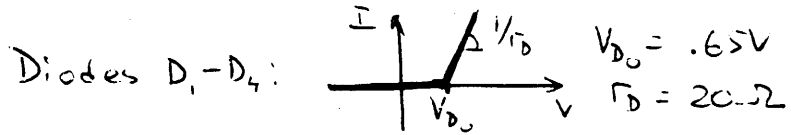

First, we have to find out how this circuit operates.


Suppose, V_I is a sinusoidal signal with average 0.

If voltage is positive and higher than $V_{D0} = .65V$, but not high enough (let's take $1V$), then D_1 is conducting, D_4 is cut off.

But D_3 is off and Zener is off, too. The Bridge is not conducting, and $V_O = V_I$. The same is true for negative V_I . So, we need to find a threshold voltage, at which the bridge starts conducting.

1 step Find $V_{Z0} = V_Z - I_Z r_Z = 8.2V - 10mA \cdot 20\Omega = \underline{\underline{8V}}$

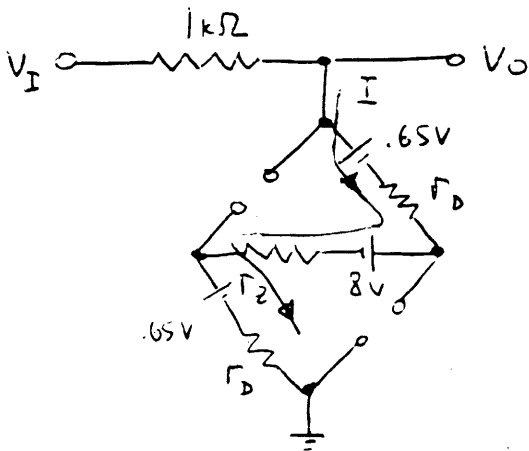2 step Draw the equivalence circuit when the Bridge is conducting at positive half-period of V_I .



The bridge starts conducting

when $V_I \geq V_{D0} + V_{Z0} + V_{D0} =$


$$= .65V + 8V + .65V = 9.3V$$

3 step When bridge is conducting, it acts as a voltage divider $V_I = V_o + V_{1k\Omega}$, and

$$m = \frac{V_o}{V_I} = \frac{V_o}{V_o + V_{1k\Omega}} = \frac{2r_D + r_z}{2r_D + r_z + 1k\Omega} = \frac{60\Omega}{60\Omega + 1000\Omega} = \underline{\underline{0.0566}}$$

@ $V_I = 20V$ $V_o = 9.3V + (20V - 9.3V) \cdot m = \underline{\underline{9.906V}}$

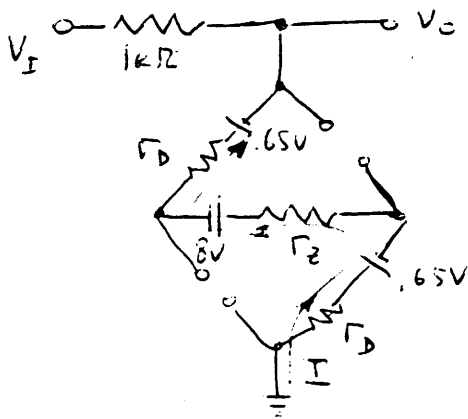When the bridge is conducting at negative half-period of V_I , the equivalent circuit is:




The bridge starts conducting when

$$V_I \leq -9.3V$$


m also equal to 0.0566

$$V_o(-20V) = -9.906V$$

4 step Transfer characteristic

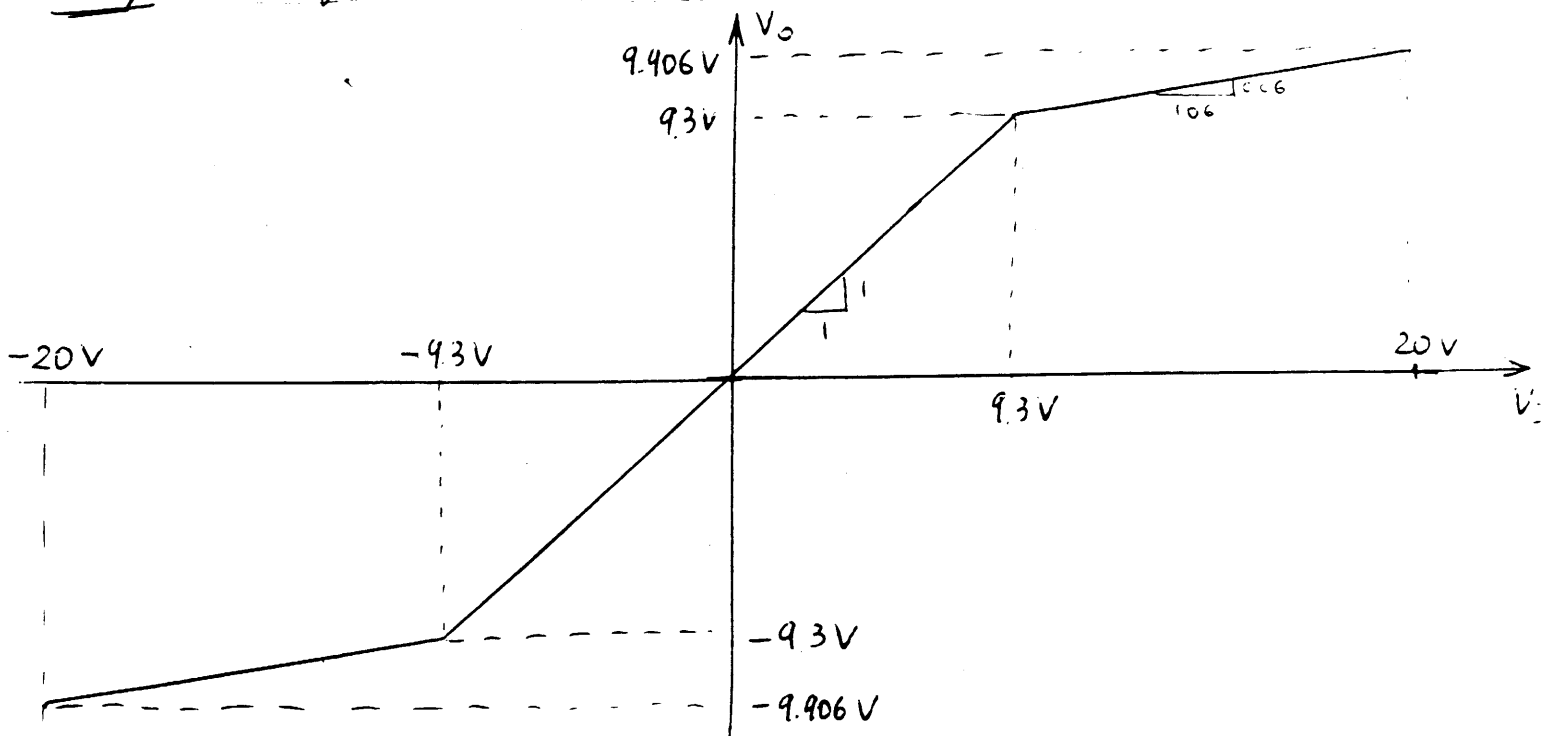

3.67

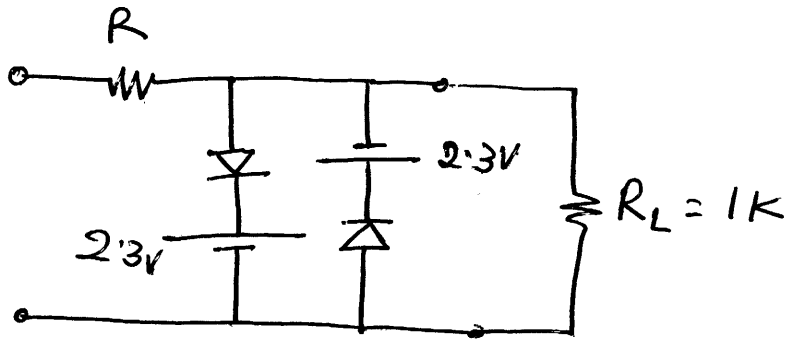

2.3V power supplies are used to provide $\pm 3V$ limiting levels



In the nonlimiting region,

$$\frac{R_L}{R + R_L} = 0.95 = \frac{1}{R + 1k}$$

$$\Rightarrow R = 0.0526 k = 52.6 \Omega$$

3.111

(a)

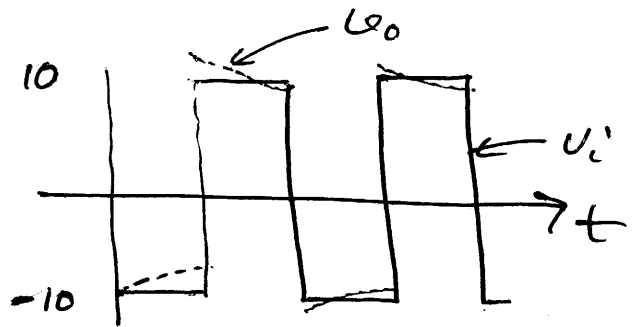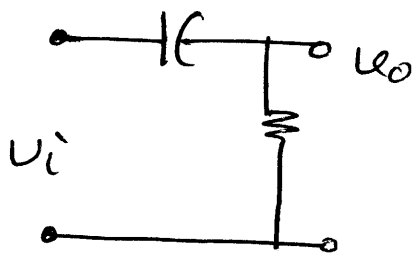

(b)

