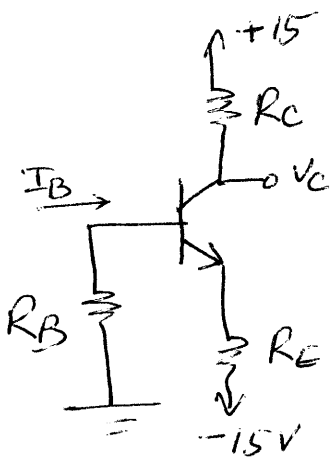


Assignment #6

EE 341

(1)

4.37



when $\beta = 100$ $I_E = 1 \text{ mA}$ & $V_C = 5 \text{ V}$

$$\alpha = \frac{\beta}{1 + \beta} = 0.99$$

$$\therefore I_C = \alpha I_E = 0.99 \text{ mA}$$

$$\therefore R_C = \frac{15 - 5}{0.99} = 10.1 \text{ k}\Omega$$

$$\text{KVL: } I_B R_B + 0.7 + I_E R_E = 15$$

$$\text{or } \frac{I_E}{1 + \beta} R_B + R_E I_E = 14.3$$

$$\therefore I_E = \frac{14.3}{R_E + \frac{R_B}{1 + \beta}}$$

So if β goes up, I_E increases.

$$1.1 = \frac{14.3}{R_E + \frac{R_B}{151}}$$

$$0.9 = \frac{14.3}{R_E + \frac{R_B}{51}}$$

After Solving for R_B & R_E

(1) $R_B = 221.7 \text{ k}\Omega$

(2) $R_E = 11.53 \text{ k}\Omega$

4.47

$$g_m = 80 \text{ mA/V} = \frac{I_C}{V_T} = \frac{I_C}{0.025}$$

\therefore Nominal value of $I_C = 2 \text{ mA}$

Now we know $g_m r_{\pi} = \beta$

$$r_{\pi} = \frac{\beta}{g_m}$$

Now if $I_C = 1.25 \times 2 \text{ mA} = 2.5 \text{ mA}$

$$g_m = \frac{2.5}{0.025} = 100 \text{ mA/V}$$

if $I_C = 0.75 \times 2 \text{ mA} = 1.5 \text{ mA}$

$$g_m = \frac{1.5}{0.025} = 60 \text{ mA/V}$$

$$r_{\pi}(\text{max}) = \frac{200}{60 \text{ mA/V}} = 3.34 \text{ k}\Omega$$

$$r_{\pi}(\text{min}) = \frac{50}{100 \text{ mA/V}} = 0.5 \text{ k}\Omega$$

4.48

DC analysis:


$$V_c = 2V \quad V_{cc} = 10V$$

$$I_c = \frac{V_{cc} - V_c}{R_c} = 4mA$$


$$g_m = \frac{4mA}{0.025V} = 160mA/V$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{160mA/V} = 0.625k\Omega$$

$$I_B = \frac{4mA}{100} = 40\mu A$$

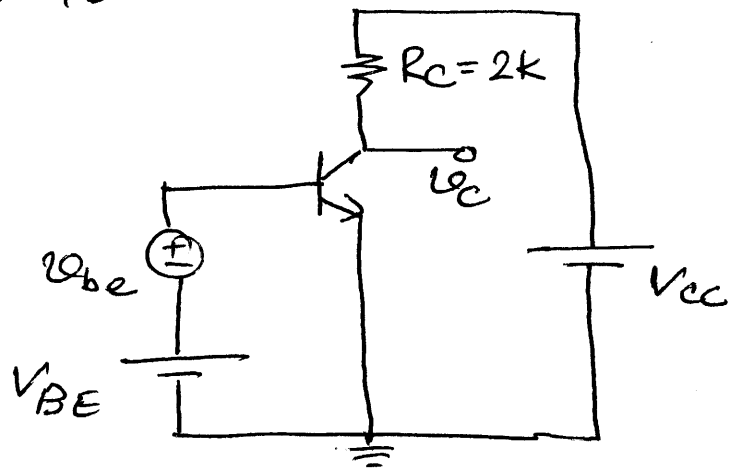

Small signal equivalent ckt

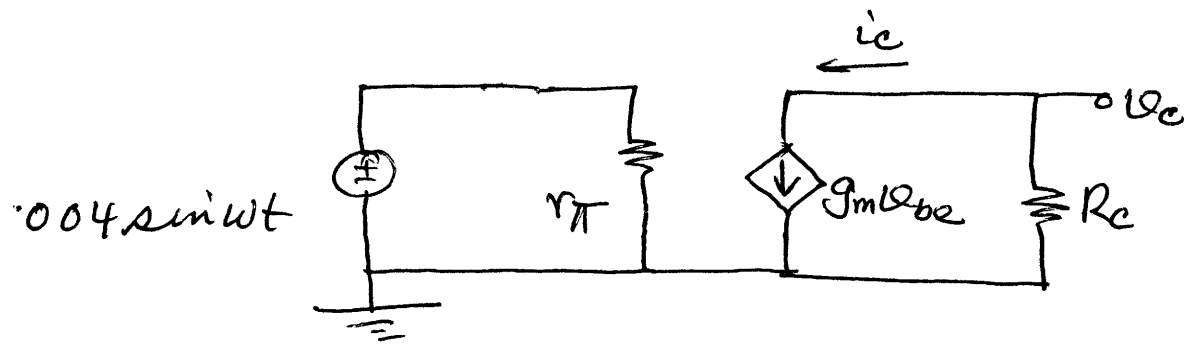

$$v_c = -i_c R_c = -g_m v_{be} R_c$$

$$= -160 \frac{mA}{V} \cdot 2k\Omega \cdot 0.004 \sin \omega t$$

$$= -1.28 \sin \omega t$$

$$i_c(t) = g_m v_{be} = 160 \frac{mA}{V} \cdot 0.004 \sin \omega t$$

$$= 0.64 \sin \omega t \text{ mA}$$

$$i_B(t) = \frac{i_c(t)}{\beta} = 0.0064 \sin \omega t \text{ mA} = 6.4 \sin \omega t \mu A$$

$$v_c(t) = 2 - 1.28 \sin \omega t \text{ V}$$


$$i_c(t) = 4 + 0.64 \sin \omega t \text{ mA}$$

$$i_B(t) = 40 + 6.4 \sin \omega t \mu A$$

$$A_v = -g_m R_c$$

$$= -320 \text{ V/V}$$

4.61

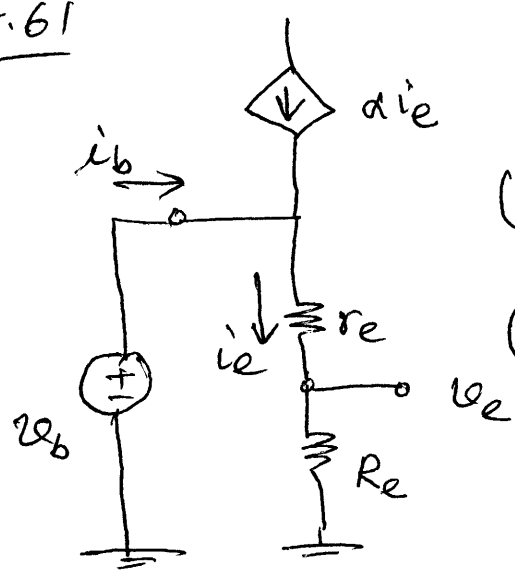

By voltage divider rule

(a) $v_e = v_b \frac{R_e}{r_e + R_e}$, $\frac{v_e}{v_b} = \frac{1k}{1.025k} = .976$

(b) $R_{in} \equiv \frac{v_b}{i_b} \dots (1)$

But $i_b = \frac{i_e}{(\beta+1)} \dots (A)$


$\& v_b = i_e (r_e + R_e)$

$r_e = \frac{1025}{1mA} = 1.025k\Omega$ $\therefore i_e = \frac{v_b}{r_e + R_e} \dots (B)$

Using (A) & (B) in Equation (1)


$R_{in} = (1+\beta)(r_e + R_e) = (101)(1.025k) = 102.5k$

4.64

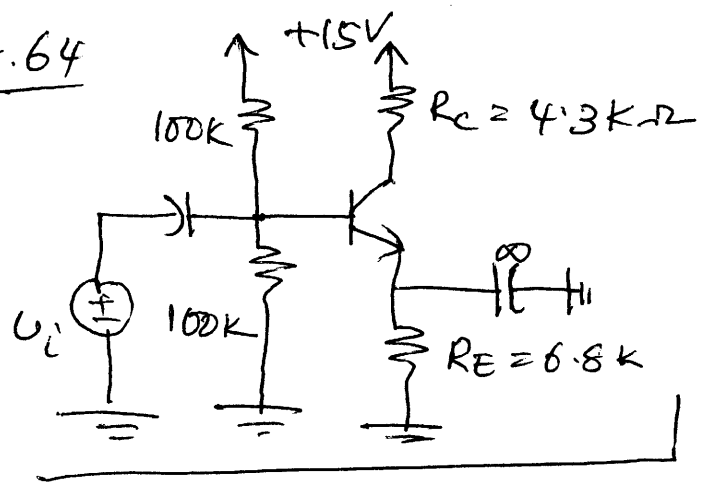

DC analysis

Thevenize the Base bias ckt

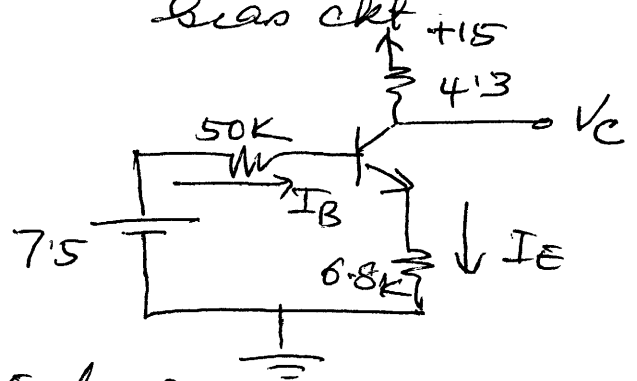

KVL around the B-E loop.


$7.5 = 50 I_B + 0.7 + 6.8 I_E$ [$I_B = \frac{I_E}{1+\beta} \rightarrow 0$]
 $= 0.7 + 6.8 I_E$ [$\beta \rightarrow \infty$]

$\therefore I_E = \frac{6.8}{6.8} = 1mA$

$I_C = \alpha I_E = 1mA$
 Since $\alpha \rightarrow 1$

$$r_e = \frac{V_T}{I_E} = \frac{0.025V}{1mA} = 25\Omega \text{ or } 0.025K\Omega$$

Small signal analysis

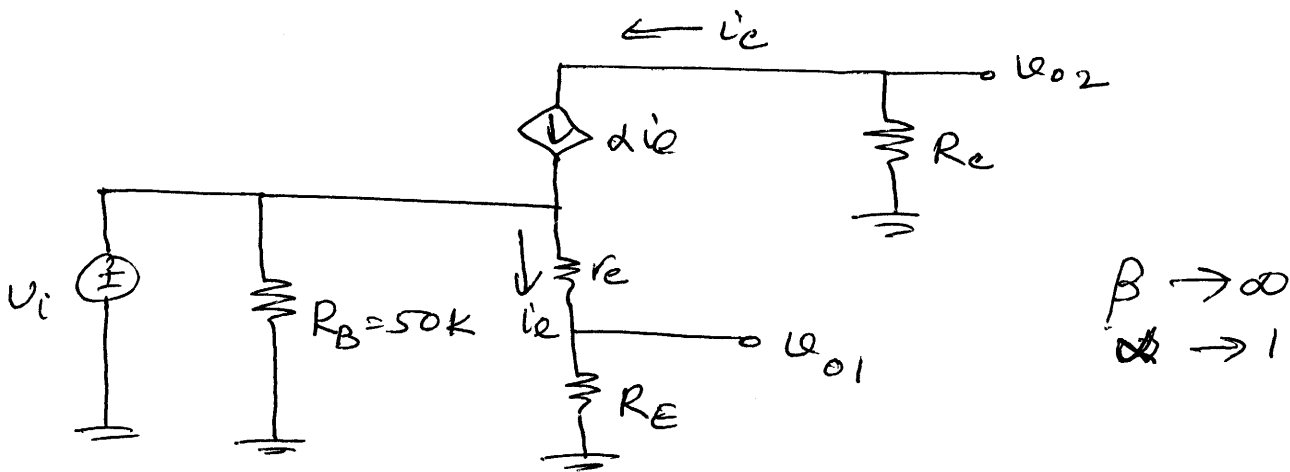

$$i_e = \frac{v_i}{r_e + R_E} \quad \therefore v_{o1} = i_e R_E = \frac{v_i R_E}{R_E + r_e}$$

$$\therefore \frac{v_{o1}}{v_i} = \frac{R_E}{R_E + r_e} = \frac{6.8}{6.8 + 0.025} = 0.996 \frac{V}{V}$$

$$v_{o2} = -i_c R_c = -\alpha i_e R_c = -\frac{\alpha R_c v_i}{R_E + r_e}$$

$$\therefore \frac{v_{o2}}{v_i} = \frac{-\alpha R_c}{R_E + r_e} = \frac{-4.3}{6.8 + 0.025} = -0.63 \frac{V}{V}$$