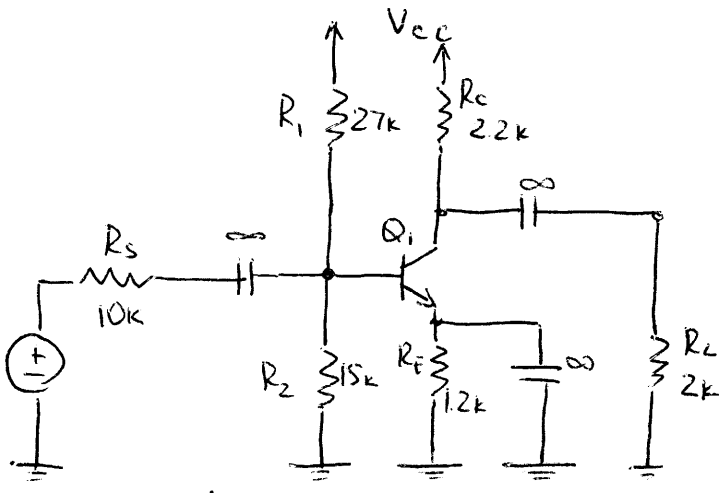


Assignment # 7

Problem 4.78



$\beta = 100$
 $V_A = 100 \text{ V}$
 $V_{CC} = 9 \text{ V}$

First, calculate the bias emitter current I_E

Writing KVL for base-emitter: $V_{BB} - 0 = 0.7 \text{ V} + I_E R_E + I_B R_{BB}$


where V_{BB} and R_{BB} are found from: $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2} = 9 \text{ V} \frac{15 \text{ k}}{27 \text{ k} + 15 \text{ k}} \approx 3.21 \text{ V}$

$R_{BB} = \frac{R_1 R_2}{R_1 + R_2} = \frac{15 \text{ k} \cdot 27 \text{ k}}{15 \text{ k} + 27 \text{ k}} = 9.64 \text{ k}\Omega$

$$I_E = \frac{V_{BB} - 0.7 \text{ V}}{R_E + \frac{R_{BB}}{\beta + 1}} = \frac{V_{CC} \frac{R_2}{R_1 + R_2} - 0.7 \text{ V}}{R_E + \frac{R_1 R_2}{(\beta + 1)(R_1 + R_2)}} = \frac{3.21 \text{ V} - 0.7 \text{ V}}{1.2 \text{ k}\Omega + \frac{9.64 \text{ k}\Omega}{101}} \approx 1.94 \text{ mA}$$

$I_C = \alpha I_E \approx 1.92 \text{ mA}$

Equivalent circuit:

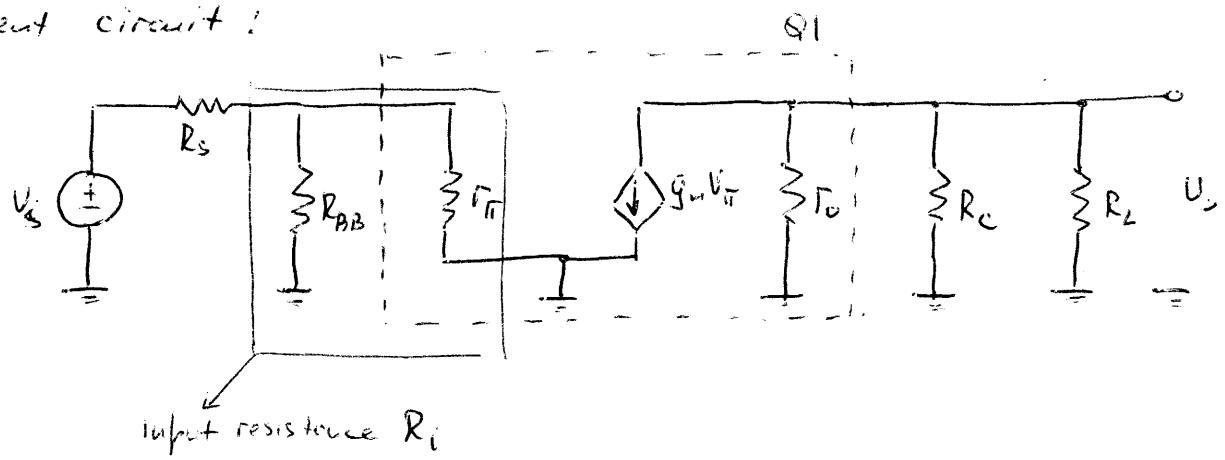

Now, we are able to find small signal characteristics:

Transconductance g_m ; r_π ; r_o :

$$g_m = \frac{I_C}{V_T} = \frac{1.92 \text{ mA}}{25 \text{ mV}} = .0768 \text{ A/V} = 76.8 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{76.8 \text{ mA/V}} = 1.3 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100 \text{ V}}{1.92 \text{ mA}} = 52.08 \text{ k}\Omega$$

Input resistance $R_i = R_{BB} \parallel r_\pi$ (see equivalent circuit)

$$R_i = \frac{R_{BB} r_\pi}{R_{BB} + r_\pi} = \frac{9.64 \text{ k}\Omega \cdot 1.3 \text{ k}\Omega}{9.64 \text{ k}\Omega + 1.3 \text{ k}\Omega} = \underline{\underline{1.15 \text{ k}\Omega}}$$

The voltage gain $A_v = \frac{V_o}{V_s} = \frac{V_o}{V_\pi} \cdot \frac{V_\pi}{V_s}$

$$\frac{V_\pi}{V_s} = \frac{R_i}{R_i + R_s} \quad (\text{voltage divider}) \quad \frac{V_o}{V_\pi} = -g_m \cdot (r_o \parallel R_c \parallel R_L)$$


$$A_v = - \frac{g_m (R_i \cdot (r_o \parallel R_c \parallel R_L))}{R_i + R_s} \quad r_o \parallel R_c \parallel R_L = 1.027 \text{ k}\Omega$$

$$A_v = - \frac{76.8 \frac{\text{mA}}{\text{V}} \cdot 1.15 \text{ k}\Omega \cdot 1.027 \text{ k}\Omega}{1.15 \text{ k}\Omega + 10 \text{ k}\Omega} = \underline{\underline{-8.135 \text{ V/V}}}$$

$$\text{Current gain } A_i = \frac{i_o}{i_s} = \frac{V_o/R_L}{V_s/(R_s + R_i)} = \frac{V_o}{V_s} \cdot \frac{R_s + R_i}{R_L} = A_v \cdot \frac{R_s + R_i}{R_L} =$$

$$= -8.135 \text{ V/V} \cdot \frac{10 \text{ k}\Omega + 1.15 \text{ k}\Omega}{2 \text{ k}\Omega} = \underline{\underline{-45.35 \text{ A/A}}}$$

Problem 4.82

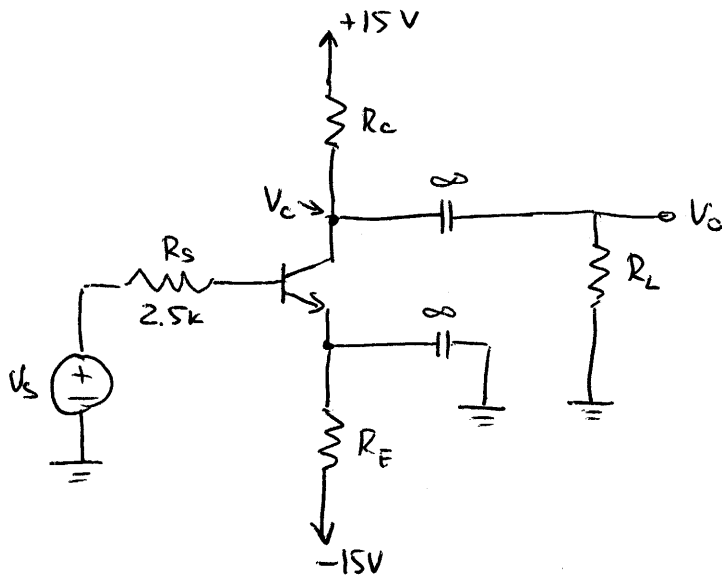

$$\beta = 100$$

(a) Find R_E to establish dc $I_E = 1\text{mA}$

Writing DC KVL base-emitter:

$$0 - (-15V) = I_E R_E + 0.7V + I_B R_s$$

$$R_E = \frac{15V - 0.7V}{I_E} - \frac{R_s}{\beta + 1} =$$


$$= \frac{14.3V}{1\text{mA}} - \frac{2.5k\Omega}{101} = \underline{\underline{14.28k\Omega}}$$

(b) Find R_C to establish dc collector voltage $+5V$

$$V_C = 15V - I_C R_C = 15V - \alpha I_E R_C \quad ; \quad R_C = \frac{15V - V_C}{\alpha I_E} = \frac{15V - 5V}{.99 \cdot 1\text{mA}} = \underline{\underline{10.1k\Omega}}$$

(c) For $R_L = 5k\Omega$ and $r_o = 100k\Omega$ draw equivalent circuit and find A_v

Equivalent circuit:

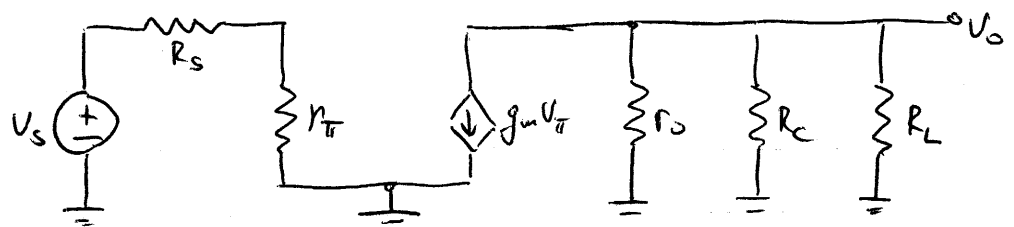

Small signal characteristics: $g_m = \frac{I_C}{V_T} = \frac{.99\text{mA}}{25\text{mV}} = 39.6 \text{ mA/V}$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{39.6 \text{ mA/V}} = 2.53k\Omega$$


$$r_o = 100k\Omega \text{ (given)}$$

Voltage gain $A_v = \frac{V_o}{V_s} = \frac{V_o}{V_{\pi}} \cdot \frac{V_{\pi}}{V_s} = \underbrace{-g_m (r_o \parallel R_C \parallel R_L)}_{\frac{V_o}{V_{\pi}}} \cdot \underbrace{\left(\frac{r_{\pi}}{R_s + r_{\pi}} \right)}_{\frac{V_{\pi}}{V_s} \text{ from voltage divider}}$

$$r_o \parallel R_C \parallel R_L = 100k\Omega \parallel 10.1k\Omega \parallel 5k\Omega = 3.24k\Omega \quad \frac{V_o}{V_{\pi}}$$

$$A_v = -39.6 \text{ mA/V} \cdot (3.24k\Omega) \cdot \frac{2.53k\Omega}{2.5k\Omega + 2.53k\Omega} = \underline{\underline{-64.53 \text{ V/V}}}$$

Problem 4.83

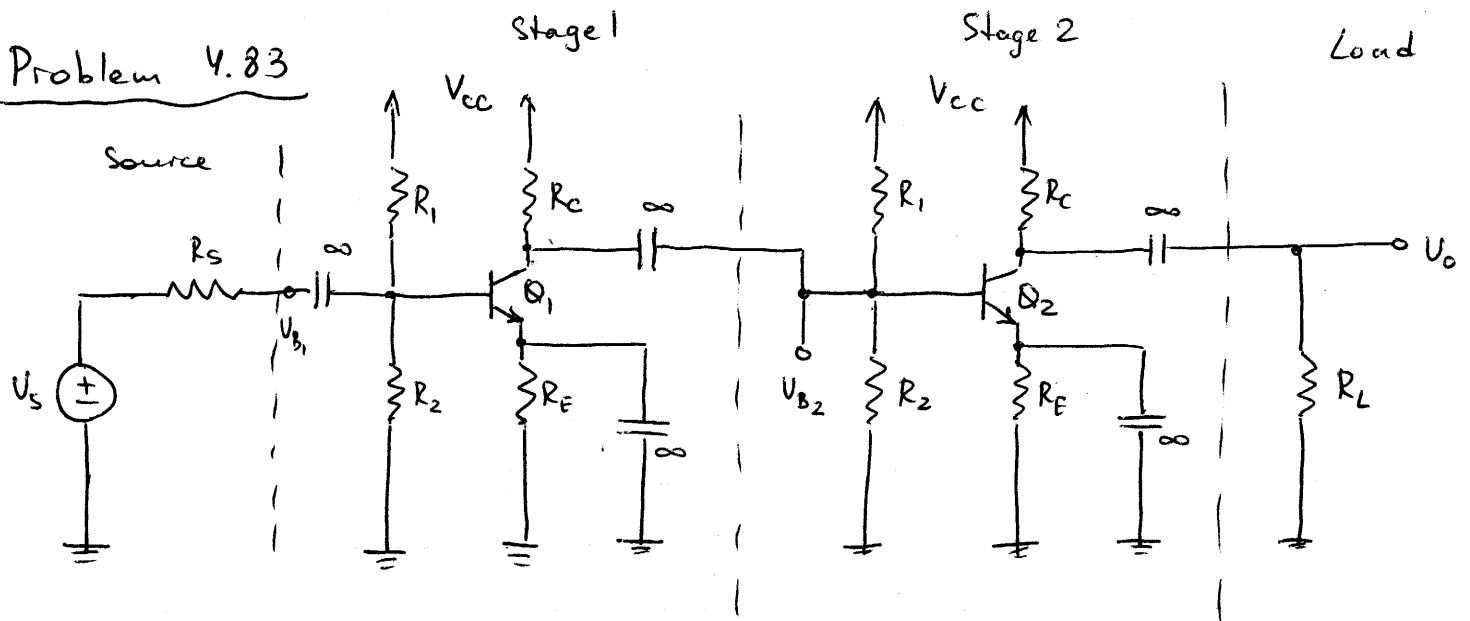

$V_{CC} = 15V$ $R_1 = 100k\Omega$ $R_2 = 47k\Omega$ $R_E = 3.9k\Omega$ $R_C = 6.8k\Omega$ $\beta = 100$
 $R_S = 5k\Omega$ $R_L = 2k\Omega$

(a) Determine DC collector current and collector voltage of each transistor.

DC for Q_1, Q_2 : $V_{BB} - 0V = I_B R_{BB} + 0.7V + I_E R_E$

V_{BB} and R_{BB} are found from: $V_{BB} = V_{CC} \cdot \frac{R_2}{R_1 + R_2} = 15V \cdot \frac{47k\Omega}{147k\Omega} = 4.8V$


$R_{BB} = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{100k\Omega \cdot 47k\Omega}{147k\Omega} \approx 32k\Omega$

$I_E = \frac{V_{BB} - 0.7V}{R_E + \frac{R_{BB}}{\beta + 1}} = \frac{4.8V - 0.7V}{3.9k\Omega + \frac{32k\Omega}{101}} = 0.97mA$

$I_C = \alpha I_E = .99 \cdot 0.97mA = .96mA$

$V_C = V_{CC} - I_C \cdot R_C = 15V - .96mA \cdot 6.8k\Omega = 8.47V$

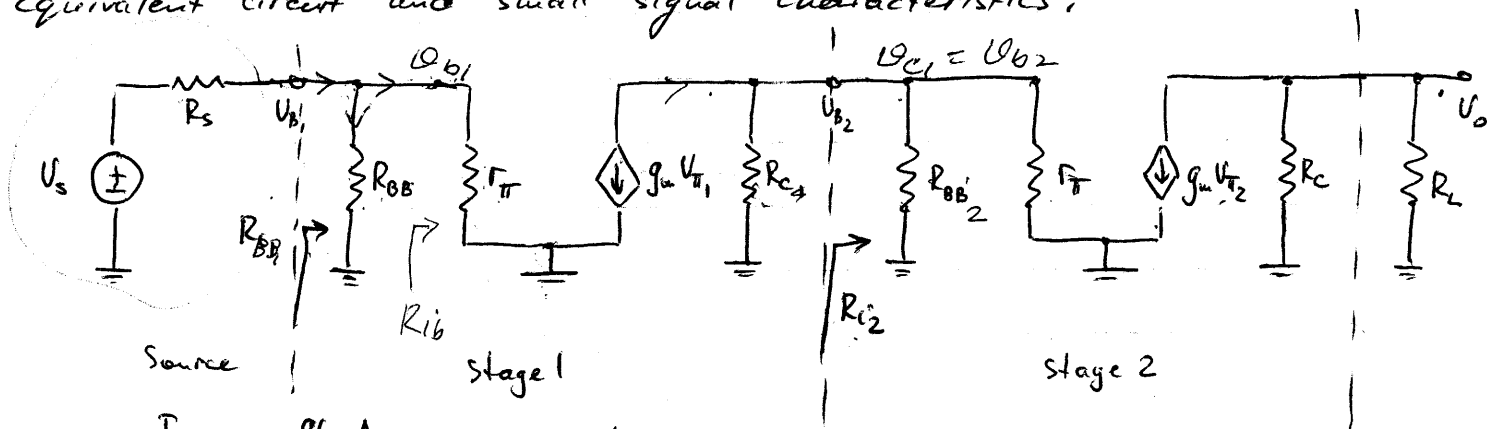(b) Equivalent circuit and small signal characteristics:



$g_m = \frac{I_C}{V_T} = \frac{.96mA}{25mV} = 38.4mA/V$

$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{38.4mA/V} = 2.6k\Omega$

$R_{i1} = R_{BB} \parallel r_{\pi} = \frac{32k\Omega \cdot 2.6k\Omega}{32k\Omega + 2.6k\Omega} = 2.4k\Omega$

$R_{i2} = R_{BB2} \parallel r_{\pi} = 2.4k\Omega$


$$\frac{\text{Input Voltage Stage 1}}{\text{Signal voltage}} = \frac{V_{B1}}{V_s} = \frac{R_{i1}}{R_s + R_{i1}} = \frac{2.4 \text{ k}\Omega}{5 \text{ k}\Omega + 2.4 \text{ k}\Omega} = 0.324 \text{ V/V}$$

$$\begin{aligned} \frac{\text{Output Stage 1}}{\text{Input Stage 1}} &= \frac{V_{B2}}{V_{B1}} = -g_m \cdot (R_c \parallel R_{BB} \parallel r_{\pi}) = -g_m (R_c \parallel R_i) = \\ &= -38.4 \text{ mA/V} \cdot \frac{6.8 \text{ k}\Omega \cdot 2.4 \text{ k}\Omega}{6.8 \text{ k}\Omega + 2.4 \text{ k}\Omega} = -68.12 \text{ V/V} \end{aligned}$$

$$\frac{\text{Output Load}}{\text{Input stage 2}} = \frac{V_o}{V_{B2}} = -g_m (R_c \parallel R_L) = -38.4 \text{ mA/V} \cdot \frac{6.8 \text{ k}\Omega \cdot 2 \text{ k}\Omega}{6.8 \text{ k}\Omega + 2 \text{ k}\Omega} = -59.35 \text{ V/V}$$

$$\frac{\text{Output load}}{\text{Input signal}} = \frac{V_o}{V_s} = \frac{V_o}{V_{B2}} \cdot \frac{V_{B2}}{V_{B1}} \cdot \frac{V_{B1}}{V_s} = -59.35 \text{ V/V} \cdot (-68.12 \text{ V/V}) \cdot 0.324 \text{ V/V} \approx \underline{\underline{1309 \text{ V/V}}}$$

Problem 4.84

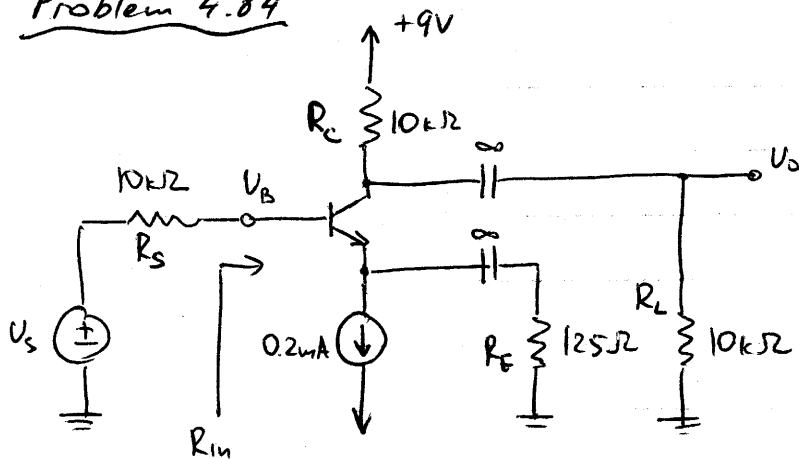

V_s - small sine-wave signal with 0 average.

$$\beta = 50$$

$$R_{in} = (\beta + 1)(r_e + R_E)$$

$$r_e = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{0.2 \text{ mA}} = 125 \Omega$$

given by current source

$$R_{in} = (50 + 1) \cdot (125 \Omega + 125 \Omega) = \underline{\underline{12.75 \text{ k}\Omega}}$$

$$\frac{V_B}{V_s} = \frac{R_{in}}{R_{in} + R_s} = \frac{12.75 \text{ k}\Omega}{12.75 \text{ k}\Omega + 10 \text{ k}\Omega} = \underline{\underline{0.56 \text{ V/V}}}$$

$$\frac{\text{Output}}{\text{Input}} = \frac{V_o}{V_B} = \frac{-\alpha \cdot (R_c \parallel R_L)}{r_e + R_E} = \frac{-0.98 \cdot 5 \text{ k}\Omega}{250 \Omega} = \underline{\underline{-19.6 \text{ V/V}}}$$


$$\frac{V_o}{V_s} = \frac{V_o}{V_B} \cdot \frac{V_B}{V_s} = -19.6 \text{ V/V} \cdot 0.56 \text{ V/V} = \underline{\underline{-10.98 \text{ V/V}}}$$

If $V_{BE} = 5 \text{ mV}$ (it drops on r_e), then $V_{RE} = 5 \text{ mV}$ (since $R_E = r_e = 125 \Omega$)

$$V_B = V_{BE} + V_E = 10 \text{ mV}, \quad V_s = \frac{V_B}{(V_B/V_s)} = \frac{10 \text{ mV}}{0.56 \text{ V/V}} = \underline{\underline{17.9 \text{ mV}}}$$

$$V_o = \underline{\underline{17.9 \text{ mV}}} \cdot \left(\frac{V_o}{V_s}\right) = 17.9 \text{ mV} \cdot (-10.98 \text{ V/V}) = \underline{\underline{-196.5 \text{ mV}}}$$

Problem 4.85

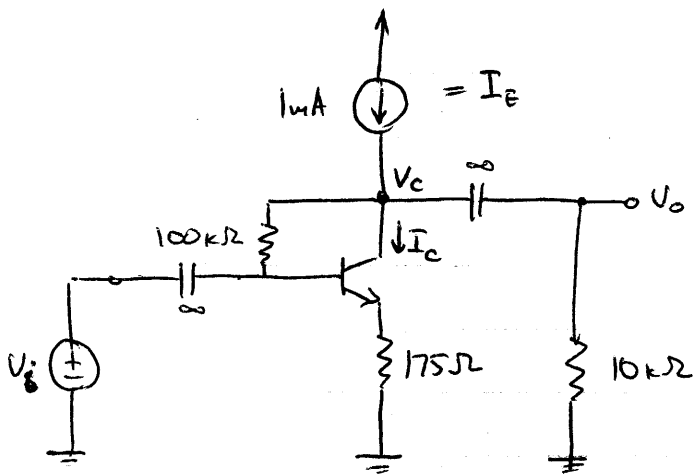

$\beta = 100$


a) dc collector current

$$I_c = \frac{\beta}{\beta + 1} \cdot 1\text{mA} = .99\text{mA}$$

dc collector voltage

$$V_c = I_B \cdot 100\text{k}\Omega + 0.7\text{V} + I_E \cdot 175\Omega = 0.7\text{V} + I_E \left(175\Omega + \frac{100\text{k}\Omega}{101} \right) = \underline{\underline{1.87\text{V}}}$$

b) T-model:

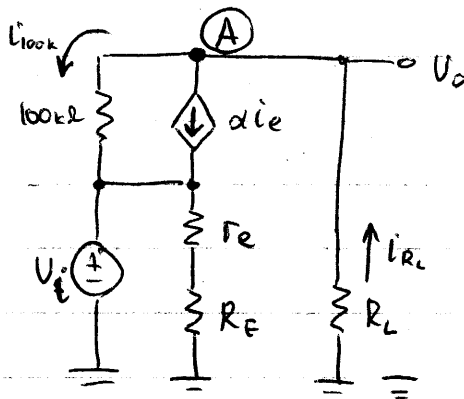

From the figure,

$$V_i = i_e \cdot (R_E + r_e)$$

$$r_e = \frac{V_T}{I_E} = \frac{25\text{mV}}{1\text{mA}} = 25\Omega$$

Writing node equation for (A)


$$i_{R_L} + \alpha i_e + i_{100k} = 0$$

$$\text{or } \frac{V_o}{R_L} + \alpha i_e + \frac{V_o - V_i}{100\text{k}\Omega} = 0 \quad ; \quad \frac{V_o}{R_L} + \alpha \cdot \frac{V_i}{R_E + r_e} + \frac{V_o - V_i}{100\text{k}\Omega} = 0$$

$$V_o \left(\frac{1}{R_L} + \frac{1}{100\text{k}\Omega} \right) = V_i \left(\frac{1}{100\text{k}\Omega} - \frac{\alpha}{R_E + r_e} \right)$$

$$\frac{V_o}{V_i} = \frac{\left(\frac{1}{100\text{k}\Omega} - \frac{\alpha}{R_E + r_e} \right)}{\left(\frac{1}{R_L} + \frac{1}{100\text{k}\Omega} \right)} = \frac{\left(\frac{1}{100\text{k}\Omega} - \frac{0.99}{175\Omega + 25\Omega} \right)}{\left(\frac{1}{10\text{k}\Omega} + \frac{1}{100\text{k}\Omega} \right)} = \frac{-4.94}{0.11} = \underline{\underline{-44.9\text{ V/V}}}$$

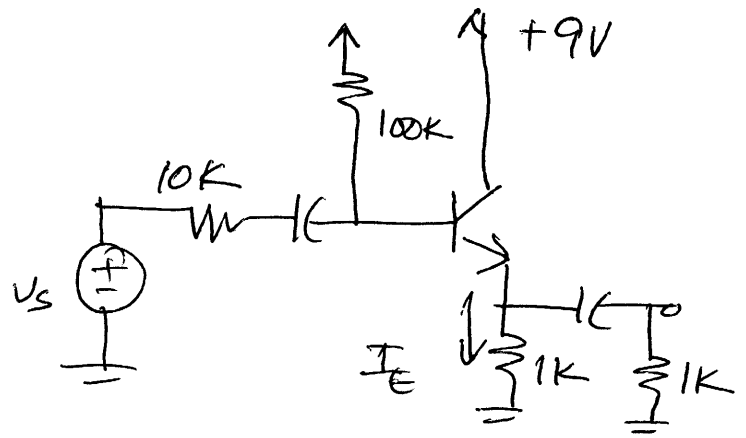4.91 $I_E = \frac{9 - 0.7}{1K + \frac{100K}{\beta + 1}}$



if $\beta = 20$:


$I_E = \frac{8.3}{1 + \frac{100}{21}} = 1.44 \text{ mA}$ $V_E = 1.44 \text{ mA} \times 1K = 1.44 \text{ V}$

$V_B = V_E + 0.7 = 2.14 \text{ V}$
Active

if $\beta = 200$

$I_E = 5.54 \text{ mA}$, $V_E = 5.54 \text{ V}$, $V_B = 6.24 \text{ V}$
Active

Small signal equivalent ckt

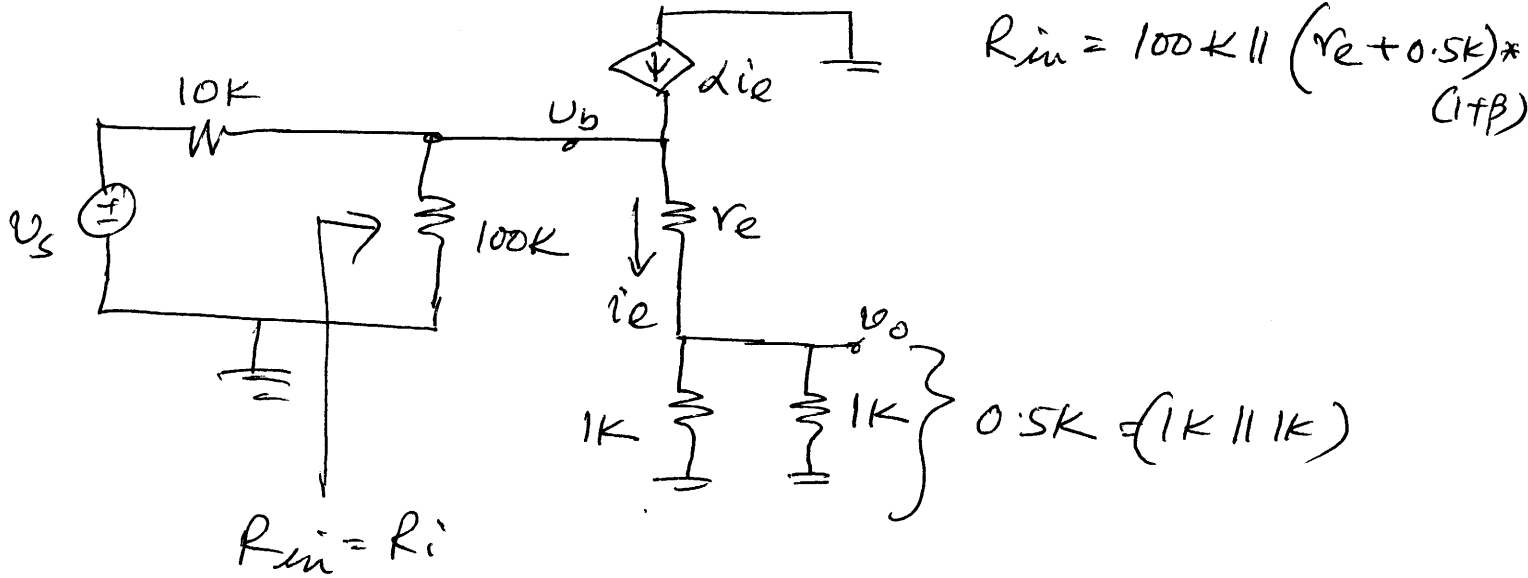

if $\beta = 20$ $r_e = 17.4 \Omega$ $R_{in} = 9.8K \Omega$

if $\beta = 200$ $r_e = 4.51 \Omega$ $R_{in} = 50.3K \Omega$

$\frac{V_o}{V_s} = \frac{V_o}{V_b} \cdot \frac{V_b}{V_s} = \frac{(1K \parallel 1K)}{r_e + (1K \parallel 1K)} \cdot \frac{R_{in}}{R_{in} + 10K}$

$\left[\begin{array}{l} \beta = 20; \frac{V_o}{V_s} = 0.478 \frac{V}{V} \\ \beta = 200; \frac{V_o}{V_s} = 0.827 \frac{V}{V} \end{array} \right.$