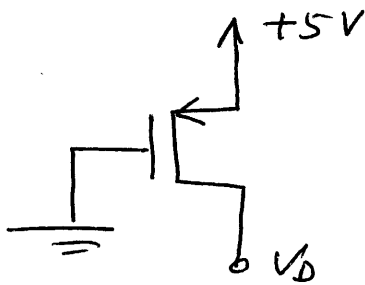


# Home work #9

Ex 5.8



$$V_{GS} = -5$$

$$k_p' \frac{W}{L} = 100 \frac{\mu A}{V^2} = \beta_p$$

$$V_t = -2V$$

"Saturation edge" is when

$$V_{DS} = V_{GS} - V_t$$

$$V_D - 5 = (0 - 5) - V_t$$

$$V_D = +2V$$

when  $V_D = -5V$


$$V_{DS} = -5 - 5 = -10V < V_{GS} - V_t$$

Transistor in saturation

$$I_D = \frac{1}{2} \beta_p (V_{GS} - V_t)^2 = \frac{1}{2} \times 100 \frac{\mu A}{V^2} (-5 - (-2))^2$$

$$= 50 \mu A \times 9 = 450 \mu A = 0.45 \text{ mA}$$

D5.35

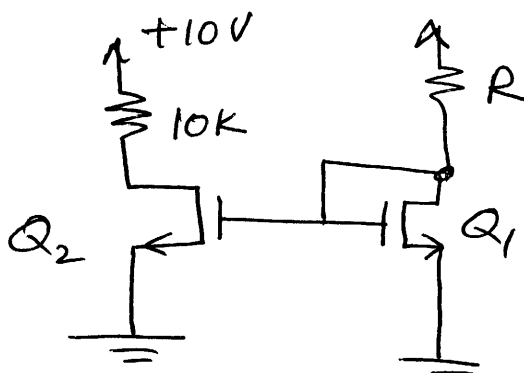

$$V_t = 2V \quad \mu_n C_{ox} = 20 \frac{\mu A}{V^2}$$

$$L_1 = L_2 = 10 \mu \quad W = 100 \mu A$$

$Q_1$  is in saturation since  $V_{G1} = V_D$

$$(a) \quad 0.1 \text{ mA} = 100 \mu A = \frac{1}{2} (\mu_n C_{ox}) \frac{W_1}{L_1} (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 20 \cdot \left(\frac{100}{10}\right) (V_{GS} - 2)^2$$

$$(V_{GS} - 2)^2 = 1 \Rightarrow V_{GS} = 3 \text{ or } (+1) < V_t \text{ not possible}$$


$$\therefore V_{GS} = 3V$$

$$\therefore R = \frac{10 - 3}{0.1} = 70 \text{ k}\Omega$$

$$(b) \quad 0.5 = \frac{1}{2} (20) \times 10^{-3} \frac{W_2}{10} (3-2)^2$$

$$W = \frac{2 \times 5 \times 10 \times 10^3}{20 \times 1} = 500 \mu\text{m}$$

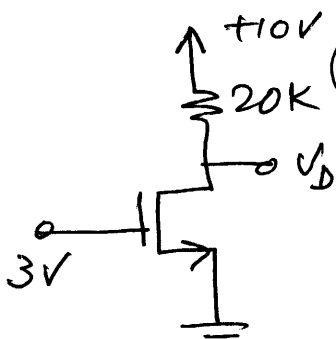D 5-42      $\beta_n = k_n' \frac{W}{L} = 200 \frac{\mu\text{A}}{\text{V}^2}$       $V_E = 2\text{V}$       $V_A = 20\text{V}$



(a) Assume Saturation

$$V_D = 10 - 20 I_D \quad \text{or} \quad I_D = \frac{10 - V_D}{20\text{K}}$$

$$\frac{10 - V_D}{20\text{K}} = \frac{1}{2} (200 \times 10^{-6}) (3 - 2)^2 \left(1 + \frac{V_D}{20}\right)$$

$$= 100 \times 10^{-6} \left(1 + \frac{V_D}{20}\right)$$

$$\Rightarrow V_D = 7.27 > V_G - V_E = 1 \quad (\text{Sat})$$

(b) Assume Saturation

$$\frac{20 - V_D}{20\text{K}} = 100 \times 10^{-6} \left(1 + 0.05 V_D\right) \Rightarrow V_D = 16.36 > V_G - V_E$$


(Sat)

(c) Assume Saturation

$$\frac{20 - V_D}{20\text{K}} = (100 \mu\text{A}) (4) \left(1 + 0.05 V_D\right) \Rightarrow V_D = 8.57 > V_G - V_E$$

(Sat)

5.55

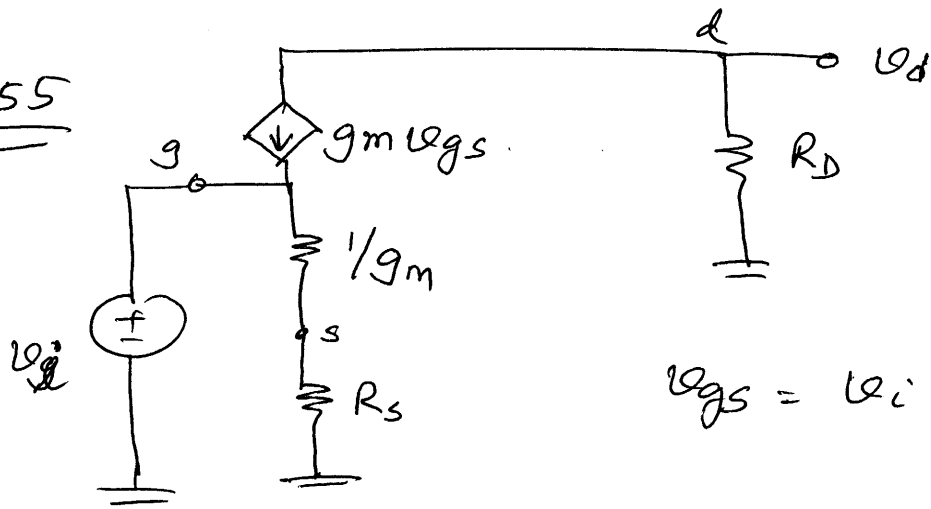

$$v_{gs} = v_i \frac{1/g_m}{1/g_m + R_s} = \frac{v_i}{1 + g_m R_s}$$


$$v_s = v_i \frac{R_s}{1/g_m + R_s} = v_i \frac{g_m R_s}{1 + g_m R_s}$$

$$\therefore \frac{v_s}{v_i} = \left[ \frac{g_m R_s}{1 + g_m R_s} \right]$$

$$v_d = -g_m v_{gs} R_D = -g_m \left( \frac{v_i}{1 + g_m R_s} \right) R_D$$

$$\therefore \frac{v_d}{v_i} = - \left( \frac{g_m R_D}{1 + g_m R_s} \right)$$

5.57

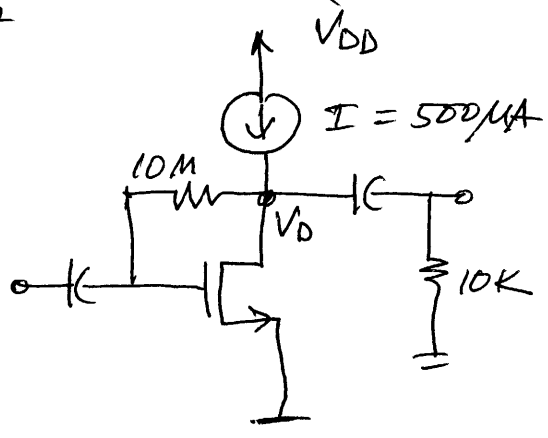


$|V_{t}| = 0.9V \quad V_A = 50V$

$V_D = 2V$

$$r_D = \frac{50V}{0.5mA} = 100K$$

$$g_m = \frac{2I_D}{V_{DS} - V_t} = \frac{2(0.5mA)}{2 - 0.9} = 0.91 \frac{mA}{V}$$

## Small signal equivalent ckt

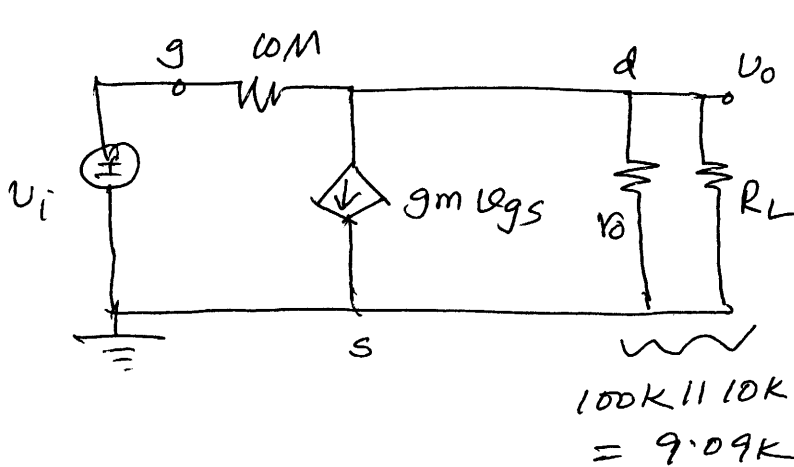

$$v_{gs} = v_i$$

$$v_o = -g_m v_i (r_o \parallel R_L)$$

$$\therefore \frac{v_o}{v_i} = -0.91 \frac{\text{mA}}{\text{V}} \cdot 9.09 \text{K}$$

$$= -8.27 \frac{\text{V}}{\text{V}}$$

This transistor is always in saturation

$$I_D = \frac{1}{2} \left( k_n' \frac{W}{L} \right) (V_{GS} - V_T)^2 \left( 1 + \frac{V_{DS}}{V_A} \right)$$

Note  
 $V_{GS} = V_{DS}$   
 $= V_D$

$$0.5 \text{mA} = \frac{1}{2} \left( k_n' \frac{W}{L} \right) (2 - 0.9)^2 \left( 1 + \frac{2}{50} \right)$$

$$\Rightarrow \frac{1}{2} \left( k_n' \frac{W}{L} \right) = 3.97 \times 10^{-4} \frac{\text{A}}{\text{V}^2}$$

Now when  $I$  is increases to  $1 \text{mA}$

$$10^{-3} = 3.97 \times 10^{-4} (V_D - 0.9)^2 \left( 1 + \frac{V_D}{50} \right) = 0$$

Assume  $\left( 1 + \frac{V_D}{50} \right) \approx 1$  (for the time being)

$$(V_D - 0.9)^2 = \frac{10}{3.97} = 2.51 \Rightarrow V_D = 2.48 \text{ or } 0.687$$

$\uparrow$   
 discard.

Second iteration

$$(V_D - 0.9)^2 = \frac{10}{3.97} \left( \frac{1}{1 + \frac{2.48}{50}} \right) \Rightarrow V_D = 2.446 \text{V}$$

$$\text{when } I_D = 1\text{mA} \quad g_m = \frac{2 \times 1\text{mA}}{2.45 - 0.9} = 1.29 \frac{\text{mA}}{\text{V}}$$

$$r_o = \frac{V_A}{I_D} = 50\text{K}$$

$$\therefore \frac{v_o}{v_i} = -g_m (r_o \parallel 10\text{K}) = -10.75 \frac{\text{V}}{\text{V}}$$