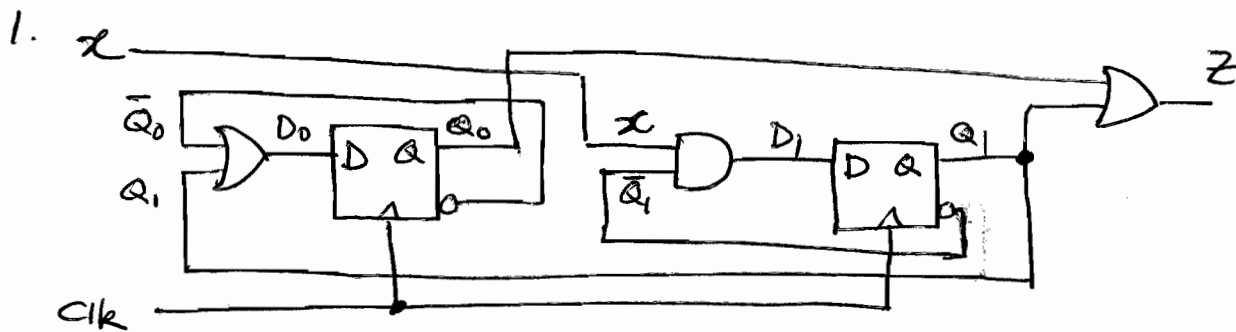


Solution to HW#4



$$\begin{aligned} D_0 &= Q_0^* = Q_1 + \bar{Q}_0 \\ D_1 &= Q_1^* = x \cdot \bar{Q}_1 \\ Z &= Q_0 + Q_1 \end{aligned} \quad \left. \begin{array}{l} \text{excitation Equation} \\ \text{output Equation} \end{array} \right\}$$

Excitation / Transition Table

Present Values Input state $x \quad Q_1 \quad Q_0$	Next values $Q_1^* \quad Q_0^*$	Present output Z
0 0 0	0 1	0
0 0 1	0 0	1
0 1 0	0 1	1
0 1 1	0 1	1
1 0 0	1 1	0
1 0 1	1 0	1
1 1 0	0 1	1
1 1 1	0 1	1

Let state $S = Q_1 Q_0$

A = 00

B = 01

C = 10



D = 11

Next state $\Rightarrow S^*$

State Output Table

x	S	S^*	Z
0	A	B	0
0	B	A	1
0	C	B	1
0	D	B	1
1	A	D	0
1	B	C	1
1	C	B	1
1	D	B	1

State Diagram (always useful to draw)

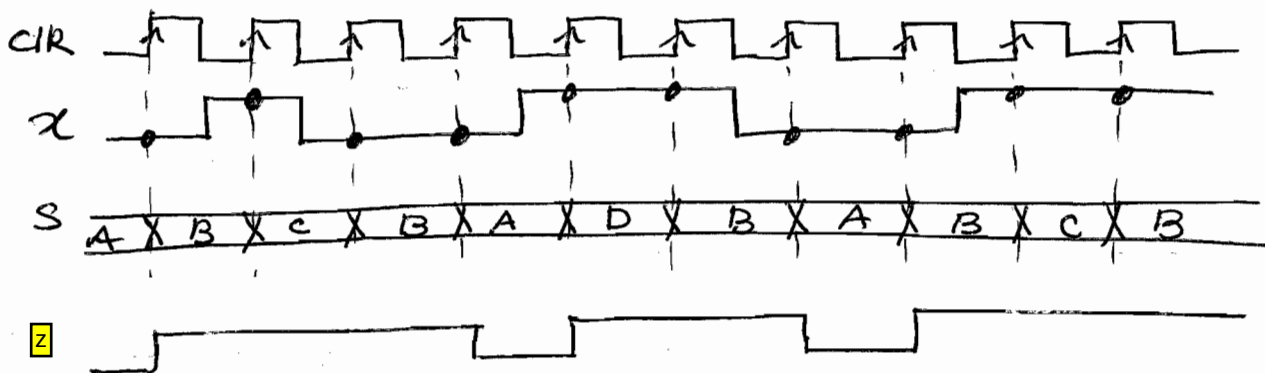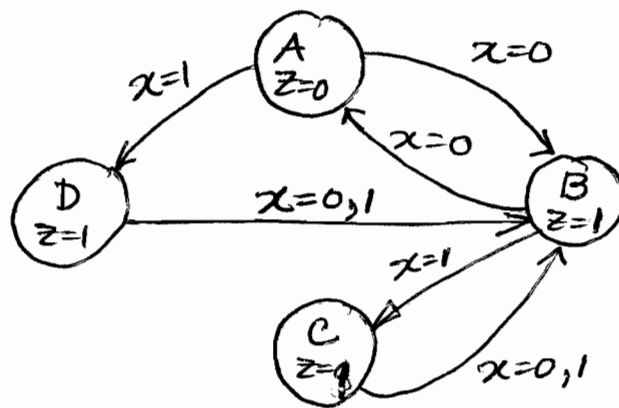

2. Swap AND + OR gates in Prob 1.

$$D_0 = Q_0^* = Q_1 \cdot \bar{Q}_0$$

$$D_1 = Q_1^* = x + \bar{Q}_1$$

$$z = Q_0 \cdot Q_1$$

Excitation Transition Table

x	Q ₁	Q ₀	Q ₁ [*]	Q ₀ [*]	z
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	1	0	1



State/output Table

x	s	s [*]	z
0	A	C	0
0	B	C	0
0	C	B	0
0	D	A	1
1	A	C	0
1	B	C	0
1	C	D	0
1	D	C	1

$$A = Q_1 Q_0 = 00 \quad C = 10$$

$$B = 01 \quad D = 11$$

State Diagram

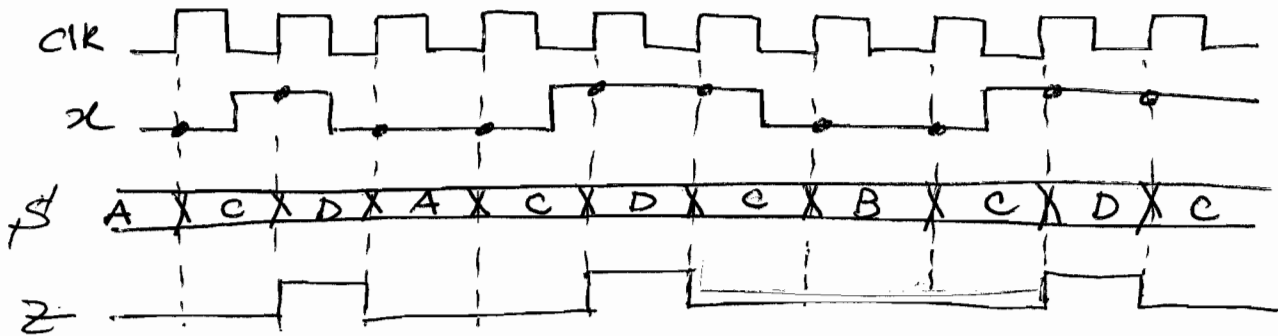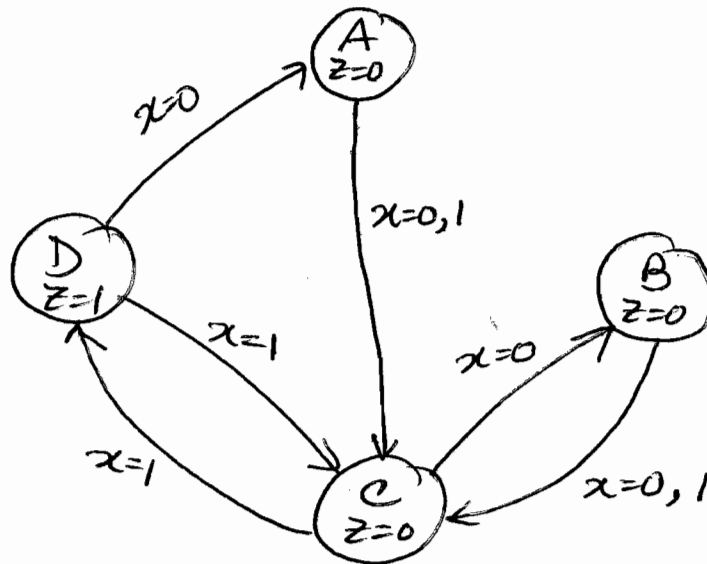


5. Design a counter with an active-low enable $\overline{En-L}$ & the follow sequence

$0 \rightarrow 4 \rightarrow 5 \rightarrow 7 \rightarrow 2$

Solution

Highest number is 7. $\log_2 7 > 2$.
Use 3 Flipflops.

Counter state	Number
$Q_2 Q_1 Q_0$	
0 0 0	0
1 0 0	4
1 0 1	5
1 1 1	7
0 1 0	2

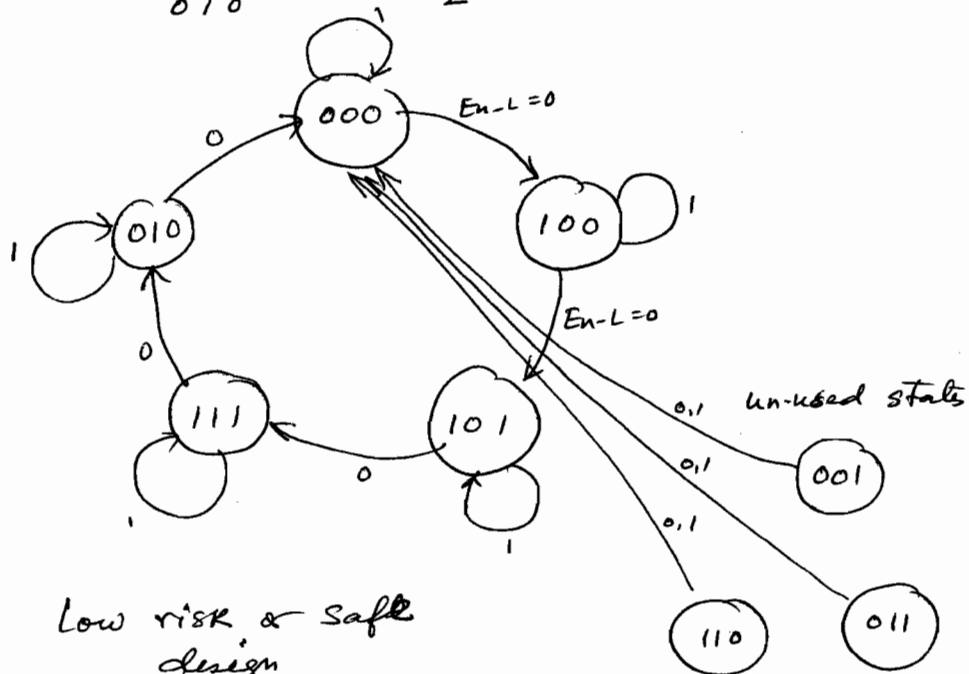

Excitation Transition Table

$E_{n-L} Q_2 Q_1 Q_0$	$Q_2^* Q_1^* Q_0^*$
0 0 0 0	1 0 0
0 0 0 1	0 0 0
0 0 1 0	0 0 0
0 0 1 1	0 0 0
0 1 0 0	1 0 1
0 1 0 1	1 1 1
0 1 1 0	0 0 0
0 1 1 1	0 1 0
1 0 0 0	0 0 0
1 0 0 1	0 0 0
1 0 1 0	0 1 0
1 0 1 1	0 0 0
1 1 0 0	1 0 0
1 1 0 1	1 0 1
1 1 1 0	0 0 0
1 1 1 1	1 1 1

K-map for $Q_2^* = D_2$

$Q_1 Q_0$		Q_2			
		00	01	11	10
E_{n-L}	00	1	0	0	0
	01	1	1	0	0
	11	1	1	1	0
	10	0	0	0	0

$$Q_2^* = D_2 = (\overline{E_{n-L}} \cdot \overline{Q_1} \cdot \overline{Q_0}) + (Q_2 \cdot \overline{Q_1}) + (E_{n-L} \cdot Q_2 \cdot Q_0)$$

K-map for $Q_1^* = D_1$


$Q_1 Q_0$		Q_2			
		00	01	11	10
E_{n-L}	00	0	0	0	0
	01	0	1	1	0
	11	0	0	1	0
	10	0	0	0	1

$$Q_1^* = D_1 = (\overline{E_{n-L}} \cdot Q_2 \cdot Q_0) + (Q_2 \cdot Q_1 \cdot Q_0) + (E_{n-L} \cdot \overline{Q_2} \cdot Q_1 \cdot \overline{Q_0})$$

K-map for $Q_0^* = D_0$

$Q_1 Q_0$		Q_2			
		00	01	11	10
E_{n-L}	00	0	0	0	0
	01	1	1	0	0
	11	0	1	1	0
	10	0	0	0	0
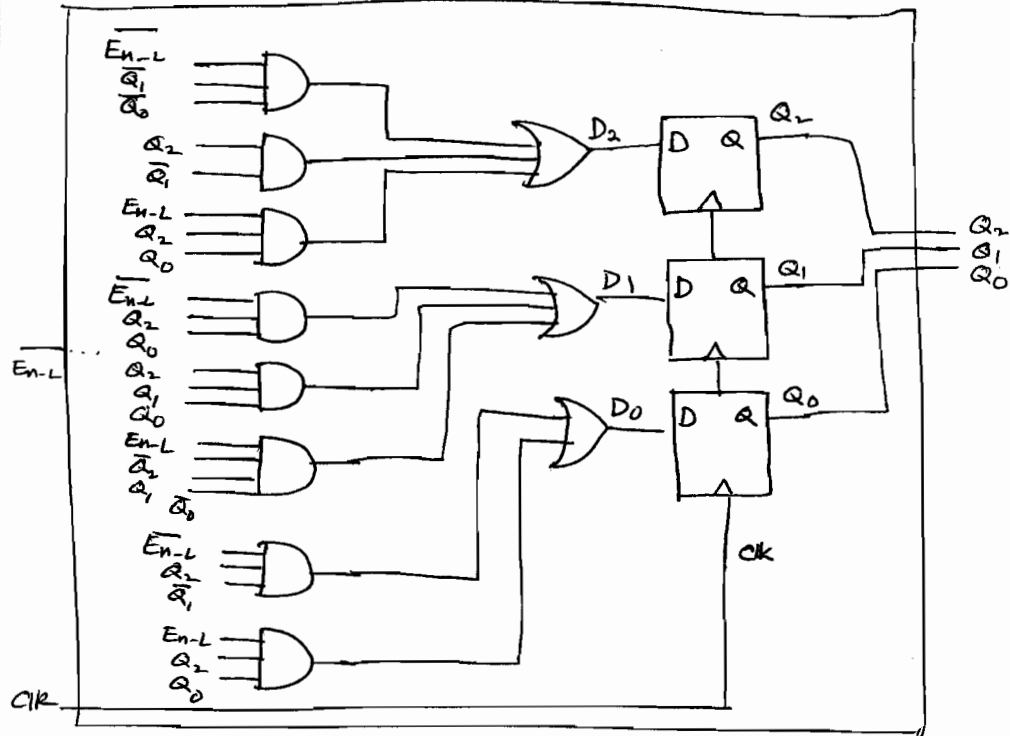
$$Q_0^* = D_0 = (\overline{E_{n-L}} \cdot Q_2 \cdot \overline{Q_1}) + (E_{n-L} \cdot Q_2 \cdot Q_0)$$



Inverters are not shown