

Example


The input to this circuit is the voltage source voltage

$$v_1 = 2e^{-2 \times 10^4 t} \text{ V}$$

The output is the current, i . The initial conditions are

$$i(0) = 1 \text{ A}, v(0) = 8 \text{ V}$$

Determine the current i for $t \geq 0$.

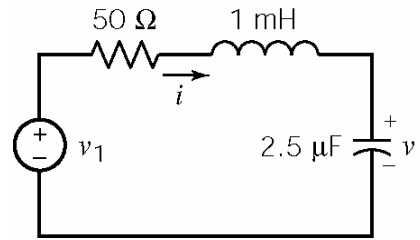
**Solution:**

KVL:

$$50i + 0.001 \frac{di}{dt} + v = 2e^{-2 \times 10^4 t} \text{ for } t \geq 0$$

The capacitor current and voltage are related by
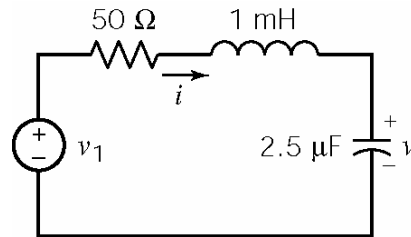
$$i = (2.5 \times 10^{-6}) \frac{dv}{dt}$$



$$v_1 = 2e^{-2 \times 10^4 t} \text{ V}, i(0) = 1 \text{ A}, v(0) = 8 \text{ V}$$

Taking the Laplace transforms of these equations:

$$50 I(s) + 0.001 [s I(s) - i(0)] + V(s) = \frac{2}{s + 2 \times 10^4}$$

$$I(s) = (2.5 \times 10^{-6}) [s V(s) - v(0)]$$

Solving for $I(s)$ yields

$$I(s) = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s + 10^4)(s + 2 \times 10^4)(s + 4 \times 10^4)} = \frac{A}{s + 10^4} + \frac{B}{s + 2 \times 10^4} + \frac{C}{s + 4 \times 10^4}$$

where

$$A = (s + 10^4) I(s) \Big|_{s = -10^4} = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s + 2 \times 10^4)(s + 4 \times 10^4)} \Big|_{s = -10^4} = \frac{-2 \times 10^8}{3 \times 10^8} = \frac{-2}{3}$$

$$B = (s + 2 \times 10^4) I(s) \Big|_{s = -2 \times 10^4} = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s + 10^4)(s + 4 \times 10^4)} \Big|_{s = -2 \times 10^4} = \frac{0.4 \times 10^8}{2 \times 10^8} = \frac{1}{5}$$

$$C = (s + 4 \times 10^4) I(s) \Big|_{s = -4 \times 10^4} = \frac{s^2 + 1.4 \times 10^4 s - 1.6 \times 10^8}{(s + 10^4)(s + 2 \times 10^4)} \Big|_{s = -4 \times 10^4} = \frac{8.8 \times 10^8}{6 \times 10^8} = \frac{22}{15}$$

Finally


$$I(s) = -\frac{2/3}{s + 10000} + \frac{1/5}{s + 20000} + \frac{22/15}{s + 40000} \Rightarrow i(t) = \frac{1}{15} [-10e^{-10000t} + 3e^{-20000t} + 22e^{-40000t}] u(t) \text{ A}$$

Example


Determine the capacitor voltage, v_c , for $t \geq 0$.

The initial conditions is

$$v_c(0) = 0$$

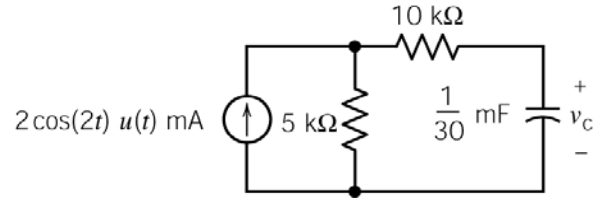**Solution:**

After a source transformation we have

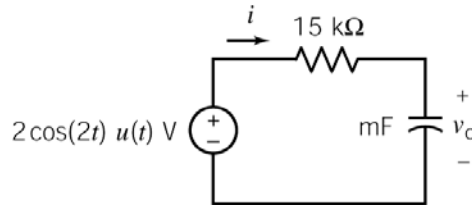

Then

$$\left. \begin{aligned} v_c + 15 \times 10^3 i &= 10 \cos 2t \\ i &= \left(\frac{1}{30} \times 10^{-3} \right) \frac{dv_c}{dt} \end{aligned} \right\} \Rightarrow \frac{dv_c}{dt} + 2v_c = 20 \cos 2t$$

Taking the Laplace Transform yields:

$$sV_c(s) - v_c(0) + 2V_c(s) = 20 \frac{s}{s^2 + 4}$$

With $v_c(0) = 0$, we have

$$V_c(s) = \frac{20s}{(s+2)(s^2+4)} = \frac{A}{s+2} + \frac{B}{s+j2} + \frac{B^*}{s-j2}$$

where


$$A = \frac{20s}{s^2+4} \Big|_{s=-2} = \frac{-40}{8} = -5, \quad B = \frac{20s}{(s+2)(s-j2)} \Big|_{s=-j2} = \frac{5}{1-j} = \frac{5}{2} + j\frac{5}{2} \quad \text{and} \quad B^* = \frac{5}{2} - j\frac{5}{2}$$

Then

$$V_c(s) = \frac{-5}{s+2} + \frac{\frac{5}{2} + j\frac{5}{2}}{s+j2} + \frac{\frac{5}{2} - j\frac{5}{2}}{s-j2} \Rightarrow v_c(t) = -5e^{-2t} + 5(\cos 2t + \sin 2t) \text{ V}$$

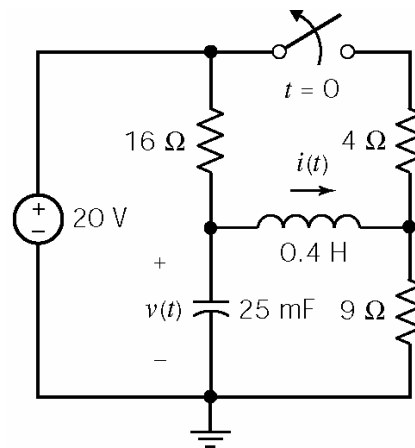Example:

Determine the inductor current, $i(t)$, in this circuit.




Solution

After the switch opens, apply KCL and KVL to get

$$R_1 \left(i(t) + C \frac{d}{dt} v(t) \right) + v(t) = V_s$$

Apply KVL to get
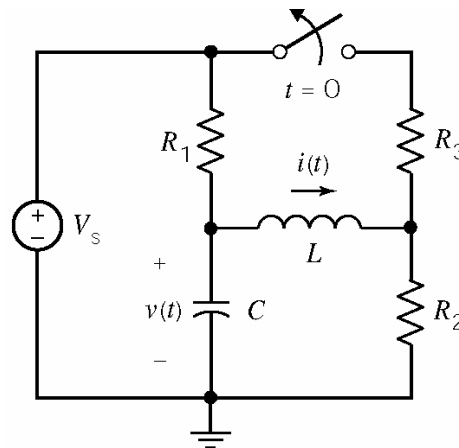
$$v(t) = L \frac{d}{dt} i(t) + R_2 i(t)$$



Substituting $v(t)$ into the first equation gives

$$R_1 \left(i(t) + C \frac{d}{dt} \left(L \frac{d}{dt} i(t) + R_2 i(t) \right) \right) + L \frac{d}{dt} i(t) + R_2 i(t) = V_s$$

then

$$R_1 C L \frac{d^2}{dt^2} i(t) + (R_1 C R_2 + L) \frac{d}{dt} i(t) + (R_1 + R_2) i(t) = V_s$$

Dividing by $R_1 C L$:

$$\frac{d^2}{dt^2} i(t) + \left(\frac{R_1 C R_2 + L}{R_1 C L} \right) \frac{d}{dt} i(t) + \left(\frac{R_1 + R_2}{R_1 C L} \right) i(t) = \frac{V_s}{R_1 C L}$$

With the given values: $\frac{d^2}{dt^2} i(t) + 25 \frac{d}{dt} i(t) + 156.25 i(t) = 125$

Taking the Laplace transform:


$$\left[s^2 I(s) - \left(\frac{d}{dt} i(0+) + s i(0+) \right) \right] + 25 [s I(s) - i(0+)] + 156.25 I(s) = \frac{125}{s}$$

We need the initial conditions. For $t < 0$, The switch is closed and the circuit is at steady state. At steady state, the capacitor acts like an open circuit and the inductor acts like a short circuit. Using voltage division

$$v(0^-) = \frac{9}{9 + (16 \parallel 4)} 20 = 14.754 \text{ V}$$

Then, using current division
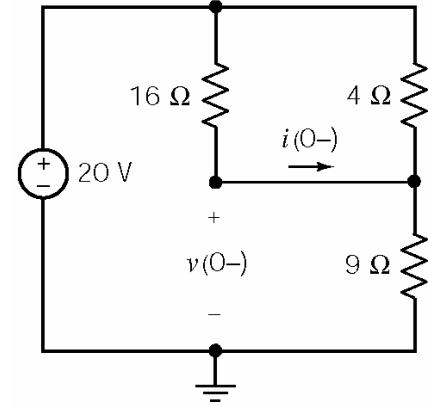
$$i(0^-) = \left(\frac{4}{16 + 4} \right) \frac{v(0^-)}{9} = 0.328 \text{ A}$$



The capacitor voltage and inductor current are continuous so $v(0^+) = v(0^-)$ and $i(0^+) = i(0^-)$.

After the switch opens

$$v(t) = L \frac{d}{dt} i(t) + R_2 i(t) \Rightarrow \frac{d}{dt} i(0^+) = \frac{v(0^+)}{0.4} + \frac{9 i(0^+)}{0.4} = \frac{14.754}{0.4} + \frac{9(0.328)}{0.4} = 29.508$$

Substituting these initial conditions into the Laplace transformed differential equation gives

$$\left[s^2 I(s) - (29.508 + 0.328s) \right] + 25 \left[s I(s) - 0.328 \right] + 156.25 I(s) = \frac{125}{s}$$

$$\left(s^2 + 25s + 156.25 \right) I(s) = \frac{125}{s} + (29.508 + 0.328s) + 25(0.328)$$

so

$$\begin{aligned} I(s) &= \frac{0.328s^2 + (29.508 + 25(0.328)) + 125}{s(s^2 + 25s + 156.25)} \\ &= \frac{0.328s^2 + (29.508 + 25(0.328)) + 125}{s(s + 12.5)^2} = \frac{-0.471}{s + 12.5} + \frac{23.6}{(s + 12.5)^2} + \frac{0.8}{s} \end{aligned}$$

Taking the inverse Laplace transform

$$i(t) = 0.8 + e^{-12.5t} (23.6t - 0.471) \text{ A for } t \geq 0$$

so

$$i(t) = \begin{cases} 0.328 \text{ A} & \text{for } t \leq 0 \\ 0.8 + e^{-12.5t} (23.6t - 0.471) \text{ A} & \text{for } t \geq 0 \end{cases}$$