

**Example**


The input to a linear circuit is the voltage,  $v_i$ . The output is the voltage,  $v_o$ . The transfer function of the circuit is

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

The poles and zeros of  $H(s)$  are shown on this pole-zero diagram. (There are no zeros.) The dc gain of the circuit is

$$\mathbf{H}(0) = 5$$

Determine the step response of the circuit.

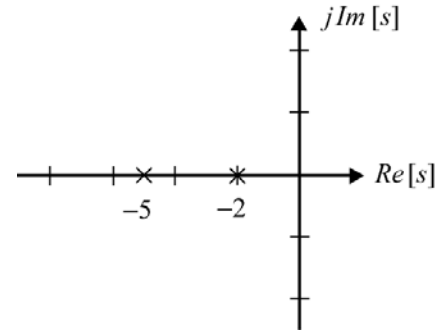**Solution:**

The transfer function of the circuit is

$$H(s) = \frac{a}{(s+2)(s+5)}$$

where  $a$  is a constant to be determined. The circuit is stable because all its poles lie in the right half of the  $s$ -plane. Consequently,

$$\mathbf{H}(\omega) = H(s) \Big|_{s=j\omega} = \frac{a}{(2+j\omega)(5+j\omega)} = \frac{\frac{a}{10}}{\left(1+j\frac{\omega}{2}\right)\left(1+j\frac{\omega}{5}\right)}$$

At dc ( $\omega = 0$ )

$$5 = \mathbf{H}(0) = \frac{a}{10} \Rightarrow a = 50$$

The step response is given by

$$v_o(t) = \mathcal{L}^{-1} \left[ \frac{H(s)}{s} \right] = \mathcal{L}^{-1} \left[ \frac{50}{s(s+2)(s+5)} \right] = \mathcal{L}^{-1} \left[ \frac{5}{s} + \frac{\frac{10}{3}}{s+5} - \frac{\frac{25}{3}}{s+2} \right] = \left( 5 + \frac{10}{3}e^{-5t} - \frac{25}{3}e^{-2t} \right) u(t) \quad \text{V}$$



**Example**


The input to a linear circuit is the voltage,  $v_i$ . The output is the voltage,  $v_o$ . The transfer function of the circuit is

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

The poles and zeros of  $H(s)$  are shown on this pole-zero diagram. At  $\omega = 5$  rad/s the gain of the circuit is

$$\mathbf{H}(5) = 10$$

Determine the step response of the circuit.

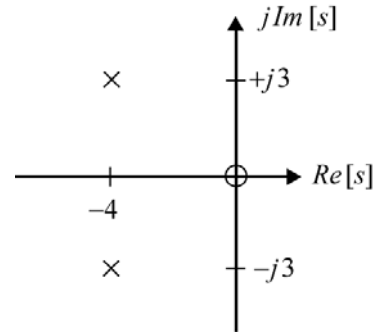**Solution:**

The transfer function of the circuit is

$$H(s) = \frac{a(s-0)}{(s+4-j3)(s+4+j3)} = \frac{as}{s^2+8s+25}$$

where  $a$  is a constant to be determined. The circuit is stable because all its poles lie in the right half of the  $s$ -plane. Consequently,

$$\mathbf{H}(\omega) = H(s)|_{s=j\omega} = \frac{ja\omega}{(j\omega)^2 + j8\omega + 25} = \frac{ja\omega}{(25 - \omega^2) + j8\omega}$$

At  $\omega = 5$  rad/s

$$10 = \frac{ja5}{(25 - 5^2) + j8(5)} = \frac{a}{8} \Rightarrow a = 80$$

The step response is given by

$$\begin{aligned} v_o(t) &= \mathcal{L}^{-1} \left[ \frac{H(s)}{s} \right] = \mathcal{L}^{-1} \left[ \frac{80s}{s(s^2+8s+25)} \right] = \mathcal{L}^{-1} \left[ \frac{80}{s^2+8s+25} \right] = \mathcal{L}^{-1} \left[ \frac{80}{3} \times \frac{3}{(s+4)^2+3^2} \right] \\ &= \frac{80}{3} e^{-4t} \sin(4t) u(t) \text{ V} \end{aligned}$$




**Example**

The input to a linear circuit is the voltage,  $v_i$ . The output is the voltage,  $v_o$ . The transfer function of the circuit is

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

The poles and zeros of  $H(s)$  are shown on this pole-zero diagram. (There is a double pole at  $s = -4$ .) The dc gain of the circuit is

$$\mathbf{H(0) = 5}$$

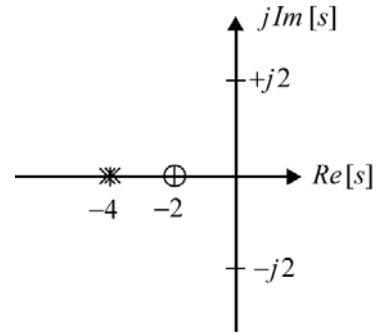

Determine the step response of the circuit.

**Solution:**

The transfer function of the circuit is

$$H(s) = \frac{a(s+2)}{(s+4)^2}$$

where  $a$  is a constant to be determined. The circuit is stable because all its poles lie in the right half of the  $s$ -plane. Consequently,

$$\mathbf{H(\omega) = H(s)}\bigg|_{s=j\omega} = \frac{a(j\omega+2)}{(j\omega+4)^2} = \frac{\frac{a}{8}\left(1+j\frac{\omega}{2}\right)}{\left(1+j\frac{\omega}{4}\right)^2}$$

At dc ( $\omega = 0$ )

$$5 = \mathbf{H(0)} = \frac{a}{8} \Rightarrow a = 40$$

The step response is given by

$$v_o(t) = \mathcal{L}^{-1}\left[\frac{H(s)}{s}\right] = \mathcal{L}^{-1}\left[\frac{40(s+2)}{s(s+4)^2}\right] = \mathcal{L}^{-1}\left[\frac{5}{s} - \frac{5}{s+4} + \frac{20}{(s+4)^2}\right] = (5 + (20t - 5)e^{-4t})u(t) \text{ V}$$



**Example:**

The input to a circuit is the voltage,  $v_i$ . The step response of the circuit is

$$v_o = 5e^{-4t} \sin(2t)u(t) \text{ V}$$


Sketch the pole-zero diagram for this circuit.

**Solution:**

$$\begin{aligned} \frac{H(s)}{s} &= \mathcal{L}[5e^{-4t} \sin(2t)u(t)] = 5 \times \frac{2}{s^2 + 2^2} \Big|_{s \leftarrow s+4} = \frac{10}{(s+4)^2 + 2^2} \\ &= \frac{10}{s^2 + 8s + 20} = \frac{10}{(s+4-j2)(s+4+j2)} \end{aligned}$$

Consequently

$$H(s) = \frac{10s}{(s+4-j2)(s+4+j2)}$$

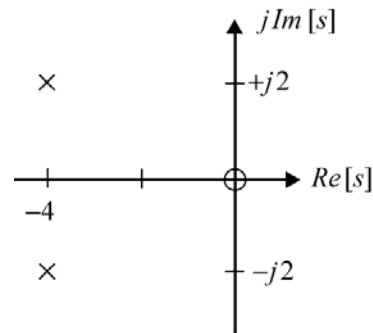**Example:**

The input to a circuit is the voltage,  $v_i$ . The step response of the circuit is

$$v_o = 5te^{-4t}u(t) \text{ V}$$

Sketch the pole-zero diagram for this circuit.

**Solution:**

$$\frac{H(s)}{s} = \mathcal{L}[5te^{-4t}u(t) \text{ V}] = 5 \times \frac{1}{s^2} \Big|_{s \leftarrow s+4} = \frac{5}{(s+4)^2}$$

Consequently

$$H(s) = \frac{5s}{(s+4)^2}$$

