
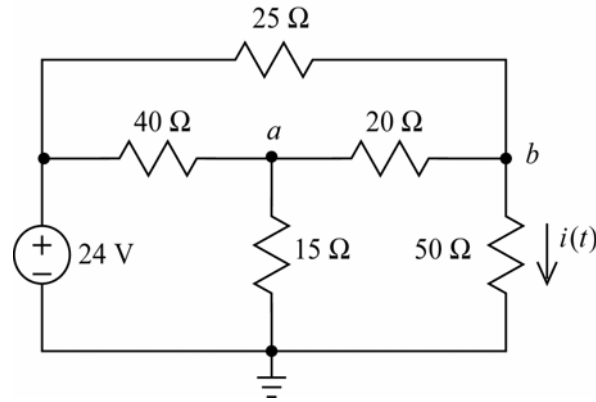


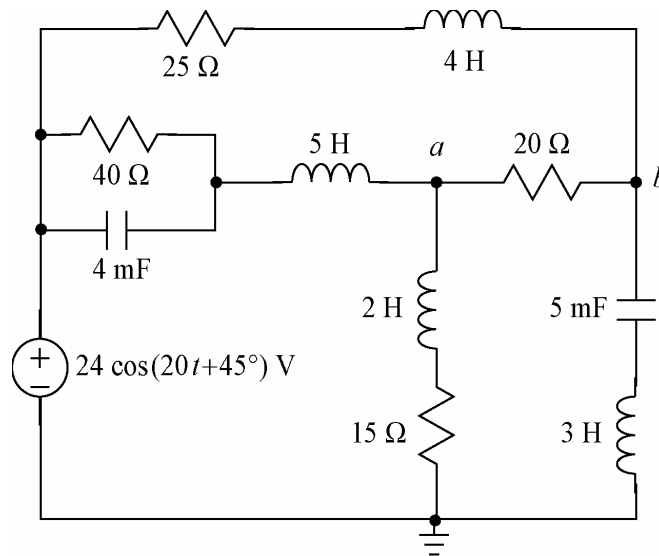Example1 : Determine the node voltages at nodes a and b of each of the circuits shown in Figure 1.



(a)



(b)

Figure 1

Solution:

(a) The node equations are

$$\frac{24 - v_a}{40} = \frac{v_a - v_b}{20} + \frac{v_a}{15}$$

$$\frac{24 - v_b}{25} + \frac{v_a - v_b}{20} = \frac{v_b}{50}$$


or

$$\begin{bmatrix} \frac{1}{40} + \frac{1}{20} + \frac{1}{15} & -\frac{1}{20} \\ -\frac{1}{20} & \frac{1}{25} + \frac{1}{20} + \frac{1}{50} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} \frac{24}{40} \\ \frac{24}{25} \end{bmatrix}$$

Solving using MATLAB gives

$$v_a = 8.713 \text{ V} \quad \text{and} \quad v_b = 12.69 \text{ V}$$

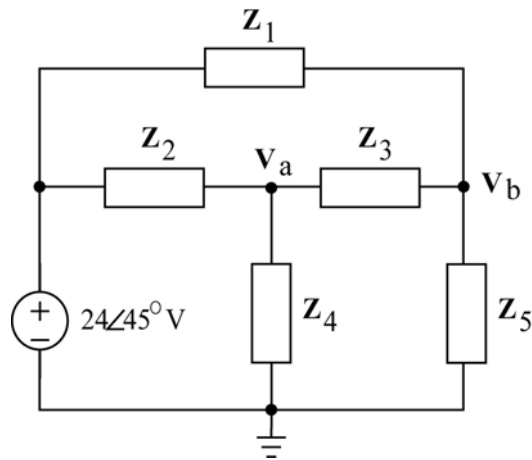(b) Use phasors and impedances to represent the circuit in the frequency domain as



where

$$\mathbf{Z}_1 = 25 + j(20)4 = 25 + j80 = 83.82 \angle 72.7^\circ \Omega$$

$$\mathbf{Z}_2 = \left(40 \parallel \frac{1}{j(20)(0.004)} \right) + j(20)5 = 3.56 + j88.6 = 88.68 \angle 87.7^\circ \Omega$$

$$\mathbf{Z}_3 = 20 \Omega$$

$$\mathbf{Z}_4 = 15 + j(20)2 = 15 + j40 = 42.72 \angle 69.4^\circ$$

$$\mathbf{Z}_5 = j(20)3 + \frac{1}{j(20)(0.005)} = j50 = 50 \angle 90^\circ \Omega$$

The node equations are

$$\frac{24 \angle 45^\circ - \mathbf{V}_a}{\mathbf{Z}_2} = \frac{\mathbf{V}_a}{\mathbf{Z}_4} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3}$$

$$\frac{24 \angle 45^\circ - \mathbf{V}_b}{\mathbf{Z}_1} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3} = \frac{\mathbf{V}_b}{\mathbf{Z}_5}$$

$$\begin{bmatrix} \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{Z_4} & -\frac{1}{Z_3} \\ -\frac{1}{Z_3} & \frac{1}{Z_1} + \frac{1}{Z_3} + \frac{1}{Z_5} \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} = \begin{bmatrix} \frac{24\angle 45^\circ}{Z_2} \\ \frac{24\angle 45^\circ}{Z_1} \end{bmatrix}$$

Solving using MATLAB gives

$$V_a = 7.89\angle 44.0^\circ$$


$$V_b = 8.45\angle 45.1^\circ$$

so


$$v_a(t) = 7.89 \cos(20t + 44^\circ) \text{ V}$$

$$v_b(t) = 8.45 \cos(20t + 45.1^\circ) \text{ V}$$

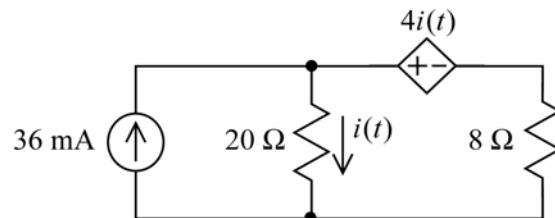Example 2 Determine the steady state current, $i(t)$, for each of the circuits shown in 2.



(a)

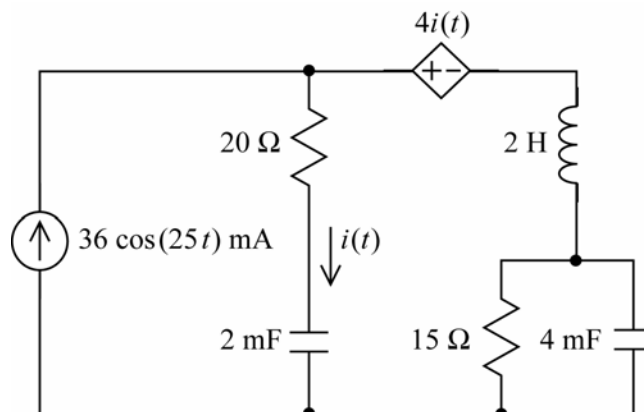

(b)

Figure 2

Solution

(a) Use KVL to see that the voltage across the $8\ \Omega$ resistor is $20i(t) - 4i(t) = 16i(t)$.


Apply KCL to the supernode corresponding to the dependent voltage source to get

$$0.036 = i(t) + \frac{16i(t)}{8} = 3i(t)$$

so

$$i(t) = 12\ \text{mA}$$

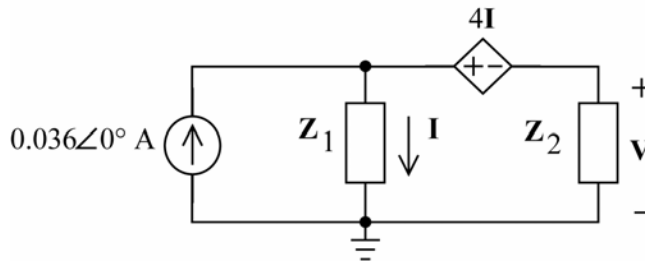(b) Represent the circuit in the frequency domain using phasors and impedances.



Where

$$\mathbf{Z}_1 = 20 + \frac{1}{j(25)(0.002)} = 20 - j20\ \Omega$$

$$\mathbf{Z}_2 = j50 + \left(15 \parallel \frac{1}{j(25)(0.004)} \right) = 43.3 \angle 83.9^\circ\ \Omega$$

Use KVL to get

$$\mathbf{V} = \mathbf{Z}_1 \mathbf{I} - 4\mathbf{I} = (\mathbf{Z}_1 - 4)\mathbf{I}$$

Then apply KCL to the supernode corresponding to the dependent source to get

$$0.036 \angle 0^\circ = \mathbf{I} + \frac{(\mathbf{Z}_1 - 4)\mathbf{I}}{\mathbf{Z}_2} = \left(\frac{\mathbf{Z}_1 + \mathbf{Z}_2 - 4}{\mathbf{Z}_2} \right) \mathbf{I}$$

so

$$\mathbf{I} = \frac{\mathbf{Z}_2 (0.036 \angle 0^\circ)}{\mathbf{Z}_1 + \mathbf{Z}_2 - 4} = 50.4 \angle 35.7^\circ\ \text{mA}$$

so

$$i(t) = 50.4 \cos(25t + 35.7^\circ)\ \text{mA}$$