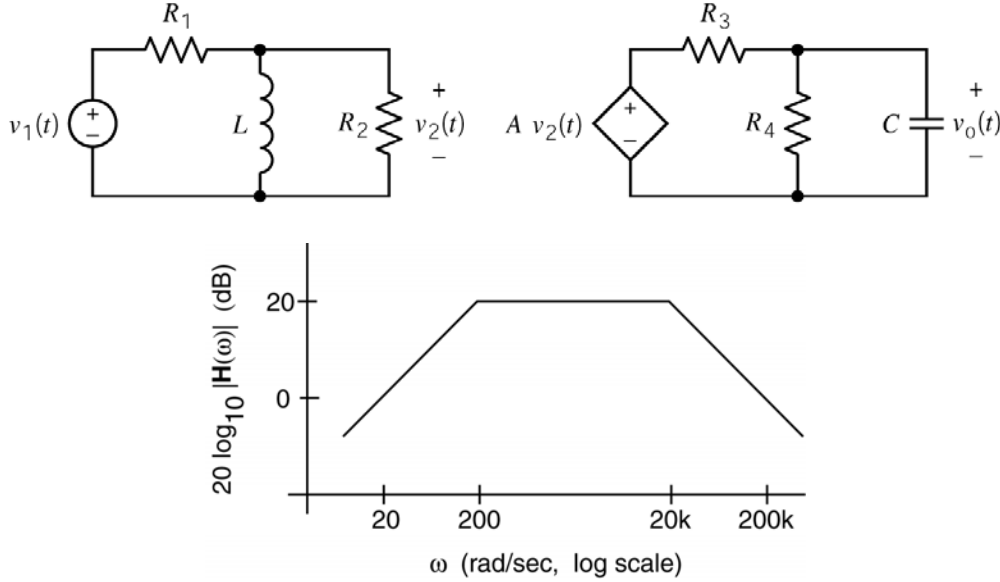



**Example:**

Consider this circuit and corresponding asymptotic magnitude Bode plot. The input to this circuit is the voltage of the voltage source,  $v_1(t)$ . The output is the capacitor voltage  $v_o(t)$ . Design this circuit to have this Bode plot.



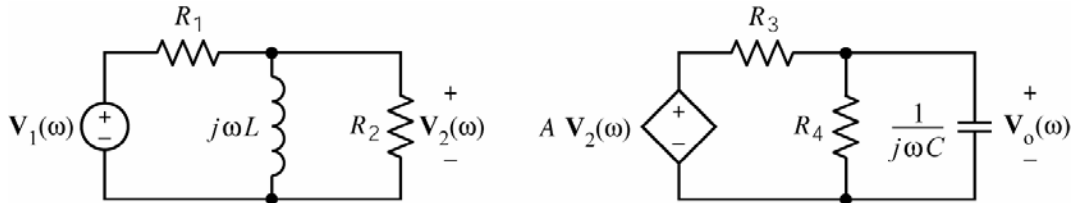**Solution:**

Represent the circuit in the frequency domain:



Using voltage division twice gives:

$$\frac{V_2(\omega)}{V_1(\omega)} = \frac{\frac{j\omega L R_2}{R_2 + j\omega L}}{R_1 + \frac{j\omega L R_2}{R_2 + j\omega L}} = \frac{j\omega L R_2}{R_1 R_2 + j\omega L(R_1 + R_2)} = \frac{L}{R_1} \frac{j\omega}{1 + j\omega \frac{L(R_1 + R_2)}{R_1 R_2}}$$

and

$$\frac{V_o(\omega)}{V_2(\omega)} = \frac{\frac{R_4}{1 + j\omega C R_4}}{R_3 + \frac{R_4}{1 + j\omega C R_4}} A = \frac{A R_4}{R_3 + R_4 + j\omega C R_3 R_4} = \frac{\frac{A R_4}{R_3 + R_4}}{1 + j\omega \frac{C R_3 R_4}{R_3 + R_4}}$$

Combining these equations gives

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{ALR_4}{R_1(R_3 + R_4)} \frac{j\omega}{\left(1 + j\omega \frac{L(R_1 + R_2)}{R_1 R_2}\right) \left(1 + j\omega \frac{CR_3 R_4}{R_3 + R_4}\right)}$$

The Bode plot corresponds to the network function:

$$\mathbf{H}(\omega) = \frac{k j\omega}{\left(1 + j \frac{\omega}{p_1}\right) \left(1 + j \frac{\omega}{p_2}\right)} = \frac{k j\omega}{\left(1 + j \frac{\omega}{200}\right) \left(1 + j \frac{\omega}{20000}\right)}$$

$$\mathbf{H}(\omega) \approx \begin{cases} \frac{k j\omega}{1 \cdot 1} = k j\omega & \omega \leq p_1 \\ \frac{k j\omega}{j\omega \cdot 1} = k p_1 & p_1 \leq \omega \leq p_2 \\ \frac{k j\omega}{j\omega \cdot j\omega} = \frac{k p_1 p_2}{j\omega} & \omega \geq p_2 \end{cases}$$

This equation indicates that  $|\mathbf{H}(\omega)| = k p_1$  when  $p_1 \leq \omega \leq p_2$ . The Bode plot indicates that  $|\mathbf{H}(\omega)| = 20 \text{ dB} = 10$  when  $p_1 \leq \omega \leq p_2$ . Consequently

$$k = \frac{10}{p_1} = \frac{10}{200} = 0.05$$

Finally,

$$\mathbf{H}(\omega) = \frac{0.05 j\omega}{\left(1 + j \frac{\omega}{200}\right) \left(1 + j \frac{\omega}{20000}\right)}$$


Comparing the equation for  $\mathbf{H}(\omega)$  obtained from the circuit to the equation for  $\mathbf{H}(\omega)$  obtained from the Bode plot gives:

$$0.05 = \frac{ALR_4}{R_1(R_3 + R_4)}, \quad 200 = \frac{R_1 R_2}{L(R_1 + R_2)} \quad \text{and} \quad 20000 = \frac{R_3 + R_4}{C R_3 R_4}$$

Pick  $L = 1 \text{ H}$ , and  $R_1 = R_2$ , then  $R_1 = R_2 = 400 \Omega$ . Let  $C = 0.1 \mu\text{F}$  and  $R_3 = R_4$ , then  $R_3 = R_4 = 1000 \Omega$ . Finally,  $A=40$ .

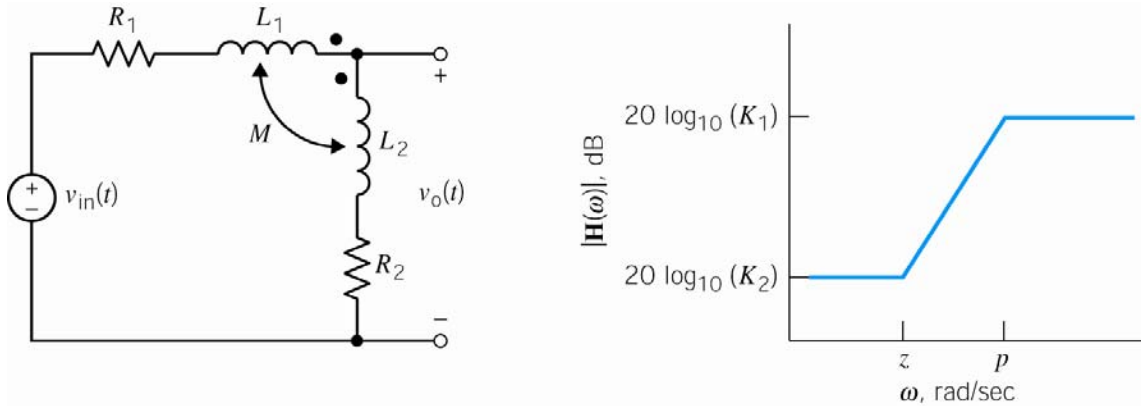
**Example:**

Consider this circuit and corresponding asymptotic magnitude Bode plot. The input to this circuit is the voltage of the voltage source,  $v_{in}(t)$ . The output is the voltage  $v_o(t)$ . Design this circuit to have this Bode plot.



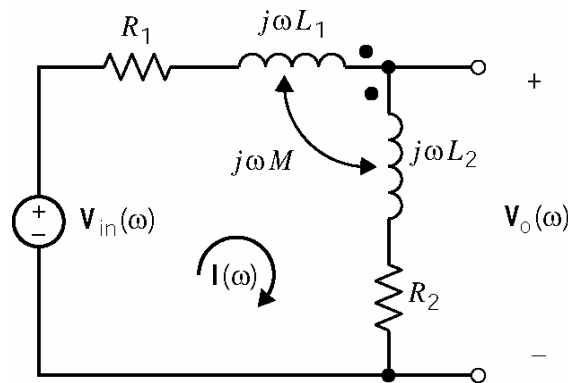**Solution:**

Represent the circuit in the frequency domain:



Mesh equations:

$$\mathbf{V}_{in}(\omega) = \mathbf{I}(\omega) [R_1 + (j\omega L_1 - j\omega M) + (-j\omega M + j\omega L_2) + R_2]$$

$$\mathbf{V}_o(\omega) = \mathbf{I}(\omega) [(-j\omega M + j\omega L_2) + R_2]$$

Solving yields:

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_{in}(\omega)} = \frac{R_2 + j\omega(L_2 - M)}{R_1 + R_2 + j\omega(L_1 + L_2 - 2M)}$$


Comparing to the given Bode plot yields:

$$K_1 = \lim_{\omega \rightarrow \infty} |\mathbf{H}(\omega)| = \frac{L_2 - M}{L_1 + L_2 - 2M} = 0.75 \quad \text{and} \quad K_2 = \lim_{\omega \rightarrow 0} |\mathbf{H}(\omega)| = \frac{R_2}{R_1 + R_2} = 0.2$$

$$z = \frac{R_2}{L_2 - M} = 333 \text{ rad/s} \quad \text{and} \quad p = \frac{R_1 + R_2}{L_1 + L_2 - 2M} = 1250 \text{ rad/s}$$

**Example:**

Consider this circuit and corresponding asymptotic magnitude Bode plot. The input to this circuit is the voltage of the voltage source,  $v_1(t)$ . The output is the capacitor voltage  $v_o(t)$ . Design this circuit to have this Bode plot.

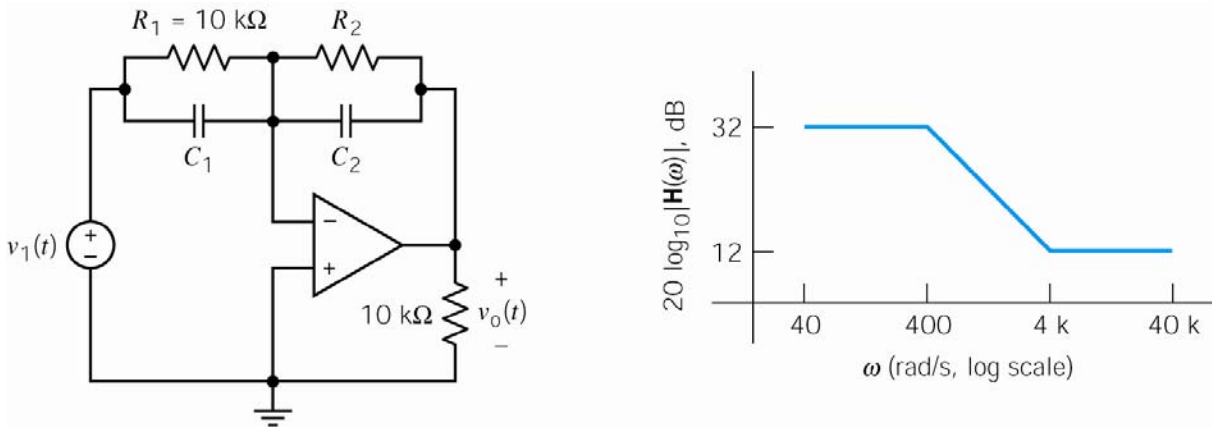**Solution:**

From Table 13.3-2:

$$\frac{R_2}{R_1} = k = 32 \text{ dB} = 40 \quad R_2 = 40(10 \times 10^3) = 400 \text{ k}\Omega$$

$$\frac{1}{C_2 R_2} = p = 400 \text{ rad/s} \Rightarrow C_2 = \frac{1}{(400)(400 \times 10^3)} = 6.25 \text{ nF}$$

$$\frac{1}{C_1 R_1} = z = 4000 \text{ rad/s} \Rightarrow C_1 = \frac{1}{(4000)(10 \times 10^3)} = 25 \text{ nF}$$