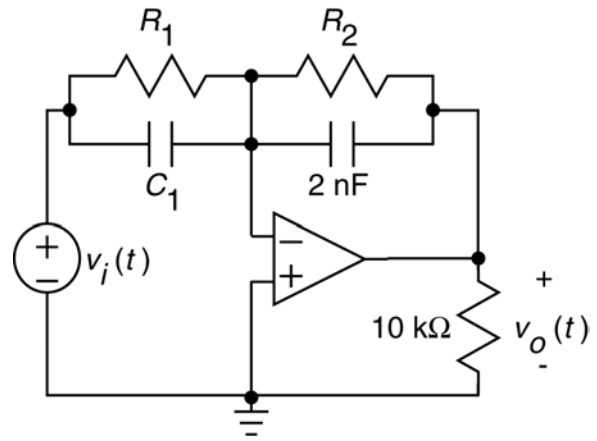


The input to this circuit shown is the voltage, $v_i(t)$, of the independent voltage source. The output is the voltage, $v_o(t)$, across the 10 k Ω resistor.



Six Bode plots, identified by the letters **A** through **F**, are shown on the next page.

1. Is it possible to design this circuit to have this Bode plot **A**? _____no_____ (yes or no)

2. Is it possible to design this circuit to have this Bode plot **B**? _____yes_____ (yes or no)

If yes, specify the required values of R_1 , R_2 and C_1 :

$$R_1 = \underline{\quad 10 \quad} \text{ k}\Omega, \quad R_2 = \underline{\quad 200 \quad} \text{ k}\Omega, \quad C_1 = \underline{\quad 4 \quad} \text{ nF}$$


3. Is it possible to design this circuit to have this Bode plot **E**? _____yes_____ (yes or no)

If yes, specify the required values of R_1 , R_2 and C_1 :


$$R_1 = \underline{\quad 10 \quad} \text{ k}\Omega, \quad R_2 = \underline{\quad 20 \quad} \text{ k}\Omega, \quad C_1 = \underline{\quad 40 \quad} \text{ nF}$$

4. Is it possible to design this circuit to implement Bode plot **F**? _____no_____ (yes or no)


Gain Bode Plots

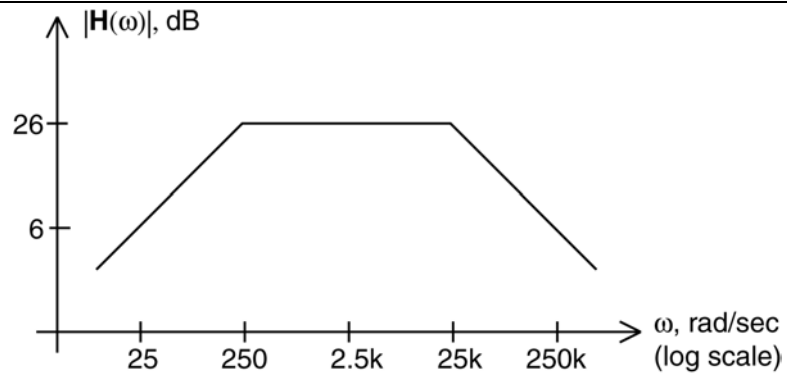


A

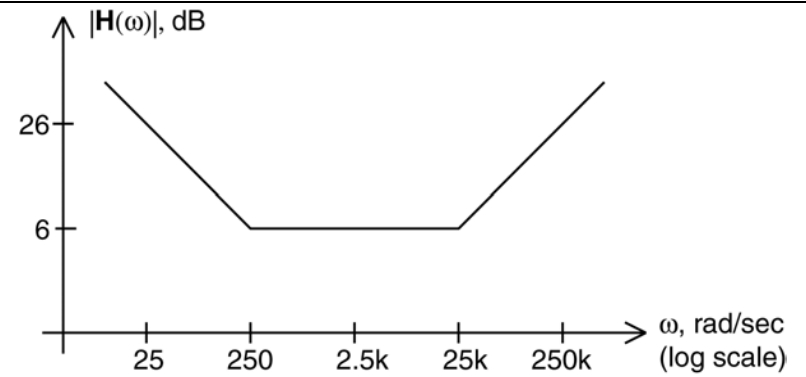


D

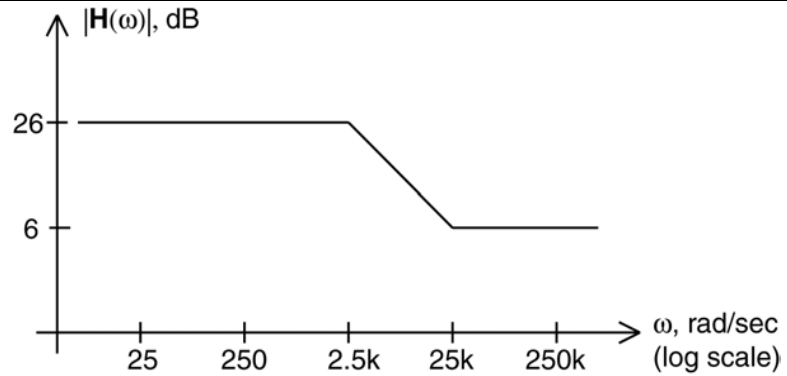


B

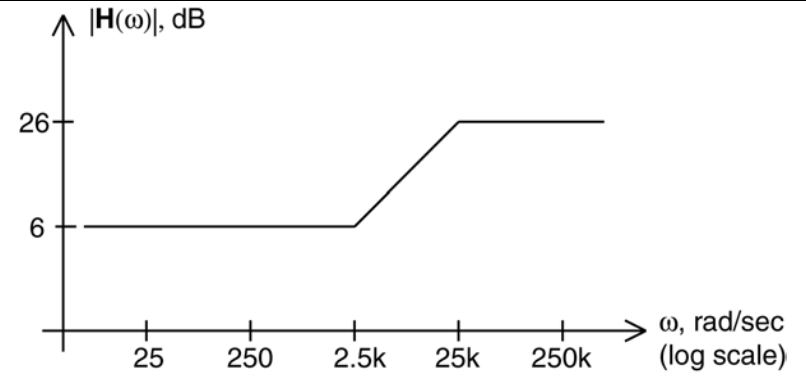

E

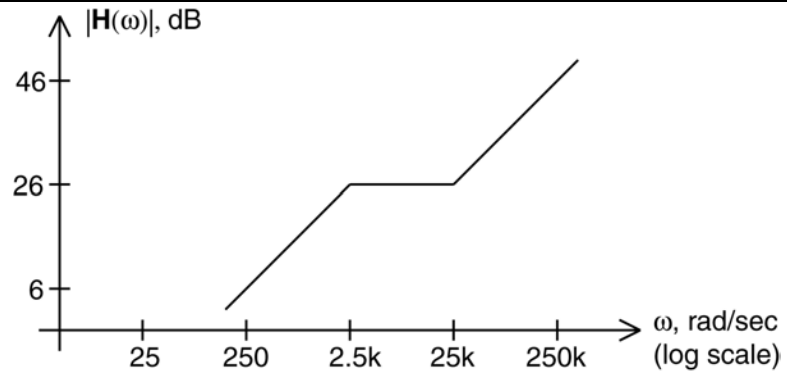

C

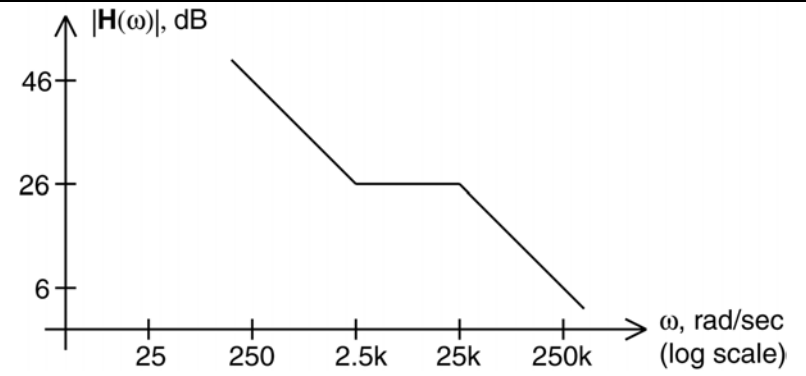

F