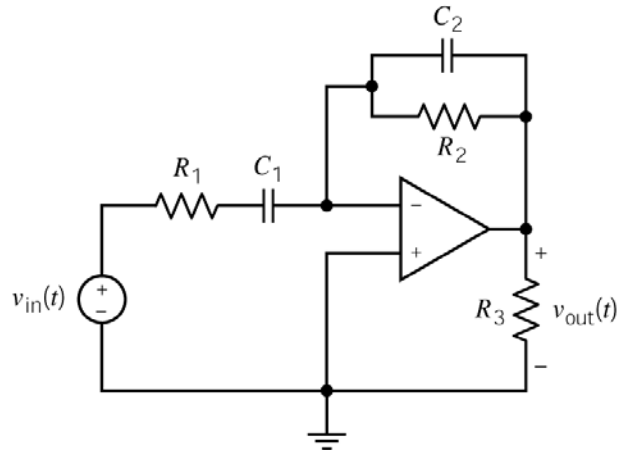


**Example:**

The input to this circuit is the voltage of the voltage source,  $v_{in}(t)$ . The output is the voltage across  $R_3$ ,  $v_{out}(t)$ . The component values are

$$C_1 = C_2 = 0.1 \mu\text{F},$$

$$R_1 = 5 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega \text{ and } R_3 = 20 \text{ k}\Omega$$



Sketch the asymptotic magnitude Bode plot for the network function.

**Solution:**

The network function is:

$$\mathbf{H}(\omega) = -\frac{R_2}{R_1 + \frac{1}{j\omega C_1}} = -C_1 R_2 \frac{j\omega}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$


This network function has poles at

$$p_1 = \frac{1}{R_1 C_1} = 2000 \text{ rad/s} \text{ and } p_2 = \frac{1}{R_2 C_2} = 1000 \text{ rad/s}$$

so


$$\mathbf{H}(\omega) \approx \begin{cases} -(C_1 R_2) j\omega & \omega < p_2 \\ -(C_1 R_2) \frac{j\omega}{j\omega C_1 R_1} = -\frac{R_2}{R_1} = -2 & p_2 < \omega < p_1 \\ -(C_1 R_2) \frac{j\omega}{(j\omega C_1 R_1)(j\omega C_2 R_2)} = -\frac{1}{j\omega C_2 R_1} & \omega > p_1 \end{cases}$$

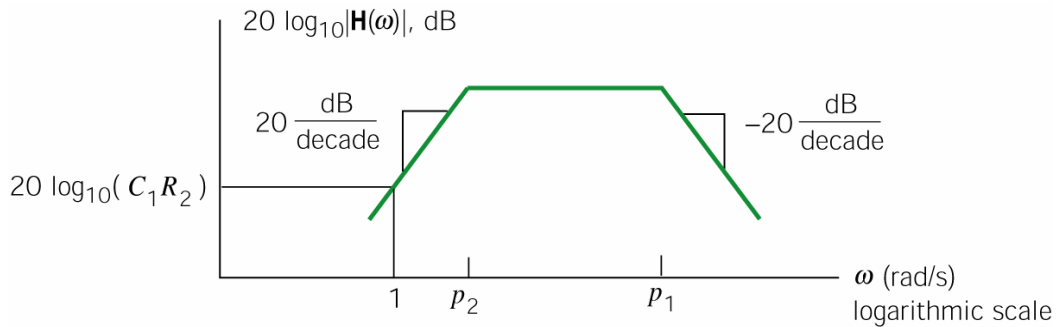The corresponding asymptotic magnitude Bode plot is:



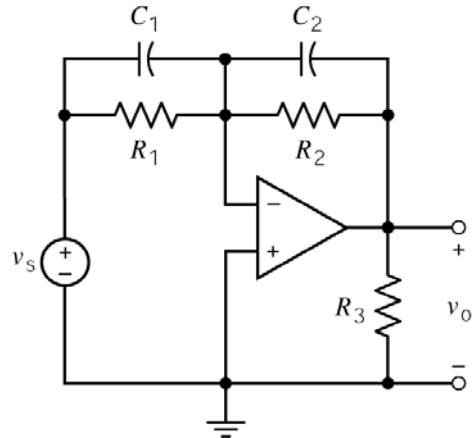**Example:**

The input to this circuit is the voltage of the voltage source,  $v_s(t)$ . The output is the voltage across  $R_3$ ,  $v_o(t)$ . Determine the network function,  $\mathbf{H}(\omega)$  and sketch the asymptotic magnitude Bode plot.




**Solution:**

The network function is:


$$\mathbf{H}(\omega) = -\frac{\frac{R_2}{1+j\omega C_2 R_2}}{\frac{R_1}{1+j\omega C_1 R_1}} = -\frac{R_2(1+j\omega C_1 R_1)}{R_1(1+j\omega C_2 R_2)} = \frac{K(1+j\frac{\omega}{z})}{1+j\frac{\omega}{p}}$$

where  $K = -\frac{R_2}{R_1}$ ,  $z = \frac{1}{C_1 R_1}$  and  $p = \frac{1}{C_2 R_2}$

When  $z < p$ , the bode plot is

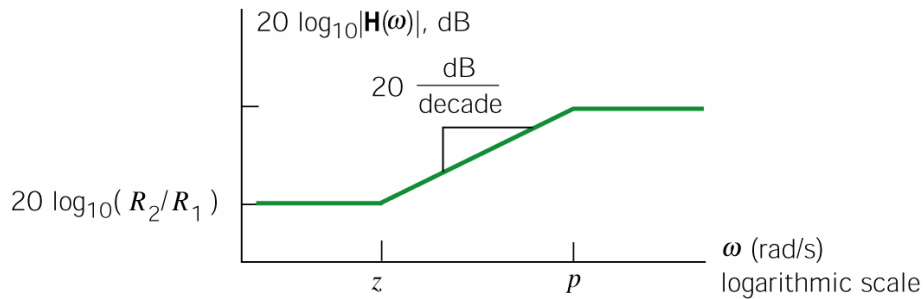


When  $z > p$ , the bode plot is

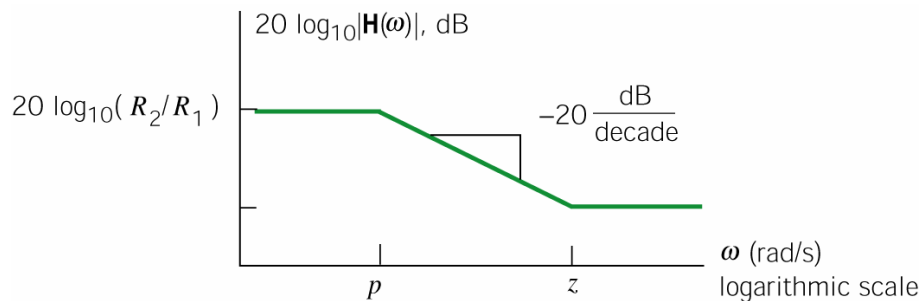

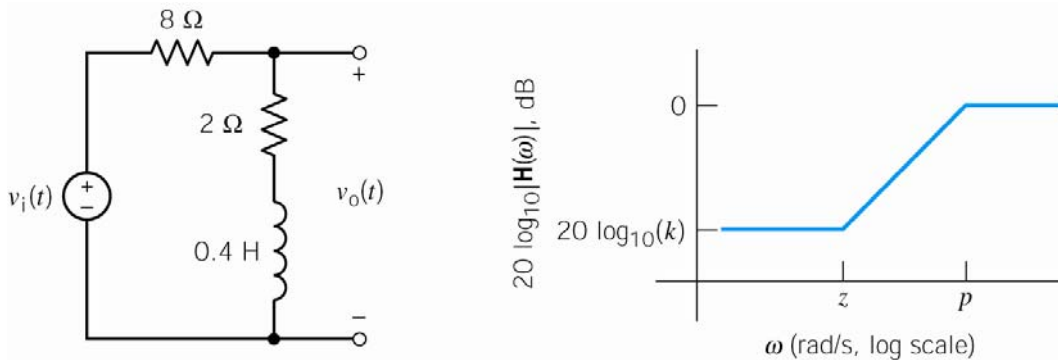**Example:**


Consider this circuit and corresponding asymptotic magnitude Bode plot. The input to this circuit is the voltage of the voltage source,  $v_i(t)$ . The output is the voltage  $v_o(t)$ . The network

function is  $\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ . Determine the values of the corner frequencies,  $p$  and  $z$ , and of the low-frequency gain,  $k$ .



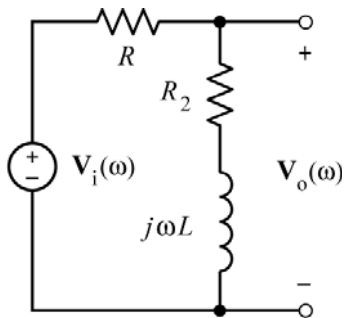**Solution:**

Represent the circuit in the frequency domain:



Using voltage division, the network function is:

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{R_2 + j\omega L}{R + R_2 + j\omega L}$$

$$= \left( \frac{R_2}{R + R_2} \right) \left( \frac{1 + j\omega \frac{L}{R_2}}{1 + j\omega \frac{L}{R + R_2}} \right)$$

With the given values:

$$\mathbf{H}(\omega) = \frac{(0.2)(1 + j(0.2)\omega)}{1 + j(0.04)\omega} \Rightarrow \begin{cases} k = 0.2 \\ z = \frac{1}{0.2} = 5 \\ p = \frac{1}{0.04} = 25 \end{cases}$$