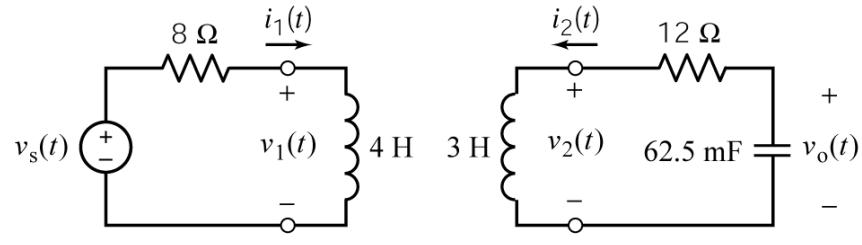



**Example:** Four similar circuits are shown below.. In each of these circuits

$$v_s(t) = 5 \cos(4t + 45^\circ) \text{ V.}$$


Determine  $v_2(t)$  for each of the circuits.




(a)

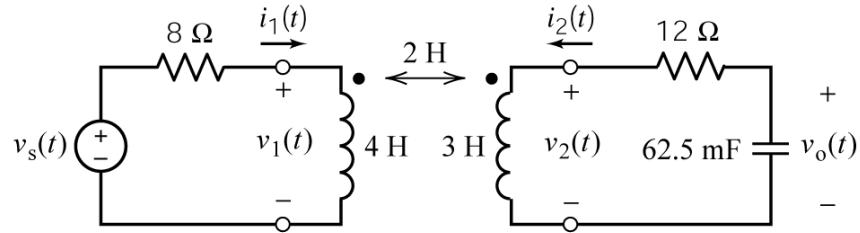

(b)

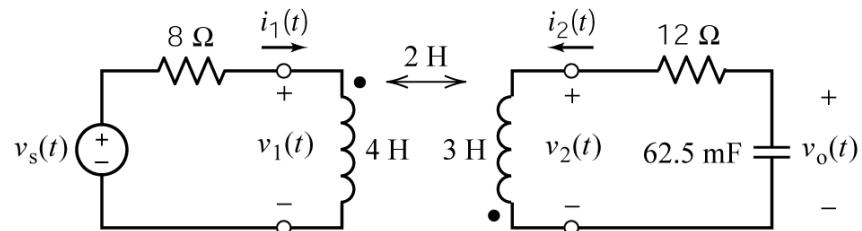


(c)

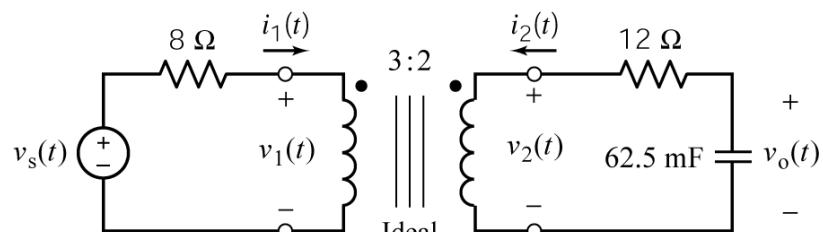

(d)

**Solution:**

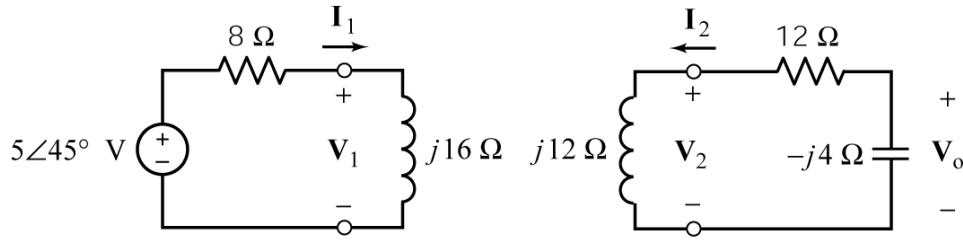

(a)

Coil voltages:

$$\mathbf{V}_1 = j16 \mathbf{I}_1$$

$$\mathbf{V}_2 = j12 \mathbf{I}_2$$

Mesh equations:

$$8 \mathbf{I}_1 + \mathbf{V}_1 - 5\angle 45^\circ = 0$$


$$-(12 - j4) \mathbf{I}_2 - j12 \mathbf{V}_2 = 0$$

Substitute the coil voltages into the mesh equations and do some algebra:

$$8 \mathbf{I}_1 + j16 \mathbf{I}_1 = 5\angle 45^\circ \Rightarrow \mathbf{I}_1 = 0.28\angle -18.4^\circ$$

$$-(12 - j4) \mathbf{I}_2 - j12 \mathbf{I}_2 = 0 \Rightarrow (-12 + j8) \mathbf{I}_2 = 0 \Rightarrow \mathbf{I}_2 = 0$$
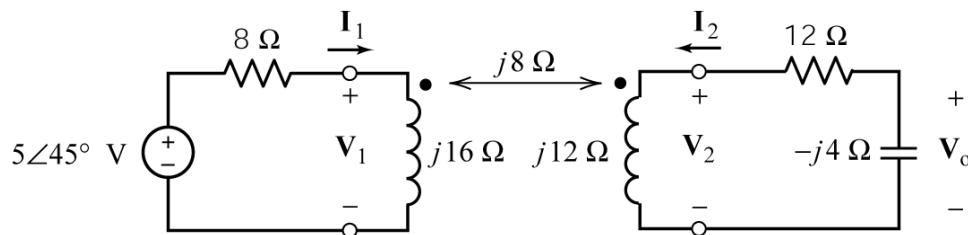
$$\mathbf{V}_o = -(-j4 \mathbf{I}_2) = 0$$



(b)

Coil voltages:

$$\mathbf{V}_1 = j16 \mathbf{I}_1 + j8 \mathbf{I}_2$$

$$\mathbf{V}_2 = j12 \mathbf{I}_2 + j8 \mathbf{I}_1$$

Mesh equations:

$$8 \mathbf{I}_1 + \mathbf{V}_1 - 5\angle 45^\circ = 0$$

$$-(12 - j4) \mathbf{I}_2 - \mathbf{V}_2 = 0$$


Substitute the coil voltages into the mesh equations and do some algebra:

$$\begin{aligned} 8\mathbf{I}_1 + j16\mathbf{I}_1 + j8\mathbf{I}_2 - 5\angle 45^\circ &= 0 \\ -(12 - j4)\mathbf{I}_2 - j12\mathbf{I}_2 - j8\mathbf{I}_1 &= 0 \end{aligned}$$

$$\begin{aligned} (8 + j16)\mathbf{I}_1 + j8\mathbf{I}_2 &= 5\angle 45^\circ \\ -j8\mathbf{I}_1 - (12 + j8)\mathbf{I}_2 &= 0 \end{aligned}$$

$$\begin{bmatrix} 8 + j16 & j8 \\ -j8 & -12 - j8 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 5\angle 45^\circ \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 0.2795\angle -4.2^\circ \\ 0.155\angle -127.9^\circ \end{bmatrix}$$
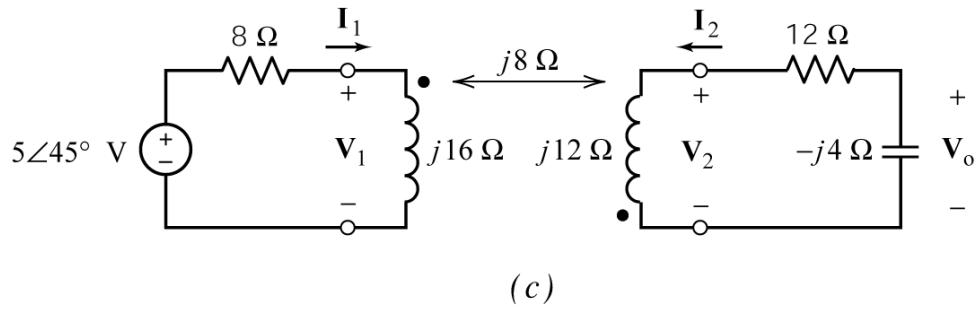
$$\mathbf{V}_o = -(-j4\mathbf{I}_2) = 0.62\angle 37.9^\circ$$



Coil voltages:

$$\begin{aligned} \mathbf{V}_1 &= j16\mathbf{I}_1 - j8\mathbf{I}_2 \\ \mathbf{V}_2 &= j12\mathbf{I}_2 - j8\mathbf{I}_1 \end{aligned}$$

Mesh equations:

$$\begin{aligned} 8\mathbf{I}_1 + \mathbf{V}_1 - 5\angle 45^\circ &= 0 \\ -(12 - j4)\mathbf{I}_2 - \mathbf{V}_2 &= 0 \end{aligned}$$



Substitute the coil voltages into the mesh equations and do some algebra:

$$\begin{aligned} 8\mathbf{I}_1 + j16\mathbf{I}_1 - j8\mathbf{I}_2 - 5\angle 45^\circ &= 0 \\ -(12 - j4)\mathbf{I}_2 - j12\mathbf{I}_2 + j8\mathbf{I}_1 &= 0 \end{aligned}$$

$$\begin{aligned} (8 + j16)\mathbf{I}_1 - j8\mathbf{I}_2 &= 5\angle 45^\circ \\ j8\mathbf{I}_1 - (12 + j8)\mathbf{I}_2 &= 0 \end{aligned}$$

$$\begin{bmatrix} 8 + j16 & -j8 \\ j8 & -12 - j8 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 5\angle 45^\circ \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 0.2795\angle -4.2^\circ \\ 0.155\angle 52.3^\circ \end{bmatrix}$$
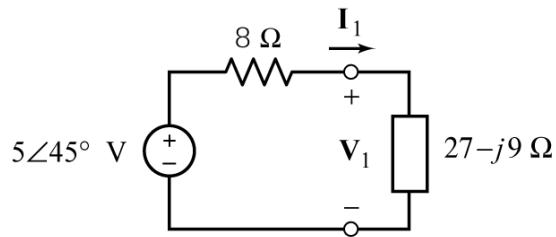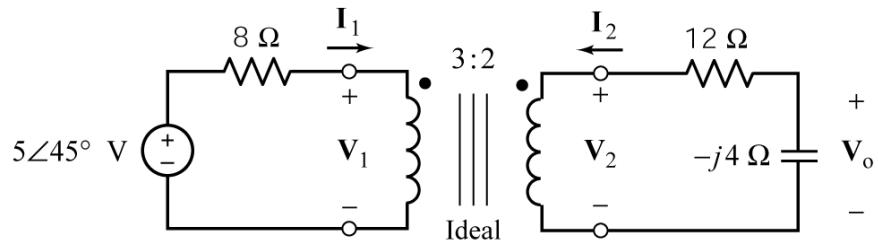
$$\mathbf{V}_o = -(-j4\mathbf{I}_2) = 0.62\angle 142.3^\circ$$



(d)

$$\mathbf{I}_1 = \frac{5\angle 45^\circ}{8 + 27 - j9} = \frac{5\angle 45^\circ}{35 - j9} = \frac{5\angle 45^\circ}{36.1\angle -14.4^\circ} = 0.1385\angle 59.4^\circ \text{ A}$$

$$\mathbf{V}_1 = (27 - j9)\mathbf{I}_1 = (27 - j9)(0.1385\angle 59.4^\circ) = (2.85\angle -18.4^\circ)(0.1385\angle 59.4^\circ) = 3.95\angle 41^\circ \text{ V}$$

$$\mathbf{I}_2 = -\frac{3}{2}\mathbf{I}_1 = (1.5\angle -180^\circ)(0.1385\angle 59.4^\circ) = 0.02078\angle -120.6^\circ \text{ A}$$

$$\mathbf{V}_o = -(-j4\mathbf{I}_2) = 0.835\angle 30.6^\circ$$