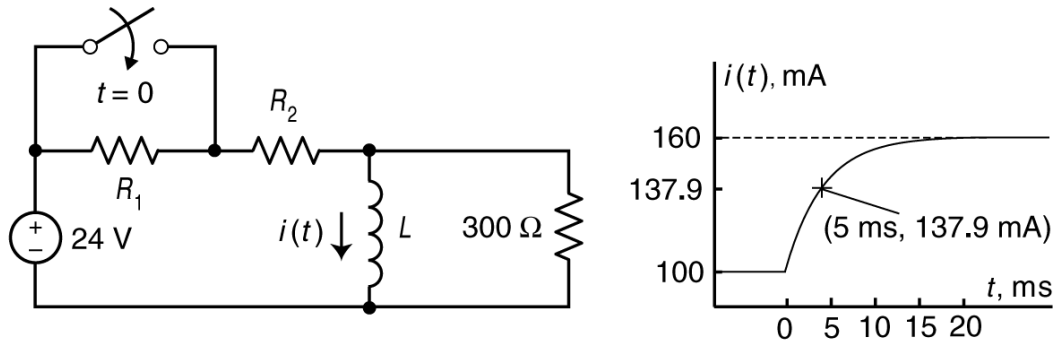


EE221 1st Midterm Exam - Spring 2014

Name _____

Student # _____

1.




Determine the values of R_1 and R_2 .

$$R_1 = \underline{90} \ \Omega \text{ and } R_2 = \underline{150} \ \Omega.$$

b. Determine the value of the time constant, τ , of this circuit after the switch closes: $\tau = \underline{5} \text{ ms}$.

2.

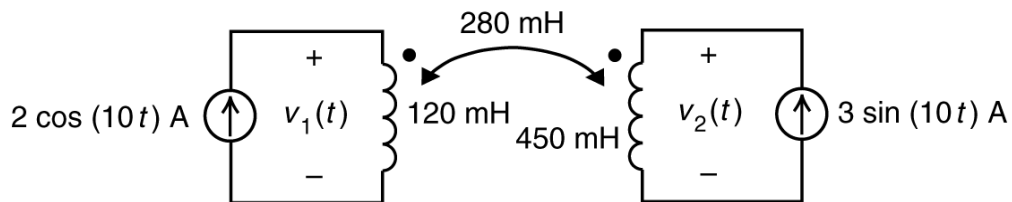

(Recall that $\sin(\omega t) = \cos(\omega t - 90^\circ)$.) The coil voltages in this circuit are $v_1(t) = A \cos(10t + 15.95^\circ)$ V and $v_2(t) = B \cos(10t + 22.53^\circ)$ V. Determine the values of A and B :

$$A = \underline{8.736} \text{ V and } B = \underline{14.615} \text{ V}$$


3. An AC source is connected to a load:

a) Suppose that the voltage source supplies

$$\mathbf{S} = 9.1 \angle 24.49^\circ = 8.2814 + j3.7723 \text{ VA}$$

Determine values of the resistance and inductance.
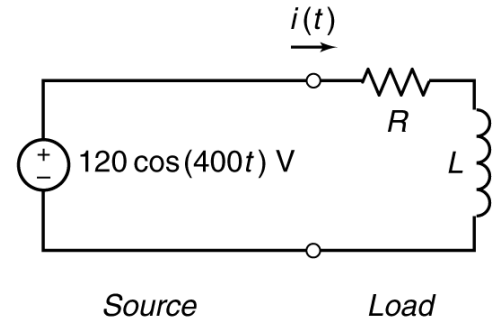
$$R = \underline{\quad 720 \quad} \Omega \quad \text{and} \quad L = \underline{\quad 820 \quad} \text{mH}$$



b) Suppose **instead** that $R = 420 \Omega$ and $L = 800 \text{ mH}$. Determine the power factor of the load:

$$pf = \underline{\quad 0.7954 \quad}$$


c) Suppose **instead** that the voltage source supplies 9.1278 W at a power factor of 0.7962 lagging. Determine the values of the apparent and reactive powers supplied by the source to the load.

$$|\mathbf{S}| = \underline{\quad 11.464 \quad} \text{ VA} \quad \text{and} \quad Q = \underline{\quad 6.936 \quad} \text{ VAR}$$

d) Suppose **instead** that $i(t) = 176.47 \cos(400t - 28.1^\circ) \text{ mA}$. Determine the values of the real and reactive powers supplied by the source to the load.

$$P = \underline{\quad 9.34 \quad} \text{ W} \quad \text{and} \quad Q = \underline{\quad 4.98 \quad} \text{ VAR}$$

4.

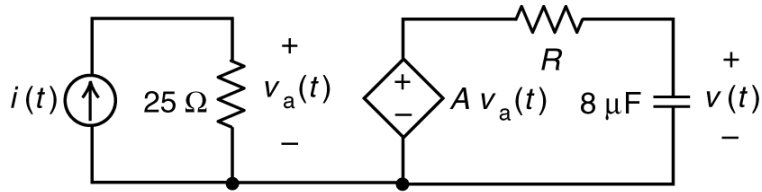

The network function of this circuit is:

$$\mathbf{H}(\omega) = \frac{\mathbf{V}(\omega)}{\mathbf{I}(\omega)} = \frac{450}{1 + j \frac{\omega}{250}}$$


- a) The value of the resistance is $R = \underline{\quad 500 \quad} \Omega$.
- b) The value of the gain of the VCVS is $A = \underline{\quad 18 \quad} \text{V/V}$.
- c) When $\omega = \underline{\quad 433 \quad} \text{rad/sec}$, the value of the gain of the circuit is 225 V/A .
- d) When $\omega = \underline{\quad 144 \quad} \text{rad/sec}$, the value of the phase shift of the circuit is -30° .
- e) When $\omega = 200 \text{ rad/sec}$, the value of the gain of the circuit is $\underline{\quad 351 \quad} \text{V/A}$.
- f) When $\omega = 200 \text{ rad/sec}$, the value of the phase shift of the circuit is $\underline{\quad -38.7 \quad}^\circ$.
- g) At low frequencies the value of the gain of the circuit is $\underline{\quad 450 \quad} \text{V/A}$.
- h) At high frequencies the value of the phase shift of the circuit is $\underline{\quad -90 \quad}^\circ$.
- i) When the input is $i(t) = 180 \cos(300t + 30^\circ) \text{ mA}$ the phase angle of $v(t)$ is $\underline{\quad -20.2 \quad}^\circ$.
- j) When the input is $i(t) = 180 \cos(300t + 30^\circ) \text{ mA}$ the amplitude of $v(t)$ is $\underline{\quad 51.85 \quad} \text{V}$.

5. The current $i(t)$ and voltage $v(t)$ labeled on the circuit drawing are

$$i(t) = A \cos(10t - 23.63^\circ) \text{ Amps}$$


and $v(t) = B \cos(10t - 23.63^\circ) \text{ V}$

Determine the values of A and B :

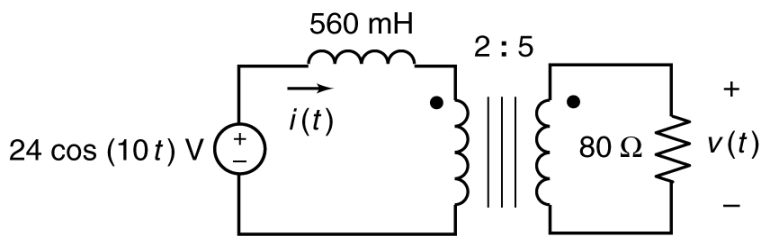

$$A = \underline{\quad 1.718 \quad} \text{ Amps} \quad \text{and} \quad B = \underline{\quad 54.97 \quad} \text{ V}$$

6.

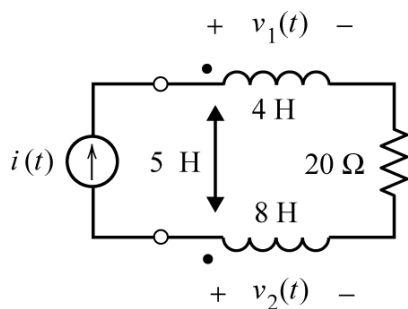

The input current is

$$i(t) = 1.3 \cos(5t) \text{ A}$$


The coil voltages are

$$v_1(t) = E \cos(5t - 90^\circ) \text{ V} \quad \text{and} \quad v_2(t) = F \cos(5t - 90^\circ) \text{ V}$$

Determine the values of E and F .

$$E = \underline{\quad 6.5 \quad} \text{ V} \quad \text{and} \quad F = \underline{\quad 19.5 \quad} \text{ V}$$

7.

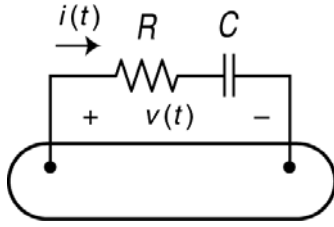


This voltage and current are given by

$$v(t) = 20 \cos(25t + 15^\circ) \text{ V} \quad \text{and} \quad i(t) = 3.05 \cos(25t + 39^\circ) \text{ A}$$

Determine the values of the resistance, R , and capacitance, C .

$$R = \underline{\quad 6 \quad} \Omega \quad \text{and} \quad C = \underline{\quad 15 \quad} \text{mF}$$

QUANTITY	RELATIONSHIP USING PEAK VALUES	RELATIONSHIP USING rms VALUES	UNITS
Element voltage, $v(t)$	$v(t) = V_m \cos(\omega t + \theta_v)$	$v(t) = V_{\text{rms}} \sqrt{2} \cos(\omega t + \theta_v)$	V
Element current, $i(t)$	$i(t) = I_m \cos(\omega t + \theta_i)$	$i(t) = I_{\text{rms}} \sqrt{2} \cos(\omega t + \theta_i)$	A
Complex power, \mathbf{S}	$\mathbf{S} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$ $+ j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$	$\mathbf{S} = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$ $+ j V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$	VA
Apparent power, $ \mathbf{S} $	$ \mathbf{S} = \frac{V_m I_m}{2}$	$ \mathbf{S} = V_{\text{rms}} I_{\text{rms}}$	VA
Average power, P	$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$	$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$	W
Reactive power, Q	$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$	$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)$	VAR

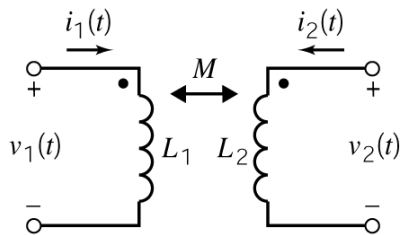


$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$\mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 + j\omega M \mathbf{I}_2$$

$$v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$
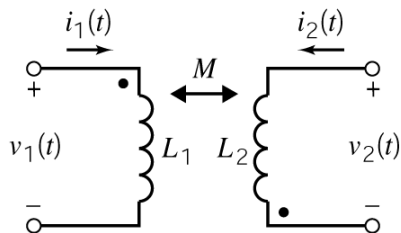
$$\mathbf{V}_2 = j\omega L_2 \mathbf{I}_2 + j\omega M \mathbf{I}_1$$




$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$\mathbf{V}_1 = j\omega L_1 \mathbf{I}_1 - j\omega M \mathbf{I}_2$$


$$v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$
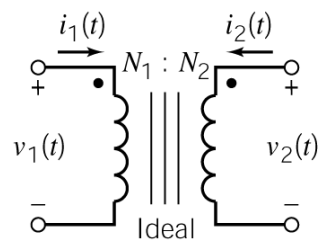
$$\mathbf{V}_2 = j\omega L_2 \mathbf{I}_2 - j\omega M \mathbf{I}_1$$



$$\mathbf{V}_1 = \frac{N_1}{N_2} \mathbf{V}_2$$
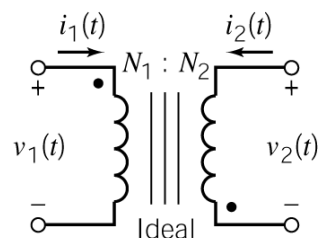
$$\mathbf{I}_1 = -\frac{N_2}{N_1} \mathbf{I}_2$$



$$\mathbf{V}_1 = -\frac{N_1}{N_2} \mathbf{V}_2$$

$$\mathbf{I}_1 = \frac{N_2}{N_1} \mathbf{I}_2$$