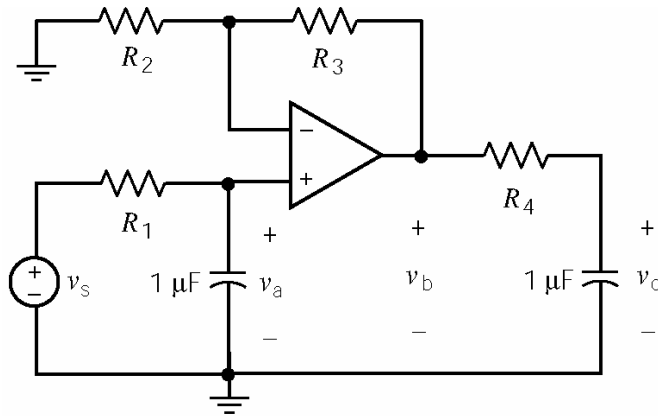


Example:

The input to this circuit is the voltage of the voltage source, v_s . The output of the circuit is the capacitor voltage, v_o .




Determine the values of the resistances R_1 , R_2 , R_3 and R_4 required to cause the network function of the circuit to be

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{21}{\left(1 + j\frac{\omega}{5}\right)\left(1 + j\frac{\omega}{200}\right)}$$

Solution:

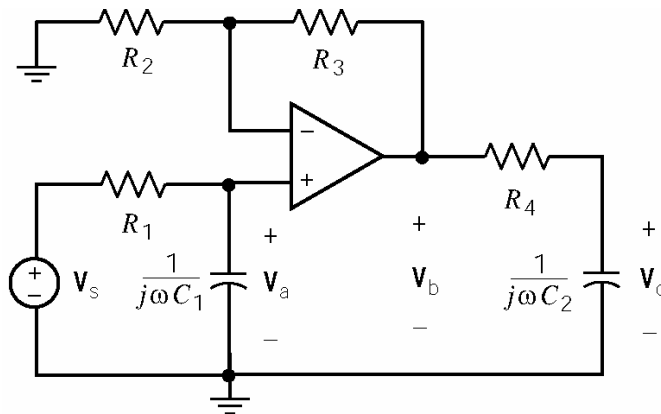Represent the circuit in the frequency domain.



Apply KCL at the top node of the left capacitor, C_1 , to get

$$\frac{\mathbf{V}_a - \mathbf{V}_s}{R_1} + j\omega C_1 \mathbf{V}_a = 0 \Rightarrow \mathbf{V}_a = \frac{1}{1 + j\omega C_1 R_1} \mathbf{V}_s$$

The op amp, together with resistors R_2 and R_3 , comprise a noninverting amplifier so

$$\mathbf{V}_b = \left(1 + \frac{R_3}{R_2}\right) \mathbf{V}_a$$

(Alternately, this equation can be obtained by applying KCL at the inverting input node of the op amp.) Apply KCL at the top node of the right capacitor, C_2 , to get

$$\frac{\mathbf{V}_o - \mathbf{V}_b}{R_4} + j\omega C_2 \mathbf{V}_o = 0 \Rightarrow \mathbf{V}_o = \frac{1}{1 + j\omega C_2 R_4} \mathbf{V}_b$$

Combining these equations gives

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{1 + \frac{R_3}{R_2}}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_4)}$$

Comparing to the specified network function gives

$$\frac{1 + \frac{R_3}{R_2}}{(1 + j\omega C_1 R_1)(1 + j\omega C_2 R_4)} = \frac{21}{\left(1 + j\frac{\omega}{5}\right)\left(1 + j\frac{\omega}{200}\right)}$$

The solution is not unique. For example, we can require


$$1 + \frac{R_3}{R_2} = 21, \quad C_1 R_1 = \frac{1}{5} = 0.2, \quad C_2 R_4 = \frac{1}{200} = 0.005$$

With the given values of capacitance, and choosing $R_2 = 10 \text{ k}\Omega$, we have

$$R_1 = 200 \text{ k}\Omega, \quad R_2 = 10 \text{ k}\Omega, \quad R_3 = 200 \text{ k}\Omega \text{ and } R_4 = 50 \text{ k}\Omega$$

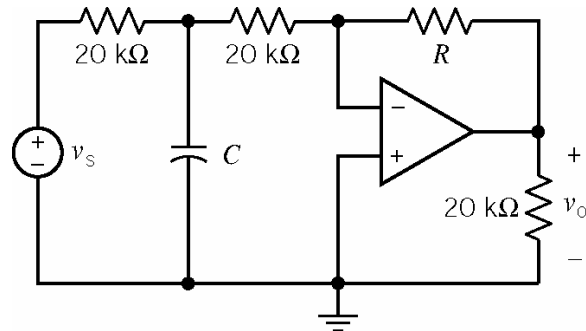Example:

The input to this circuit is the voltage of the voltage source, v_s . The output of the circuit is the resistor voltage, v_o .




Specify values for R and C that cause the network function of the circuit to be

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{-8}{1 + j\frac{\omega}{250}}$$

Solution:

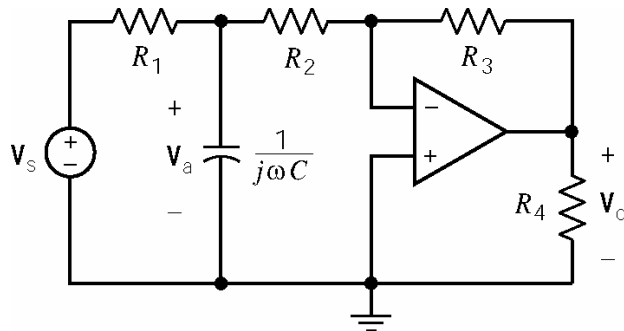Represent the circuit in the frequency domain.



The node equations are

$$\frac{\mathbf{V}_a - \mathbf{V}_s}{R_1} + \frac{\mathbf{V}_a}{\frac{1}{j\omega C}} + \frac{\mathbf{V}_a}{R_2} = 0 \Rightarrow \mathbf{V}_a = \frac{R_2}{R_1 + R_2 + j\omega C R_1 R_2} \mathbf{V}_s$$

and

$$\frac{\mathbf{V}_a}{R_2} + \frac{\mathbf{V}_o}{R_3} = 0 \Rightarrow \mathbf{V}_o = -\frac{R_3}{R_2} \mathbf{V}_a$$

The network function is

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{-\frac{R_3}{R_2} R_2}{R_1 + R_2 + j\omega C R_1 R_2} = \frac{-\frac{R_3}{R_1 + R_2}}{1 + j\omega C \frac{R_1 R_2}{R_1 + R_2}}$$

Using the given values for R_1 and R_2 and letting $R_3 = R$ gives

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{-\frac{R}{4 \times 10^4}}{1 + j\omega C(10^4)}$$


Comparing this network function to the specified network function gives

$$C(10^4) = \frac{1}{250} \Rightarrow C = 0.4 \mu\text{F} \text{ and } \frac{R}{4 \times 10^4} = 8 \Rightarrow R = 320 \text{ k}\Omega$$

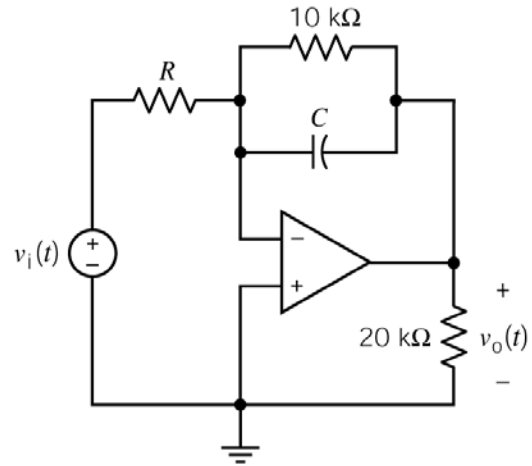Example



Consider this circuit and its frequency response, shown below.

The frequency response plots were made using PSpice and Probe. $V(R3:2)$ and $Vp(R3:2)$ denote the magnitude and angle of the phasor corresponding to $v_o(t)$. $V(V1:~)$ and $Vp(V1:~)$ denote the magnitude and angle of the phasor corresponding to $v_i(t)$. Hence $V(R3:2)/V(V1:~)$ is the gain of the circuit and $Vp(R3:2) - Vp(V1:~)$ is the phase shift of the circuit.



Determine values for R and C required to make the circuit correspond to the frequency response.

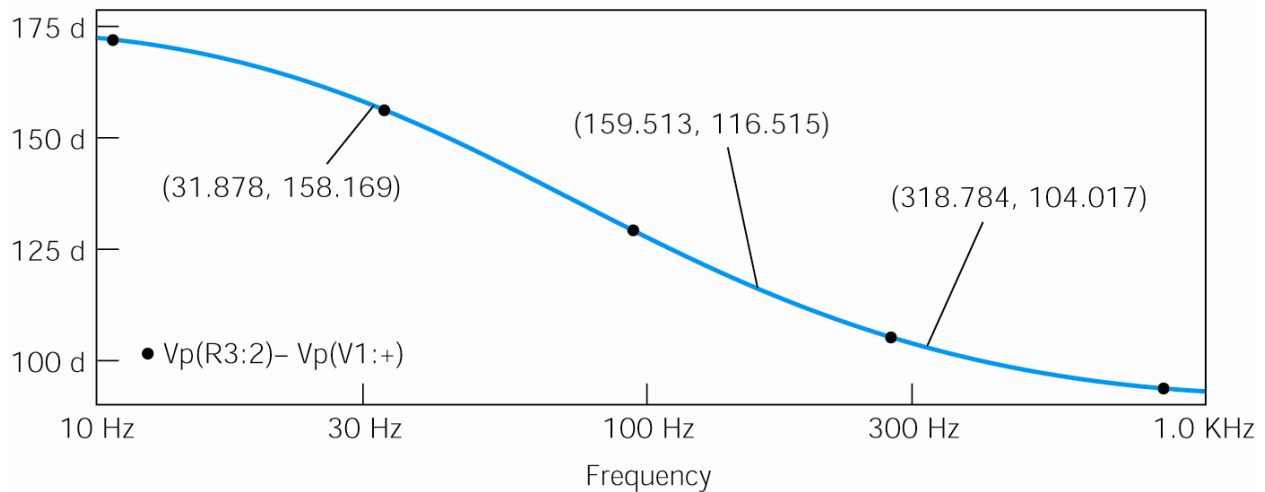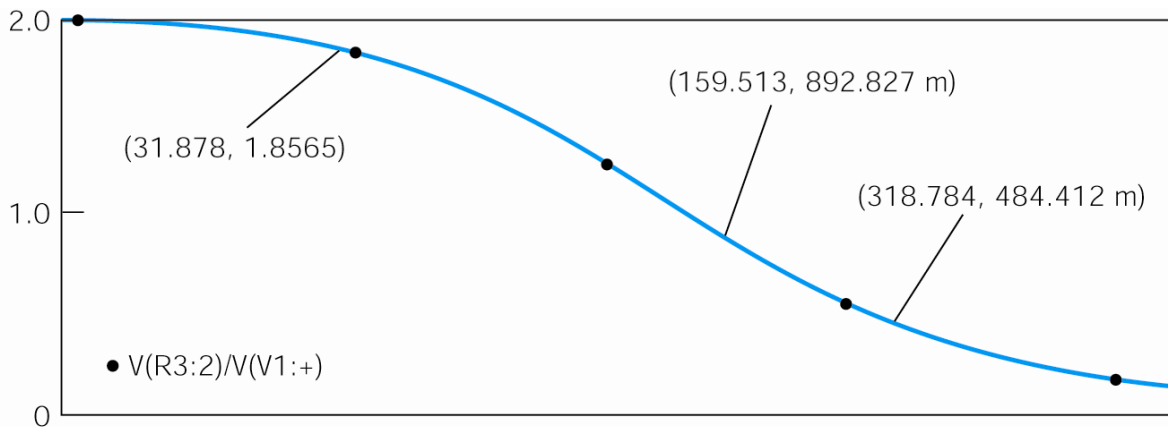Hint: PSpice and Probe use m for milli or 10^{-3} . Hence, the label (159.513, 892.827 m) indicates that the gain of the circuit is $892.827 \times 10^{-3} = 0.892827$ at a frequency of 159.513 Hertz ≈ 1000 rad/sec.



Solution:

$$\mathbf{H}(\omega) = -\frac{\frac{10^4}{R}}{1 + j\omega C 10^4} = \frac{\frac{10^4}{R}}{\sqrt{1 + (\omega C 10^4)^2}} \angle -\tan^{-1}(\omega C 10^4)$$

When $\omega = 200$ rad/sec = 31.83 Hertz

$$1.8565 \angle 158^\circ = \frac{\frac{10^4}{R}}{\sqrt{1 + (\omega C 10^4)^2}} \angle -\tan^{-1}(\omega C 10^4)$$

Equating phase shifts gives

$$\omega C 10^4 = 10^3 \frac{C R 10^4}{R + 10^4} = \tan(22^\circ) = 0.404 \Rightarrow C = 0.2 \mu\text{F}$$

Equating gains gives


$$1.8565 = \frac{\frac{10^4}{R}}{\sqrt{1 + (\omega C 10^4)^2}} = \frac{\frac{10^4}{R}}{\sqrt{1 + (0.404)^2}} \Rightarrow R = 5 \text{ k}\Omega$$

Example:

The input to this circuit is the voltage of the voltage source, v_s . The output of the circuit is the voltage, v_o . Determine the network function,

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)}$$

of the circuit.

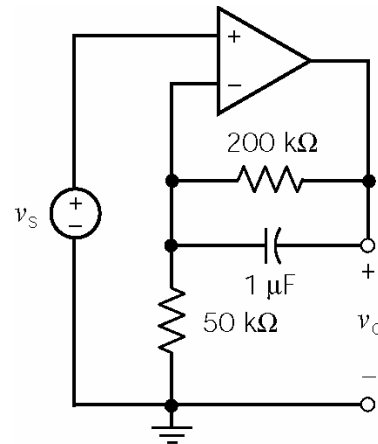**Solution:**

Represent the circuit in the frequency domain. Apply KCL at the inverting input node of the op amp to get


$$\frac{\mathbf{V}_o - \mathbf{V}_s}{R_1} + j\omega C_1 (\mathbf{V}_o - \mathbf{V}_s) + \frac{\mathbf{V}_s}{R_2} = 0$$

or

$$(R_1 + R_2 + j\omega C_1 R_1 R_2) \mathbf{V}_s = (R_2 + j\omega C_1 R_1 R_2) \mathbf{V}_o$$

so
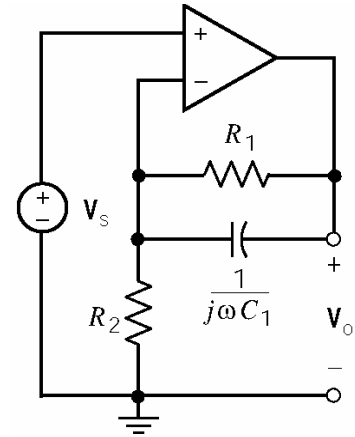
$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{R_1 + R_2 + j\omega C_1 R_1 R_2}{R_2 + j\omega C_1 R_1 R_2} = \frac{R_1 + R_2}{R_2} \times \frac{1 + j\omega C_1 \frac{R_1 R_2}{R_1 + R_2}}{1 + j\omega C_1 R_1}$$



With the given values

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{25 + j\omega}{5 + j\omega} = 5 \frac{1 + j\frac{\omega}{25}}{1 + j\frac{\omega}{5}}$$