
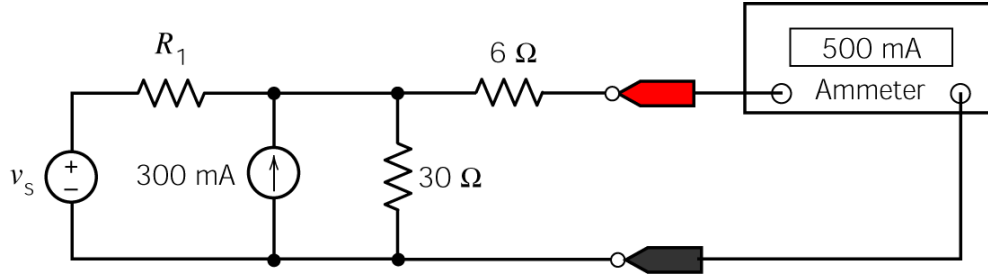



Given

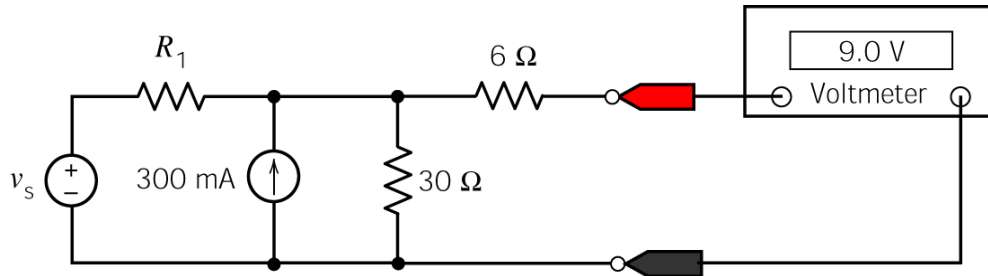

and



Consider

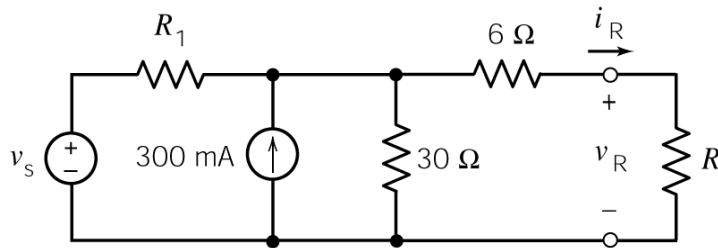

Fill in the blanks in the following statements:


- When  $R = 9 \Omega$  then  $v_R =$  \_\_\_\_\_ V.
- When  $R =$  \_\_\_\_\_  $\Omega$  then  $v_R = 2.52$  V.
- When  $R =$  \_\_\_\_\_  $\Omega$  then  $i_R = 300$  mA.
- $R_1 =$  \_\_\_\_\_  $\Omega$  and  $v_s =$  \_\_\_\_\_ V.

### Solution

Recognize that the ammeter measures the short circuit current and the voltmeter measures the open circuit voltages. Consequently



$$i_{sc} = 500 \text{ mA}, \quad v_{oc} = 9 \text{ V} \quad \text{and} \quad R_t = \frac{v_{oc}}{i_{sc}} = \frac{9}{0.5} = 18 \Omega$$

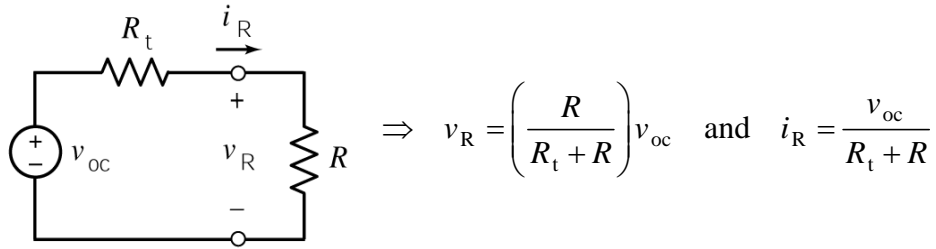Replace the part of the circuit to the left of the terminals by its Thevenin equivalent circuit to get



Using  $v_{oc} = 9 \text{ V}$  and  $R_t = 18 \Omega$  we have  $v_R = \frac{9R}{18+R}$  and  $i_R = \frac{9}{18+R}$ .

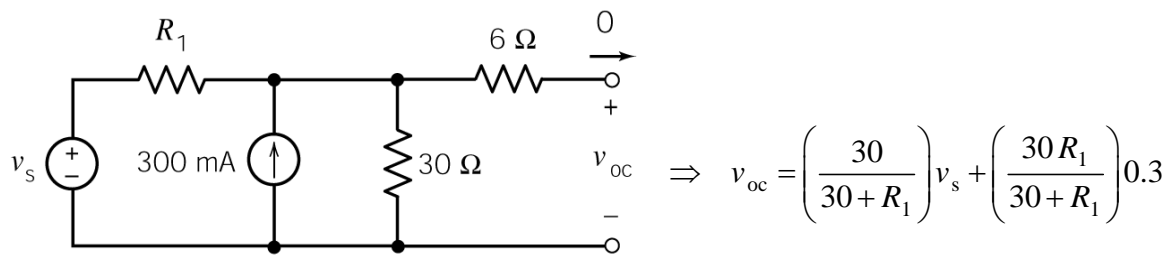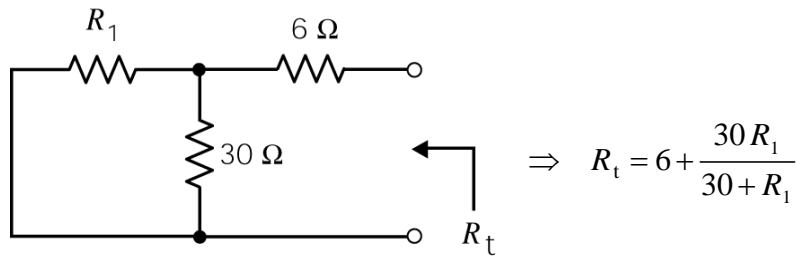- a. When  $R = 9 \Omega$  then  $v_R = \underline{\quad 3 \quad} \text{ V}$ .
- b. When  $R = \underline{\quad 7 \quad} \Omega$  then  $v_R = 2.52 \text{ V}$ .
- c. When  $R = \underline{\quad 9 \quad} \Omega$  then  $i_R = 300 \text{ mA}$ .
- d.



Using  $v_{oc} = 9 \text{ V}$  and  $R_t = 18 \Omega$  we have

$$18 = 6 + \frac{30R_1}{30 + R_1} \Rightarrow R_1 = 20 \Omega$$

$$9 = \left( \frac{30}{30 + R_1} \right) v_s + \left( \frac{30R_1}{30 + R_1} \right) 0.3 = \left( \frac{30}{30 + 20} \right) v_s + \left( \frac{30 \cdot 20}{30 + 20} \right) 0.3 = 0.6v_s + 3.6 \Rightarrow v_s = 9 \text{ V}$$