

## Determining a Thevenin Equivalent Circuit from Measured Data

### Example:


Here's a circuit and some corresponding data. Two resistances,  $R_1$  and  $R$ , and the current source current are unspecified. The tabulated data provides values of the current,  $i$ , and voltage,  $v$ , corresponding to several values of the resistance  $R$ .

(a) Consider replacing the part of the circuit connected to the resistor  $R$  by a Thevenin equivalent circuit. Use the data in rows 2 and 3 of the table to find the values of  $R_t$  and  $v_{oc}$ , the Thevenin resistance and the open circuit voltage.

(b) Use the results of part (a) to verify that the tabulated data is consistent.

(c) Fill in the blanks in the table.

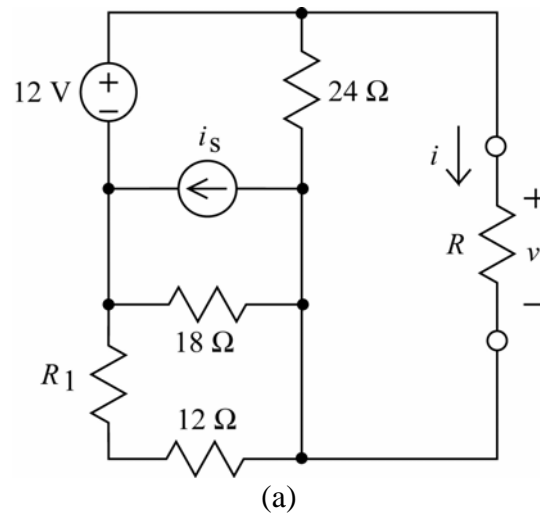(d) Determine the values of  $R_1$  and  $i_s$ .




$R, \Omega$	$i, \text{A}$	$v, \text{V}$
0	3	0
10	1.333	13.33
20	0.857	17.14
40	0.5	?
80	?	21.82

(b)

### Solution

(a)

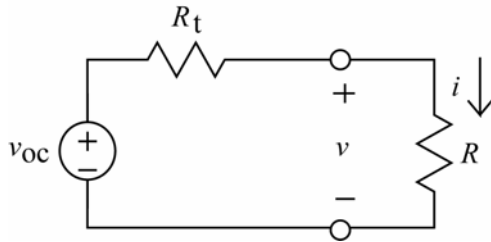

KVL gives

$$v_{oc} = (R_t + R)i$$

from row 2

$$v_{oc} = (R_t + 10)(1.333)$$

from row 3

$$v_{oc} = (R_t + 20)(0.857)$$

So

$$(R_t + 10)(1.333) = (R_t + 20)(0.857)$$

$$28(R_t + 10) = 18(R_t + 20)$$

Solving gives

$$10R_t = 360 - 280 = 80 \Rightarrow R_t = 8 \Omega$$

and

$$v_{oc} = (8 + 10)(1.333) = 24 \text{ V}$$

(b)

$$i = \frac{v_{oc}}{R_t + R} = \frac{24}{8 + R} \quad \text{and} \quad v = \frac{R}{R + R_t} v_{oc} = \frac{24R}{R + 8}$$

When  $R = 0$ ,  $i = 3 \text{ A}$ , and  $v = 0 \text{ V}$ .

When  $R = 40 \Omega$ ,  $i = \frac{1}{2} \text{ A}$ .

When  $R = 80 \Omega$ ,  $v = \frac{24(80)}{88} = \frac{240}{11} = 21.82$ .

These are the values given in the tabulated data so the data is consistent.

(c) When  $R = 40 \Omega$ ,  $v = \frac{24(40)}{48} = 20 \text{ V}$ .

When  $R = 80 \Omega$ ,  $i = \frac{24}{88} = 0.2727 \text{ A}$ .

(d) First

$$8 = R_t = 24 \parallel 18 \parallel (R_t + 12) \Rightarrow R_t = 24 \Omega$$

the, using superposition,

$$24 = v_{oc} = \frac{24}{24 + (18 \parallel (R_t + 12))} 12 + (24 \parallel 18 \parallel (R_t + 12)) i_s = 8 + 8i_s \Rightarrow i_s = 2 \text{ A}$$