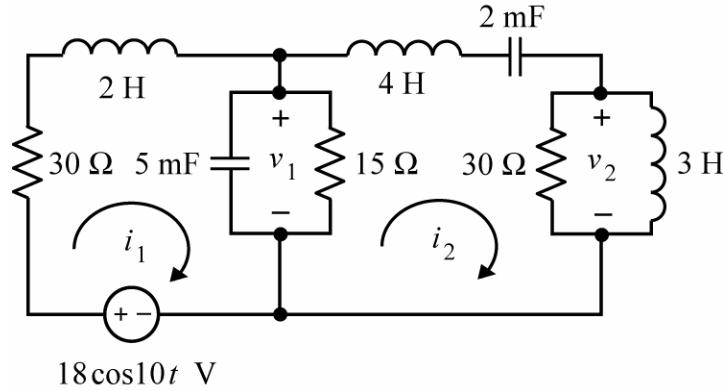


Analysis of AC Circuits

Example 1: Determine the node voltages, $v_1(t)$ and $v_2(t)$, and the mesh currents, $i_1(t)$ and $i_2(t)$, for this circuit.




Example 2: In this circuit, the node voltages are

$$v_1(t) = 3.318 \cos(10t - 39.3^\circ) \text{ V} \text{ and } v_2(t) = 4.452 \cos(10t - 12.7^\circ) \text{ V},$$

and the mesh currents are

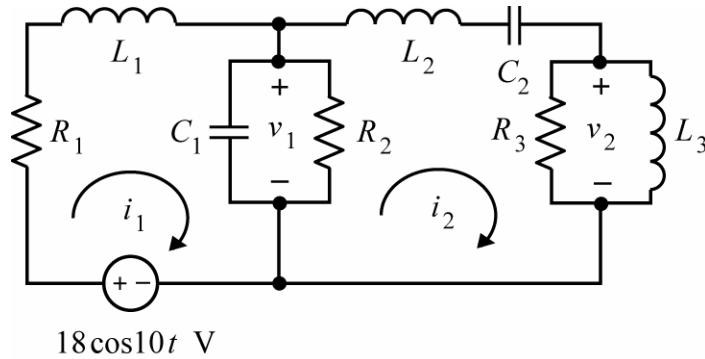
$$i_1(t) = 0.4319 \cos(10t - 25.9^\circ) \text{ A} \text{ and } i_2(t) = 0.2099 \cos(10t - 57.7^\circ) \text{ A}.$$



Determine the values of the resistances, inductances and capacitances.

Solutions

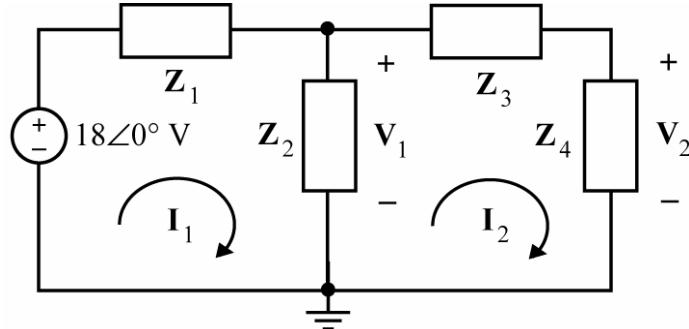Example 1: Represent the circuit in the frequency domain using impedances and phasors:



where

$$\mathbf{Z}_1 = 30 + j(10)(2) = 30 + j20 \Omega, \quad \mathbf{Z}_2 = \frac{15 \frac{1}{j(10)(0.005)}}{15 + \frac{1}{j(10)(0.005)}} = \frac{15(-j20)}{15 - j20} = 9.6 - j7.2 \Omega$$

$$\mathbf{Z}_3 = j(10)(4) + \frac{1}{j(10)(0.002)} = -j10 \Omega \quad \text{and} \quad \mathbf{Z}_4 = \frac{(30)j(10)(3)}{30 + j(10)(3)} = 15 + j15 \Omega$$

The node equations are

$$\frac{18\angle0 - \mathbf{V}_1}{\mathbf{Z}_1} = \frac{\mathbf{V}_1}{\mathbf{Z}_2} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{\mathbf{Z}_3} \Rightarrow (\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_1 \mathbf{Z}_3 + \mathbf{Z}_2 \mathbf{Z}_3) \mathbf{V}_1 - \mathbf{Z}_1 \mathbf{Z}_2 \mathbf{V}_2 = \mathbf{Z}_2 \mathbf{Z}_3 (18\angle0)$$

$$\frac{\mathbf{V}_1 - \mathbf{V}_2}{\mathbf{Z}_3} = \frac{\mathbf{V}_2}{\mathbf{Z}_4} \Rightarrow -\mathbf{Z}_4 \mathbf{V}_1 + (\mathbf{Z}_3 + \mathbf{Z}_4) \mathbf{V}_2 = 0$$

Substituting the values of the impedances and writing the equations in matrix form gives

$$\begin{bmatrix} 560 - j420 & -432 + j24 \\ -15 - j15 & 15 + j5 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} -1296 - j1728 \\ 0 \end{bmatrix}$$

Solving, for example using MATLAB, we get

$$\mathbf{V}_1 = 3.318\angle -39.3^\circ \text{ V} \quad \text{and} \quad \mathbf{V}_2 = 4.452\angle -12.7^\circ \text{ V}$$

Back in the time domain, the node voltages are

$$v_1(t) = 3.318 \cos(10t - 39.3^\circ) \text{ V} \quad \text{and} \quad v_2(t) = 4.452 \cos(10t - 12.7^\circ) \text{ V}$$

The mesh equations are

$$\mathbf{Z}_1 \mathbf{I}_1 + \mathbf{Z}_2 (\mathbf{I}_1 - \mathbf{I}_2) - 18\angle 0^\circ = 0 \Rightarrow (\mathbf{Z}_1 + \mathbf{Z}_2) \mathbf{I}_1 - \mathbf{Z}_2 \mathbf{I}_2 = 18\angle 0^\circ$$

$$\mathbf{Z}_3 \mathbf{I}_2 + \mathbf{Z}_4 \mathbf{I}_2 - \mathbf{Z}_2 (\mathbf{I}_1 - \mathbf{I}_2) = 0 \Rightarrow -\mathbf{Z}_2 \mathbf{I}_1 + (\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{Z}_4) \mathbf{I}_2 = 0$$

Substituting the values of the impedances and writing the equations in matrix form gives

$$\begin{bmatrix} 39.6 - j12.8 & -9.6 + j7.2 \\ -9.6 + j7.2 & 24.6 - j2.2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 18 \\ 0 \end{bmatrix}$$


Solving, for example using MATLAB, we get

$$\mathbf{I}_1 = 0.4319\angle -25.9^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_2 = 0.2099\angle -57.7^\circ \text{ A}$$

Back in the time domain, the mesh currents are

$$i_1(t) = 0.4319 \cos(10t - 25.9^\circ) \text{ A} \quad \text{and} \quad i_2(t) = 0.2099 \cos(10t - 57.7^\circ) \text{ A}$$

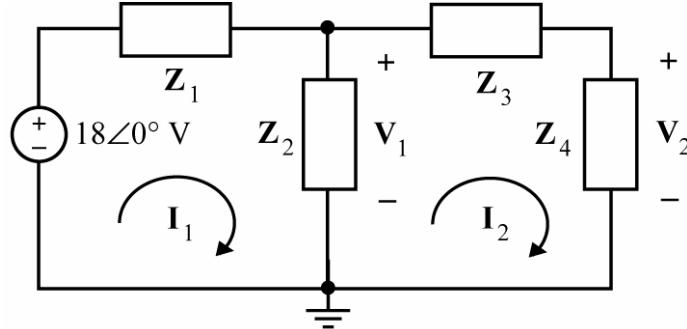Example 2: Represent the circuit in the frequency domain using impedances and phasors:



where

$$\mathbf{Z}_1 = R_1 + j\omega L_1, \quad \frac{1}{\mathbf{Z}_2} = \mathbf{Y}_2 = \frac{1}{R_2} + j\omega C_1$$

$$\mathbf{Z}_3 = j\omega L_2 + \frac{1}{j\omega C_2} = j\left(\omega L_2 - \frac{1}{\omega C_2}\right) \quad \text{and} \quad \frac{1}{\mathbf{Z}_4} = \mathbf{Y}_4 = \frac{1}{R_3} + \frac{1}{j\omega L_3} = \frac{1}{R_3} - j\frac{1}{\omega L_3}$$

and where

$$\mathbf{V}_1 = 3.318\angle -39.3^\circ \text{ V}, \quad \mathbf{V}_2 = 4.452\angle -12.7^\circ \text{ V}$$

$$\mathbf{I}_1 = 0.4319\angle -25.9^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_2 = 0.2099\angle -57.7^\circ \text{ A}$$

Recalling that $\omega = 10 \text{ rad/s}$, we have

$$R_1 + j10L_1 = \mathbf{Z}_1 = \frac{18\angle 0^\circ - \mathbf{V}_1}{\mathbf{I}_1} = \frac{18\angle 0^\circ - 3.318\angle -39.3^\circ}{0.4319\angle -25.9^\circ} = 30 + j20 \Omega$$

$$\frac{1}{R_2} + j10C_1 = \mathbf{Y}_2 = \frac{\mathbf{V}_2}{\mathbf{I}_1 - \mathbf{I}_2} = \frac{4.452\angle -12.7^\circ}{0.4319\angle -25.9^\circ - 0.2099\angle -57.7^\circ} = 0.0667 + j0.05 \text{ S}$$

$$j \left(10L_2 - \frac{1}{10C_2} \right) = \mathbf{Z}_3 = \frac{\mathbf{V}_1 - \mathbf{V}_2}{\mathbf{I}_2} = \frac{3.318\angle -39.3^\circ - 4.452\angle -12.7^\circ}{0.2099\angle -57.7^\circ} = -j10 \Omega$$

Consequently:

$$\frac{1}{R_3} - j \frac{1}{10L_3} = \mathbf{Y}_4 = \frac{\mathbf{I}_2}{\mathbf{V}_2} = \frac{0.2099\angle -57.7^\circ}{4.452\angle -12.7^\circ} = 0.0333 - j0.0333 \text{ S}$$

$$R_1 = 30 \Omega, L_1 = \frac{20}{10} = 2 \text{ H}, R_2 = \frac{1}{0.0667} = 15 \Omega, C_1 = \frac{0.05}{10} = 5 \text{ mF},$$

$$10L_2 - \frac{1}{10C_2} = -10 \Rightarrow L_2 + 1 = \frac{1}{100C_2}, \text{ e.g. } C_2 = 2 \text{ mF and } L_2 = \frac{1}{100(0.002)} - 1 = 4 \text{ H},$$

$$R_3 = \frac{1}{0.0333} = 30 \Omega \quad \text{and} \quad L_3 = \frac{1}{(10)0.0333} = 3 \text{ H}$$