
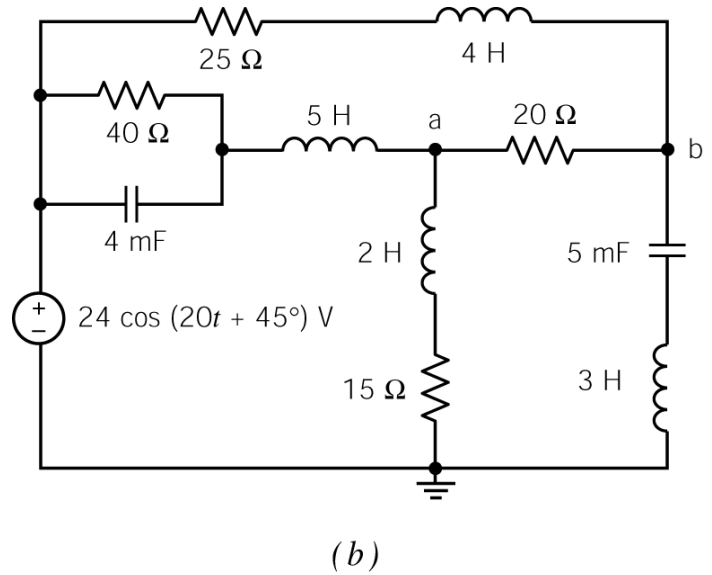


Analyzing AC Circuits by Analogy with DC Circuits

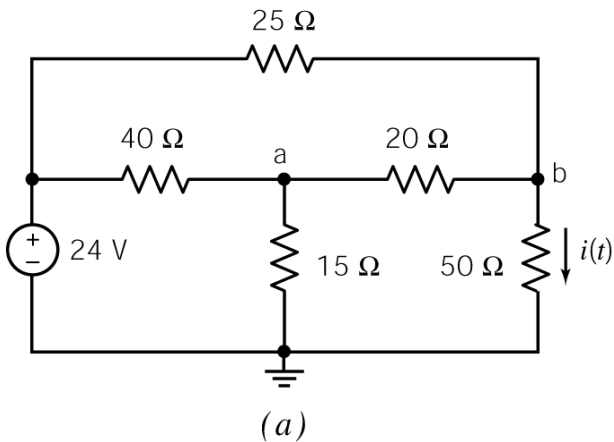Determine the node voltages of these two circuits.



Solution

(a) The node equations are

$$\frac{24 - v_a}{40} = \frac{v_a - v_b}{20} + \frac{v_a}{15}$$

$$\frac{24 - v_b}{25} + \frac{v_a - v_b}{20} = \frac{v_b}{50}$$


or

$$\begin{bmatrix} \frac{1}{40} + \frac{1}{20} + \frac{1}{15} & -\frac{1}{20} \\ -\frac{1}{20} & \frac{1}{25} + \frac{1}{20} + \frac{1}{50} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} \frac{24}{40} \\ \frac{24}{25} \end{bmatrix}$$

Solving using MATLAB gives

$$v_a = 8.713 \text{ V} \quad \text{and} \quad v_b = 12.69 \text{ V}$$

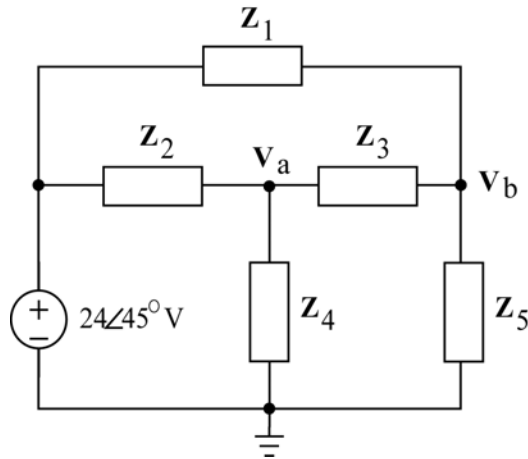(b) Use phasors and impedances to represent the circuit in the frequency domain as



where

$$\mathbf{Z}_1 = 25 + j(20)4 = 25 + j80 = 83.82\angle 72.7^\circ \Omega$$

$$\mathbf{Z}_2 = \left(40 \parallel \frac{1}{j(20)(0.004)} \right) + j(20)5 = 3.56 + j88.6 = 88.68\angle 87.7^\circ \Omega$$

$$\mathbf{Z}_3 = 20 \Omega$$

$$\mathbf{Z}_4 = 15 + j(20)2 = 15 + j40 = 42.72\angle 69.4^\circ$$

$$\mathbf{Z}_5 = j(20)3 + \frac{1}{j(20)(0.005)} = j50 = 50\angle 90^\circ \Omega$$

The node equations are

$$\frac{24\angle 45^\circ - \mathbf{V}_a}{\mathbf{Z}_2} = \frac{\mathbf{V}_a}{\mathbf{Z}_4} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3}$$

$$\frac{24\angle 45^\circ - \mathbf{V}_b}{\mathbf{Z}_1} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3} = \frac{\mathbf{V}_b}{\mathbf{Z}_5}$$

$$\begin{bmatrix} \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} + \frac{1}{\mathbf{Z}_4} & -\frac{1}{\mathbf{Z}_3} \\ -\frac{1}{\mathbf{Z}_3} & \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_3} + \frac{1}{\mathbf{Z}_5} \end{bmatrix} \begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \end{bmatrix} = \begin{bmatrix} \frac{24\angle 45^\circ}{\mathbf{Z}_2} \\ \frac{24\angle 45^\circ}{\mathbf{Z}_1} \end{bmatrix}$$

Solving using MATLAB gives

$$\mathbf{V}_a = 7.89\angle 44.0^\circ$$

$$\mathbf{V}_b = 8.45\angle 45.1^\circ$$

so

$$v_a(t) = 7.89 \cos(20t + 44^\circ) \text{ V}$$

$$v_b(t) = 8.45 \cos(20t + 45.1^\circ) \text{ V}$$

MATLAB

The dc Circuit

```
>> A = [1/40 + 1/20 + 1/15      -1/20;  
        -1/20                1/25 + 1/20 + 1/50];  
>> b = [24/40; 24/25];  
>> v=A\b
```

v =

```
8.7134  
12.6879
```

The ac Circuit

```
>> Z1 = 25 + j*20*4;  
>> Z2 = 88.7*exp(j*87.7*pi/180);  
>> Z3 = 20;  
>> Z4 = 15 + j*20*2;  
>> Z5 = j*20*3 + 1/j/20/0.005;  
>> A = [1/Z2 + 1/Z3 + 1/Z4      -1/Z3;  
        -1/Z3                1/Z1 + 1/Z3 + 1/Z5];  
>> b = [24*exp(j*45*pi/180)/Z2; 24*exp(j*45*pi/180)/Z1];  
>> v = A\b;  
>> abs(v)
```

ans =

```
7.8877  
8.9481
```

```
>> angle(v)*180/pi
```

ans =

```
44.0246  
45.1001
```