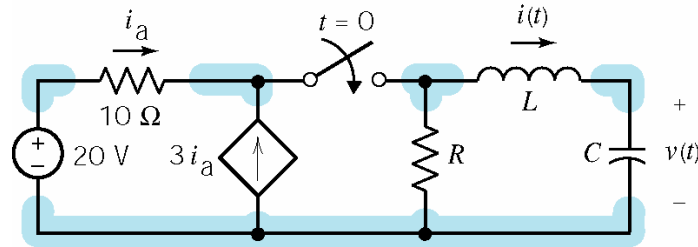


## Interpreting circuit diagrams:

An **electric circuit** is an interconnection of electric **circuit elements**. (Circuit elements are also called **devices**, **components** or **branches**.)

Each circuit element has at least two **terminals**, i.e. places where that element can be connected to other circuit elements. (Terminals are sometimes called **leads**.) The parts of the circuit where terminals are connected together are called **nodes**. (Nodes are also called vertices.)



This circuit is an interconnection of two terminal elements.



The **shape** of the element indicates its behavior.

Each element is characterized by a **parameter**, represented either as a value with units or as a variable.

Each element has two terminals that are connected to nodes of the network. The element is said to be **incident** to the nodes at which its terminals are connected.
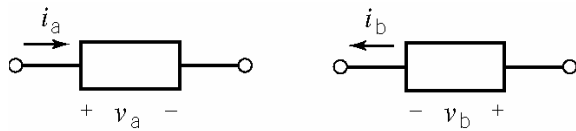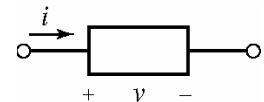
## Charge, current and voltage.

Two quantities are identified for each two-terminal circuit element: the element current and the element voltage.



$$v_b = -v_a \quad \text{and} \quad i_b = -i_a$$

Current and voltage each have a direction as well as value. The direction is constrained by the circuit element so there are only two possible directions. Changing the direction corresponds to multiplying the value by  $-1$ .

## Power and Energy

$$p = v i \quad \text{and} \quad w = \int p dt$$

