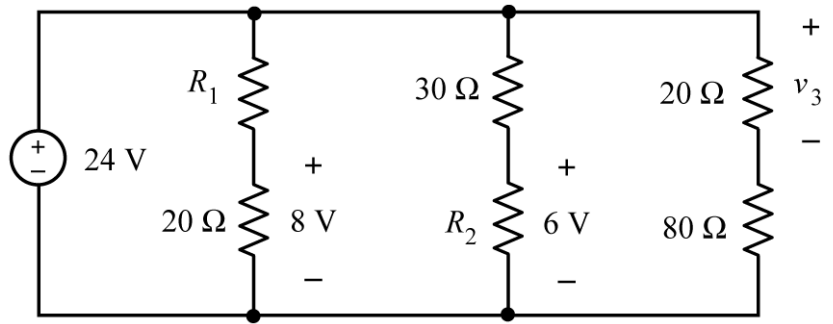


1. Determine the values of R_1 , R_2 and v_3 :

$$R_1 = \underline{40} \Omega$$

$$R_2 = \underline{10} \Omega$$

$$v_3 = \underline{4.8} \text{ V}$$



$$8 = \left(\frac{20}{R_1 + 20} \right) 24 \Rightarrow R_1 + 20 = \frac{20(24)}{8} = 60 \Rightarrow R_1 = 40 \Omega$$

$$6 = \left(\frac{R_2}{R_2 + 30} \right) 24 \Rightarrow R_2 + 30 = \frac{24R_2}{6} = 4R_2 \Rightarrow R_2 = 10 \Omega$$


$$v_3 = \left(\frac{20}{20 + 80} \right) 24 = 4.8 \text{ V}$$

2. Determine the values of Z_1 , Z_2 and V_3 :

$$Z_1 = \underline{20.1 - j 0.2} \Omega$$

$$Z_2 = \underline{10 + j 30} \Omega$$
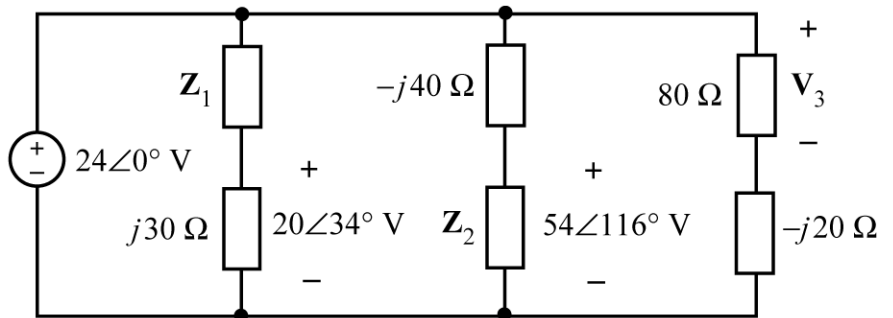
$$V_3 = \underline{23.3 \angle 14^\circ} \text{ V}$$



$$20 \angle 34^\circ = \left(\frac{j 30}{Z_1 + j 30} \right) 24 \angle 0^\circ \Rightarrow Z_1 + j 30 = \frac{j 30(24 \angle 0^\circ)}{20 \angle 34^\circ} = 20.1 + j 29.8 \Rightarrow Z_1 = 20.1 - j 0.2 \Omega$$

$$54 \angle 116^\circ = \left(\frac{Z_2}{Z_2 - j 40} \right) 24 \angle 0^\circ \Rightarrow Z_2 - j 40 = \frac{(24 \angle 0^\circ) Z_2}{54 \angle 116^\circ} \Rightarrow -j 40 = \left(\frac{24 \angle 0^\circ}{54 \angle 116^\circ} - 1 \right) Z_2$$

$$\Rightarrow Z_2 = 10 + j 30.1 \Omega$$

$$V_3 = \left(\frac{80}{80 - j 20} \right) 24 \angle 0^\circ = 23.3 \angle 14^\circ \text{ V}$$