
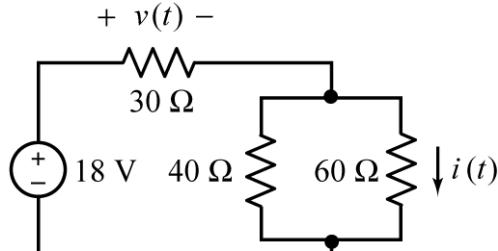


Voltage and Current Division in DC and AC Circuits

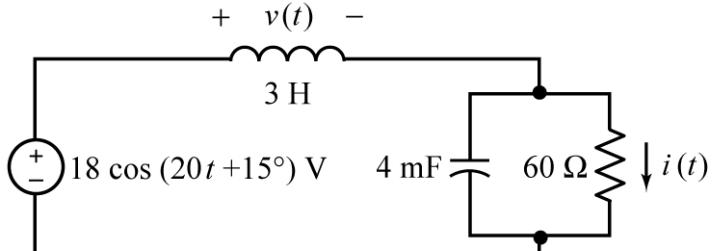Example 1. Determine the steady state voltage, $v(t)$, and current, $i(t)$, for each of these circuits.




(a)




(b)

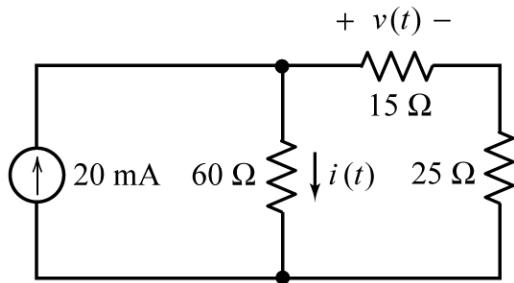Example 2. Determine the steady state voltage, $v(t)$, and current, $i(t)$, for each of these circuits.



(a)

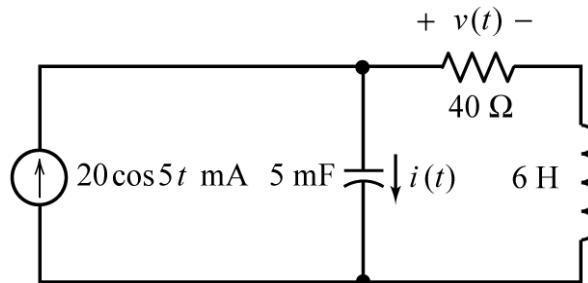

(b)

Solutions


Example 1.

(a)

$$v(t) = \frac{30}{30 + (40 \parallel 60)} \times 18 = 10 \text{ V}$$

$$i(t) = \frac{40}{40+60} \times \frac{18}{30 + (40 \parallel 60)} = \frac{4}{30} = 133 \text{ mA}$$

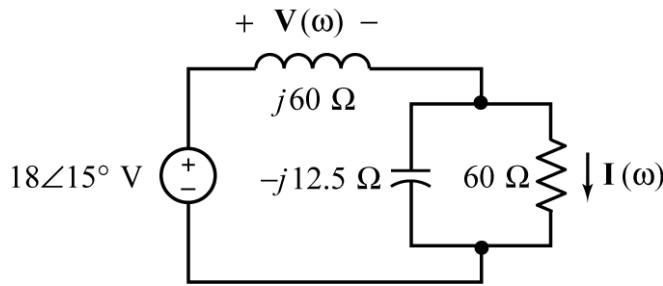(b) Represent the circuit in the frequency domain using impedances and phasors.



$$\mathbf{V}(\omega) = -\frac{j60}{j60 + (-j12.5 \parallel 60)} \times 18\angle 15^\circ = \frac{(60\angle -90^\circ)(18\angle 15^\circ)}{j60 + \frac{60(-j12.5)}{60 - j12.5}} = 22.46\angle 18^\circ \text{ V}$$

$$\mathbf{I}(\omega) = \frac{-j12.5}{60 - j12.5} \times \frac{24\angle 15^\circ}{j60 + \frac{60(-j12.5)}{60 - j12.5}} = 76.35\angle -150^\circ \text{ mA}$$

so

$$v(t) = 22.46 \cos(20t + 18^\circ) \text{ V}$$

and

$$i(t) = 76.35 \cos(20t - 150^\circ) \text{ mA}$$


Example 2.

(a)

$$i(t) = \frac{15 + 25}{60 + (15 + 25)} 0.020 = 0.008 = 8 \text{ mA}$$

$$v(t) = \frac{15}{15 + 25} \times (60 \parallel (15 + 25)) 0.020 = \frac{3}{8}(24)(0.020) = 0.18 \text{ V}$$

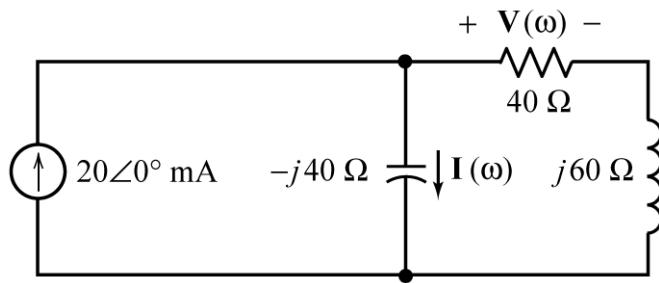(b) Represent the circuit in the frequency domain using impedances and phasors.



$$\mathbf{I}(\omega) = \frac{40 + j60}{-j40 + (40 + j60)} \times 0.020\angle 0^\circ = 24.25\angle 50.9^\circ \text{ mA}$$

and

$$\mathbf{V}(\omega) = \frac{40}{40 + j60} \times [-j40 \parallel (40 + j60)] \times 0.02\angle 0^\circ = 0.97\angle -39^\circ \text{ V}$$

Returning to the time domain:

$$i(t) = 24.25 \cos(5t + 50.9^\circ) \text{ mA}$$

and

$$v(t) = 0.97 \cos(5t - 39^\circ) \text{ V}$$