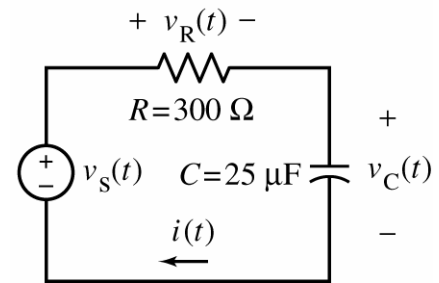


Analysis of AC Circuits

Let's represent this circuit by a differential equation. First,

$i(t) = C \frac{d}{dt} v_C(t)$. Then KVL gives

$$v_s(t) = RC \frac{d}{dt} v_C(t) + v_C(t) = 0.0075 \frac{d}{dt} v_C(t) + v_C(t)$$



When the source voltage is $v_s(t) = 25 \cos(100t + 15^\circ)$ V

we expect $v_C(t) = A \cos(100t + \theta)$

Substituting into the differential equation, we get

$$\begin{aligned} 25 \cos(100t + 15^\circ) &= 0.0075 \frac{d}{dt} [A \cos(100t + \theta)] + A \cos(100t + \theta) \\ &= 0.0075 (100) A [-\sin(100t + \theta)] + A \cos(100t + \theta) \\ &= -0.75 A \sin(100t + \theta) + A \cos(100t + \theta) \end{aligned}$$

Solution using trigonometry:

Recall that $\cos(\alpha \pm \beta) = \cos(\alpha)\cos(\beta) \mp \sin(\alpha)\sin(\beta)$

and $\sin(\alpha \pm \beta) = \sin(\alpha)\cos(\beta) \pm \cos(\alpha)\sin(\beta)$

so

$$\begin{aligned} &[25 \cos(15^\circ)] \cos(100t) - [25 \sin(15^\circ)] \sin(100t) \\ &= -0.75 A [\sin(\theta) \cos(100t) + \cos(\theta) \sin(100t)] + A [\cos(\theta) \cos(100t) + \sin(\theta) \sin(100t)] \\ &= A [(-0.75 \sin(\theta) + \cos(\theta)) \cos(100t) - (-0.75 \cos(\theta) + \sin(\theta)) \sin(100t)] \end{aligned}$$

Equating the coefficients of $\cos(100t)$ and $\sin(100t)$ gives

$$\left. \begin{aligned} 25 \cos(15^\circ) &= A(-0.75 \sin(\theta) + \cos(\theta)) \\ -25 \sin(15^\circ) &= -A(0.75 \cos(\theta) + \sin(\theta)) \end{aligned} \right\} \Rightarrow A = 20 \text{ V and } \theta = -22^\circ$$

That is $v_C(t) = 20 \cos(100t - 22^\circ)$ V

Solution using Euler's identity:

Euler's identity is: $e^{j\theta} = \cos \theta + j \sin \theta \Rightarrow \cos \theta = \operatorname{Re}\{e^{j\theta}\}$

Using $-\sin(\theta) = \cos(\theta + 90^\circ)$, we can write the differential equation as

$$25 \cos(100t + 15^\circ) = 0.75 A [\cos(100t + \theta + 90^\circ)] + A \cos(100t + \theta)$$

Using Euler's identity

$$\operatorname{Re}\{25 e^{j100t+15^\circ}\} = 0.75 A \operatorname{Re}\{e^{j100t+\theta+90^\circ}\} + A \operatorname{Re}\{e^{j100t+\theta}\}$$

$$\begin{aligned} \operatorname{Re}\{25 e^{j100t} e^{j15^\circ}\} &= 0.75 A \operatorname{Re}\{e^{j100t} e^{j\theta} e^{j90^\circ}\} + A \operatorname{Re}\{e^{j100t} e^{j\theta}\} \\ &= \operatorname{Re}\{0.75 A e^{j100t} e^{j\theta} e^{j90^\circ} + A e^{j100t} e^{j\theta}\} \end{aligned}$$

Notice that $e^{j90^\circ} = \cos 90^\circ + j \sin 90^\circ = 0 + j = j$. Consequently

$$\begin{aligned} \operatorname{Re}\{25 e^{j15^\circ} e^{j100t}\} &= \operatorname{Re}\{j 0.75 e^{j\theta} A e^{j100t} + e^{j\theta} A e^{j100t}\} \\ &= \operatorname{Re}\{(j 0.75 e^{j\theta} + e^{j\theta}) A e^{j100t}\} \\ &= \operatorname{Re}\{(1 + j 0.75) A e^{j\theta} e^{j100t}\} \end{aligned}$$

In order for this to be true at all times, it is necessary and sufficient that

$$25 e^{j15^\circ} = (1 + j 0.75) A e^{j\theta}$$

That is

$$A e^{j\theta} = \frac{25 e^{j15^\circ}}{1 + j 0.75} = \frac{25 e^{j15^\circ}}{1.25 e^{j37^\circ}} = 20 e^{-j22^\circ} \text{ V}$$

Hence

$$A = 20 \text{ V} \quad \text{and} \quad \theta = -22^\circ$$

As before

$$v_c(t) = 20 \cos(100t - 22^\circ) \text{ V}$$

Solution using phasors:

Associate the complex number $A\angle\theta$ with the sinusoid $A\cos(\omega t + \theta)$. That is

$$A\cos(\omega t + \theta) \Leftrightarrow A\angle\theta$$

We say that $A\angle\theta$ is the phasor corresponding to $A\cos(\omega t + \theta)$. Using phasors we can transform the differential equation

$$25\cos(100t + 15^\circ) = 0.75 A [\cos(100t + \theta + 90^\circ)] + A\cos(100t + \theta)$$

into
$$25\angle 15^\circ = j0.75 A\angle(\theta + 90^\circ) + A\angle\theta$$

Using $1\angle 90^\circ = j$

$$25\angle 15^\circ = (1 + j0.75)A\angle\theta \Rightarrow A\angle\theta = \frac{25\angle 15^\circ}{1 + j0.75} = \frac{25\angle 15^\circ}{1.25\angle 37^\circ} = 20\angle -22^\circ \text{ V}$$

Hence
$$A = 20 \text{ V} \text{ and } \theta = -22^\circ$$

As before
$$v_C(t) = 20\cos(100t - 22^\circ) \text{ V}$$


Solution using phasors and impedances:

Consider the capacitor. When the voltage is

$$v_C(t) = A\cos(\omega t + \theta)$$

The current is
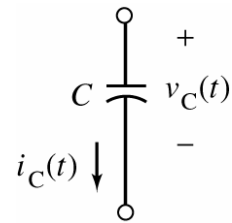
$$i_C(t) = C \frac{d}{dt} v_C(t) = -C\omega A \sin(\omega t + \theta) = C\omega A \cos(\omega t + \theta + 90^\circ)$$




Denote the corresponding phasors as

$$\mathbf{V}_C(\omega) = A\angle\theta \text{ V} \text{ and } \mathbf{I}_C(\omega) = C\omega A\angle(\theta + 90^\circ) = j\omega C A\angle\theta \text{ A}$$

Define the impedance of the element to be the ratio of the voltage phasor to the current phasor:
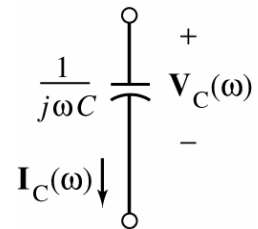
$$\mathbf{Z}_C(\omega) = \frac{\mathbf{V}_C(\omega)}{\mathbf{I}_C(\omega)} = \frac{A\angle\theta}{j\omega C A\angle\theta} = \frac{1}{j\omega C} \Omega$$




Consider the resistor. When the voltage is

$$v_R(t) = A \cos(\omega t + \theta)$$


The current is
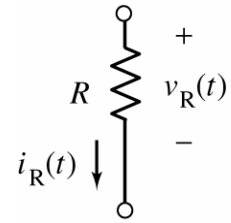
$$i_R(t) = \frac{v_R(t)}{R} = \frac{A}{R} \cos(\omega t + \theta)$$



The impedance of the resistor is the ratio of the voltage phasor to the current phasor:
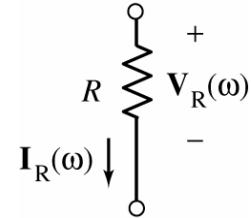
$$\mathbf{Z}_R(\omega) = \frac{\mathbf{V}_R(\omega)}{\mathbf{I}_R(\omega)} = \frac{A \angle \theta}{\frac{A}{R} \angle \theta} = R \ \Omega$$




(The impedance is numerically equal to the resistance.)

In the present case, $\mathbf{Z}_R(\omega) = 300 \ \Omega$ and $\mathbf{Z}_C(\omega) = \frac{1}{j\omega C} = \frac{1}{j100(25 \times 10^{-6})} = -j400 \ \Omega$.

Consider this circuit in which the source is labeled using the phasor and the resistor and capacitor are labeled using impedances.

Notice that $\mathbf{V}_R(\omega) = \mathbf{Z}_R(\omega) \mathbf{I}(\omega)$ and $\mathbf{V}_C(\omega) = \mathbf{Z}_C(\omega) \mathbf{I}(\omega)$ and apply KVL to get
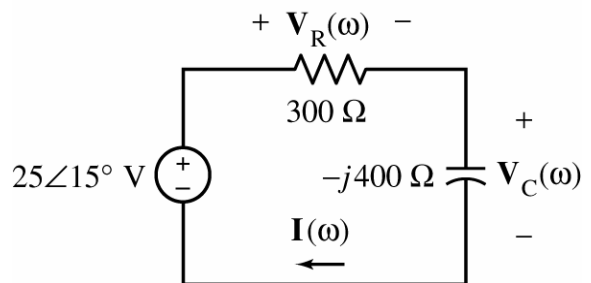
$$25 \angle 15^\circ = 300 \mathbf{I}(\omega) - 400 \mathbf{I}(\omega)$$



Solve for the phasor current:

$$\mathbf{I}(\omega) = \frac{25 \angle 15^\circ}{300 - j400} = \frac{25 \angle 15^\circ}{500 \angle -53^\circ} = 0.05 \angle 68^\circ \text{ A}$$

Using $\mathbf{V}_C(\omega) = \mathbf{Z}_C(\omega) \mathbf{I}(\omega)$ gives:

$$\mathbf{V}_C(\omega) = -j400 (0.05 \angle 68^\circ) = (400 \angle -90^\circ)(0.05 \angle 68^\circ) = 20 \angle -22^\circ \text{ V}$$

The sinusoid corresponding to this phasor is

$$v_C(t) = 20 \cos(100t - 22^\circ) \text{ V}$$

as before.