



Sinusoids and Complex Numbers

The input to this circuit is the voltage source voltage, $v_s(t)$.

The output is the voltage across the capacitor, $v_c(t)$. The input and output are the sinusoids shown below. We expect

$$v_s(t) = A \cos(\omega t + \theta) \quad \text{and} \quad v_c(t) = B \cos(\omega t + \phi)$$

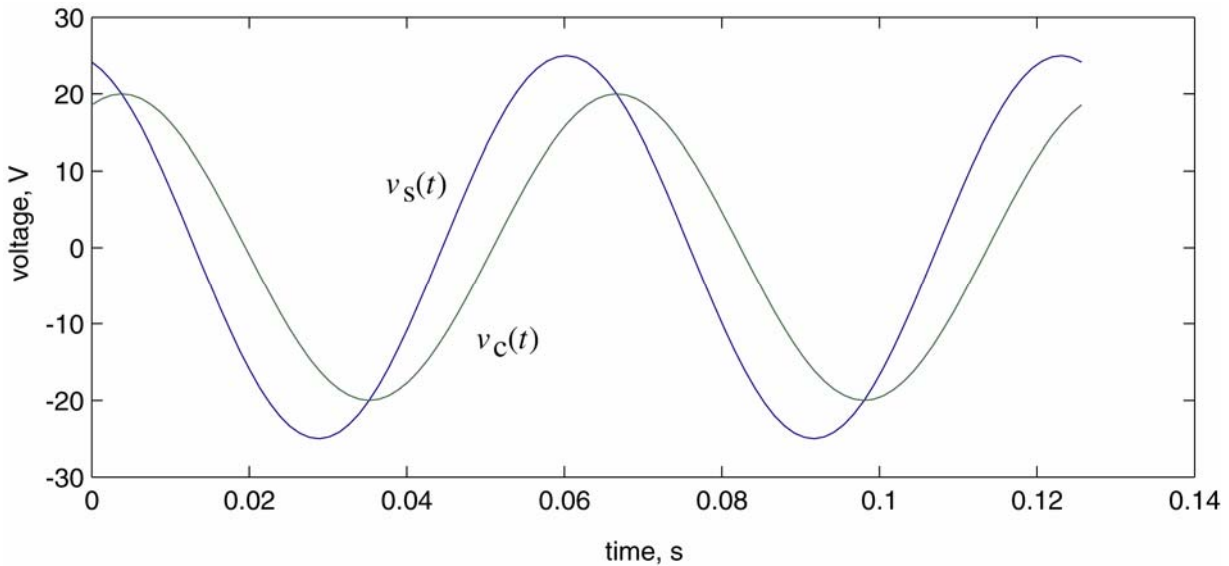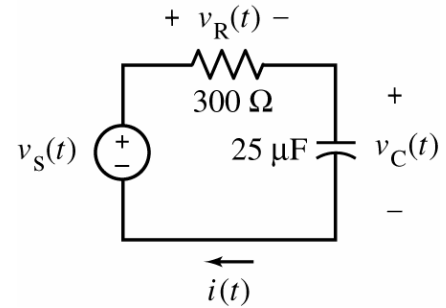where A , B , ω , θ and ϕ are constants to be determined.



From the plot

- 1) The period of both sinusoids is $T = 62.83 \text{ ms}$ so $\omega = \frac{2\pi}{0.06283} = 100 \text{ rad/s}$.
- 2) The peak-to-peak amplitude of the source voltage is 50 V so $A = 25 \text{ V}$.
- 3) The peak-to-peak amplitude of the capacitor voltage is 40 V so $B = 20 \text{ V}$.
- 4) $v_s(0) = 24.15 \text{ V}$ and $v_s(t)$ is decreasing at time $t = 0$ so $\theta = \cos^{-1}\left(\frac{24.15}{25}\right) = 15^\circ$.
- 5) $v_c(0) = 18.54 \text{ V}$ and $v_c(t)$ is increasing at time $t = 0$ so $\phi = -\cos^{-1}\left(\frac{18.54}{20}\right) = -22^\circ$.

so

$$v_s(t) = 25 \cos(100t + 15^\circ) \text{ V} \quad \text{and} \quad v_c(t) = 20 \cos(100t - 22^\circ) \text{ V}$$

Apply KVL in the circuit to get

$$v_R(t) = v_s(t) - v_c(t) = 25 \cos(100t + 15^\circ) - 20 \cos(100t - 22^\circ)$$

First, we solve this equation using trigonometry:

Recall that

$$\cos(\alpha \pm \beta) = \cos(\alpha)\cos(\beta) \mp \sin(\alpha)\sin(\beta)$$

so

$$\begin{aligned} 25 \cos(100t + 15^\circ) &= 25 [\cos(100t)\cos(15^\circ) - \sin(100t)\sin(15^\circ)] \\ &= 25 \cos(15^\circ)\cos(100t) - 25 \sin(15^\circ)\sin(100t) \\ &= 24.15 \cos(100t) - 6.47 \sin(100t) \end{aligned}$$


and

$$\begin{aligned} 20 \cos(100t - 22^\circ) &= 20 [\cos(100t)\cos(22^\circ) + \sin(100t)\sin(22^\circ)] \\ &= 20 \cos(22^\circ)\cos(100t) + 20 \sin(22^\circ)\sin(100t) \\ &= 18.54 \cos(100t) + 7.49 \sin(100t) \end{aligned}$$

The KVL equation indicates that

$$\begin{aligned} v_R(t) = v_s(t) - v_C(t) &= 25 \cos(100t + 15^\circ) - 20 \cos(100t - 22^\circ) \\ &= [24.15 \cos(100t) - 6.47 \sin(100t)] - [18.54 \cos(100t) + 7.49 \sin(100t)] \\ &= (24.15 - 18.54) \cos(100t) + (-6.47 - 7.49) \sin(100t) \\ &= 5.61 \cos(100t) - 16.96 \sin(100t) \end{aligned}$$

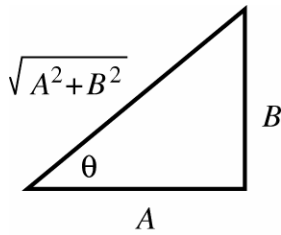We need another trigonometric identity. Consider



$$\sin(\theta) = \frac{B}{\sqrt{A^2 + B^2}}$$

$$\cos(\theta) = \frac{A}{\sqrt{A^2 + B^2}}$$

$$A \cos(\omega t) + B \sin(\omega t)$$

$$= \sqrt{A^2 + B^2} \left[\frac{A}{\sqrt{A^2 + B^2}} \cos(\omega t) + \frac{B}{\sqrt{A^2 + B^2}} \sin(\omega t) \right]$$

$$= \sqrt{A^2 + B^2} [\cos(\theta) \cos(\omega t) + \sin(\theta) \sin(\omega t)]$$

$$= \sqrt{A^2 + B^2} [\cos(-\theta) \cos(\omega t) - \sin(-\theta) \sin(\omega t)]$$

$$= \sqrt{A^2 + B^2} \cos(\omega t - \theta)$$

$$\text{where } \theta = \tan^{-1} \left(\frac{B}{A} \right)$$

Consequently

$$\begin{aligned} v_R(t) = 5.61 \cos(100t) - 16.96 \sin(100t) &= \sqrt{5.61^2 + 16.96^2} \cos \left(100t - \tan^{-1} \left(\frac{-16.96}{5.61} \right) \right) \\ &= 15 \cos(100t - (-68.1^\circ)) \\ &= 15 \cos(100t + 68.1^\circ) \text{ V} \end{aligned}$$

Second, we will solve the KVL equation using complex numbers. To do so we associate the complex number $A\angle\theta$ with the sinusoid $A\cos(\omega t + \theta)$. That is

$$A\cos(\omega t + \theta) \Leftrightarrow A\angle\theta$$

Using this association:

$$\begin{aligned} 25\cos(100t + 15^\circ) - 20\cos(100t - 22^\circ) &\Leftrightarrow 25\angle 15^\circ - 20\angle -22^\circ = (24.15 + j 6.47) - (18.54 - j 7.49) \\ &= (24.15 - 18.54) + j(6.47 + 7.49) \\ &= 5.61 + j 13.96 = 15\angle 68.1^\circ \end{aligned}$$

Then

$$15\cos(100t + 68.1^\circ) \Leftrightarrow 15\angle 68.1^\circ$$

We have achieved the same result with considerably less effort.

Check:
$$i(t) = \frac{v_R(t)}{300} = \frac{15\cos(100t + 68.1^\circ)}{300} = 0.05\cos(100t + 68.1^\circ)$$

But also

$$\begin{aligned} i(t) &= (25 \times 10^{-6}) \frac{dv_C(t)}{dt} = (25 \times 10^{-6}) \frac{d}{dt}(20\cos(100t - 22^\circ)) \\ &= (25 \times 10^{-6})(20)(100)(-\sin(100t - 22^\circ)) \\ &= 0.05\sin(100t + 180^\circ - 22^\circ) = 0.05\sin(100t + 158^\circ) \\ &= 0.05\cos(100t + 158^\circ - 90^\circ) \\ &= 0.05\cos(100t + 68^\circ) \end{aligned}$$