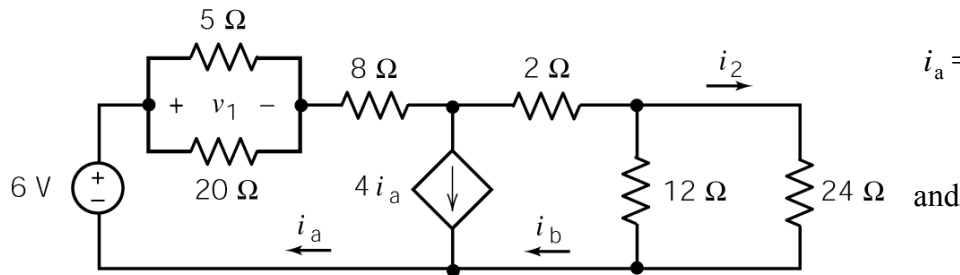


ES 250 First Midterm Practice Exam 2

1.




$$i_a = \underline{-0.333} \text{ A}, \quad i_b = \underline{1} \text{ A},$$

$$i_2 = \underline{0.333} \text{ A},$$

$$v_1 = \underline{-1.333} \text{ V}$$

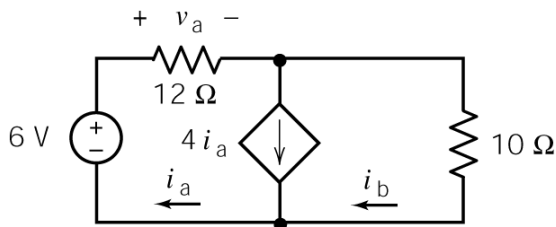Use equivalent resistances to reduce the circuit to



$$\text{From KCL } i_b = 4i_a + i_a \Rightarrow i_b = -3i_a.$$

From KVL

$$12i_a + 10i_b - 6 = 0 \Rightarrow 12i_a + 10(-3i_a) = 6$$

$$\text{So } i_a = -\frac{1}{3} \text{ A}, \quad v_a = -4 \text{ A} \text{ and } i_b = 1 \text{ A}.$$


Returning our attention to the original circuit, notice that i_a and i_b were not changed when the circuit was reduced. Now $v_1 = (5 \parallel 20)i_a = (4)(-0.333) = -1.333 \text{ V}$ and $i_2 = \frac{12}{12+24}i_b = 0.333 \text{ A}$.

2.

The current in the 20-Ω resistor is $i_a = \underline{-1.25} \text{ A}$.

The voltage across the 10-Ω resistor is $v_b = \underline{-30} \text{ V}$.

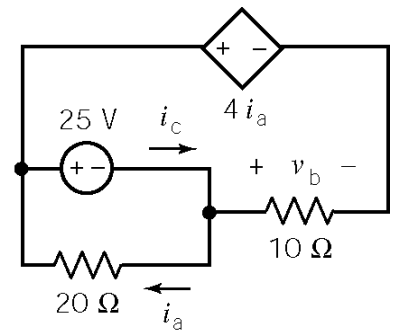The (independent) voltage source current is $i_c = \underline{-4.25} \text{ A}$.




$$\text{From Ohm's law } i_a = -\frac{25}{20} = -1.25 \text{ A}.$$

$$\text{From KVL } 4i_a - v_b + 20i_a = 0 \Rightarrow v_b = 24i_a = 24(-1.25) = -30 \text{ V}$$

$$\text{From KCL } i_c = i_a + \frac{v_b}{10} = -1.25 + \frac{-30}{10} = -4.25 \text{ A}$$

3.

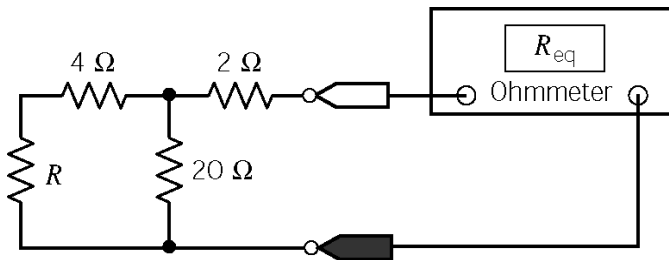

The Ohmmeter measures equivalent resistance.

a. To cause $R_{eq} = 12 \Omega$, choose $R = \underline{16} \Omega$.

b. If $R = 14 \Omega$ then $R_{eq} = \underline{11.5} \Omega$.


$R_{eq} = 2 + (20 \parallel (4 + R))$. When $R_{eq} = 12 \Omega$ then

$$12 = 2 + (20 \parallel (4 + R)) \Rightarrow 10 = \frac{20(4 + R)}{20 + (4 + R)} \Rightarrow 24 + R = 2(4 + R) \Rightarrow R = 16 \Omega$$

When $R = 14 \Omega$ then

$$R_{eq} = 2 + (20 \parallel (4 + 14)) = 2 + (20 \parallel 18) = 2 + \frac{20(18)}{20 + 18} = 11.4736 \Omega$$

4.

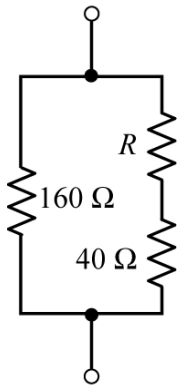

Consider this combination of resistors. Let R_p denote the equivalent resistance.

(a) Suppose $40 \Omega \leq R \leq 400 \Omega$. Determine the corresponding range of values of R_p :

$$\underline{53.33} \Omega \leq R_p \leq \underline{117.33} \Omega$$

(b) Suppose instead $R = 0$ (a short circuit). Then $R_p = \underline{32} \Omega$

(c) Suppose instead $R = \infty$ (an open circuit). Then $R_p = \underline{160} \Omega$

(d) Suppose instead the equivalent resistance is $R_p = 80 \Omega$. Then $R = \underline{120} \Omega$

$$\text{When } R = 40 \Omega \text{ then } R_p = 160 \parallel (40 + 40) = 160 \parallel 80 = \frac{160(80)}{160 + 80} = \frac{160}{3} = 53.33 \Omega.$$

$$\text{When } R = 400 \Omega \text{ then } R_p = 160 \parallel (40 + 400) = 160 \parallel 440 = \frac{160(440)}{160 + 440} = \frac{16(44)}{6} = 117.33 \Omega.$$


$$\text{When } R = 0 \text{ then } R_p = 160 \parallel (0 + 40) = 160 \parallel 40 = \frac{160(40)}{160 + 40} = \frac{16(4)}{2} = 32 \Omega.$$

$$\text{When } R = \infty \text{ then } R_p = 160 \parallel (\infty + 40) = 160 \parallel \infty = \frac{1}{\frac{1}{160} + \frac{1}{\infty}} = 160 \Omega.$$

When $R_p = 80 \Omega$ then

$$80 = 160 \parallel (R + 40) = \frac{160(R + 40)}{160 + R + 40} \Rightarrow R + 200 = \frac{160}{80}(R + 40) = 2R + 80 \Rightarrow R = 120 \Omega.$$

5.

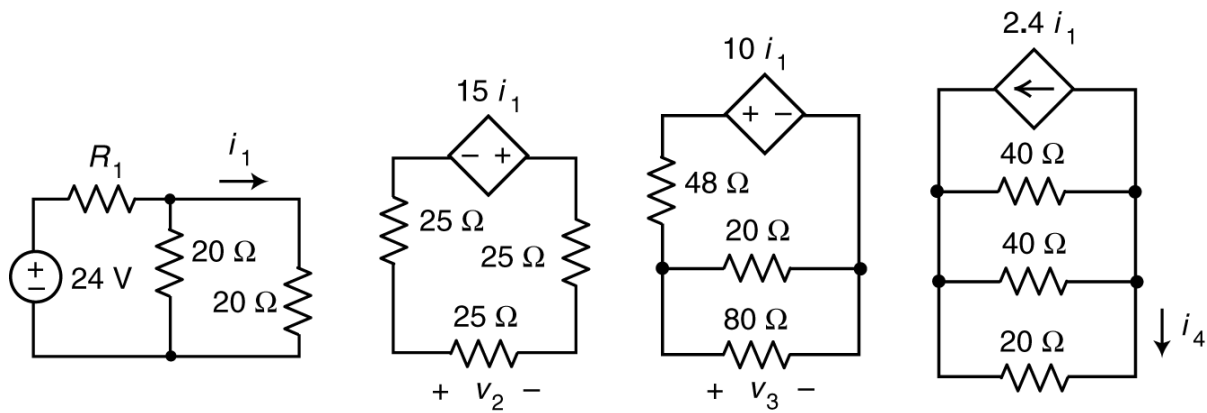

Here's a single circuit drawn in four parts for convenience. The four parts are connected by the dependent sources. Given that $i_1 = 0.8$ A, determine the values of R_1 , v_2 , v_3 , and i_4 .


$$R_1 = \underline{5} \Omega, v_2 = \underline{-4} \text{ V}, v_3 = \underline{2} \text{ V} \text{ and } i_4 = \underline{-0.96} \text{ A.}$$

$$0.8 = \frac{1}{2} \left(\frac{24}{R_1 + 10} \right) \Rightarrow R_1 + 10 = \frac{12}{0.8} = 15 \Rightarrow R_1 = 5 \Omega$$

$$v_2 = -\frac{1}{3} [15(0.8)] = -4 \text{ V}, v_3 = \frac{20 \parallel 80}{48 + (20 \parallel 80)} 10(0.8) = \frac{16}{48 + 16} 8 = 2 \text{ V}$$

$$i_4 = -\frac{40 \parallel 40}{(40 \parallel 40) + 20} 2.4(0.8) = -\frac{1}{2} (1.92) = -0.96 \text{ A}$$

6.

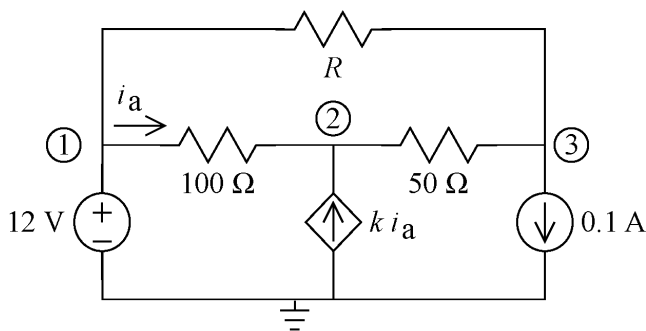

Encircled numbers are node numbers. The corresponding node voltages are:

$$v_1 = 12 \text{ V}, v_2 = 10.5 \text{ V} \text{ and } v_3 = 6 \text{ V}$$

The value of the gain of the CCCS is $k = \underline{5.00} \text{ A/A}$.


The resistance of the resistor at the top of the circuit is $R = \underline{600} \Omega$. (Round to an integer.)

The power supplied by the independent (0.1 A) current source is $\underline{-0.6} \text{ W}$.

$$i_a = \frac{12-10.5}{100} = 0.015 \text{ A}, \quad i_b = \frac{10.5-6}{50} = 0.09 \text{ A}$$


$$i_c + i_b = 0.1 \Rightarrow i_c = -0.09 + 0.1 = 0.01 \text{ A}$$
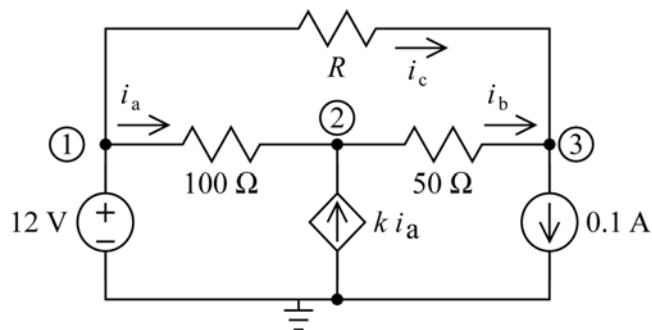
$$i_a + k i_a = i_b \Rightarrow k i_a = i_b - i_a = 0.09 - 0.015 = 0.075 \text{ A}$$



$$k = \frac{k i_a}{i_a} = \frac{0.075}{0.015} = 5 \text{ A/A}, \quad R = \frac{12-6}{i_c} = \frac{6}{0.01} = 600 \Omega \text{ and the power is } -(6)(0.1) = -0.6 \text{ W}$$

7.

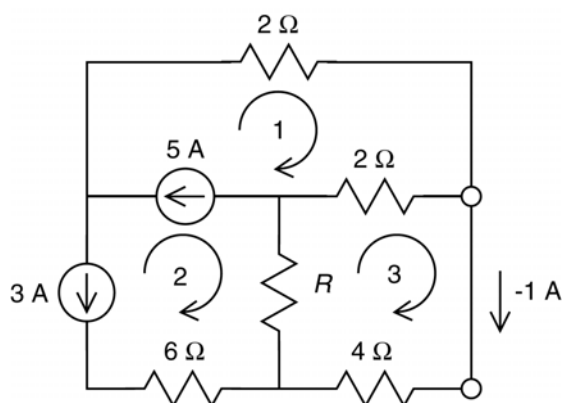

Let i_1, i_2 and i_3 denote the mesh currents in meshes 1, 2 and 3, respectively.

Determine the values of these mesh currents:

$$i_1 = \underline{2} \text{ A and } i_2 = \underline{-3} \text{ A}$$

Determine the value of the resistance R :

$$R = \underline{5} \Omega$$

$i_2 = -3 \text{ A}, \quad i_1 - i_2 = 5 \Rightarrow i_1 = 2 \text{ A}, \quad i_3 = -1 \text{ A}$. The applying KVL to mesh 3 gives

$$2(i_3 - i_1) + 4i_3 + R(i_3 - i_2) = 0 \Rightarrow R = -\frac{2(i_3 - i_1) + 4i_3}{i_3 - i_2} = -\frac{2(-1-2) + 4(-1)}{-1 - (-3)} = 5 \Omega$$