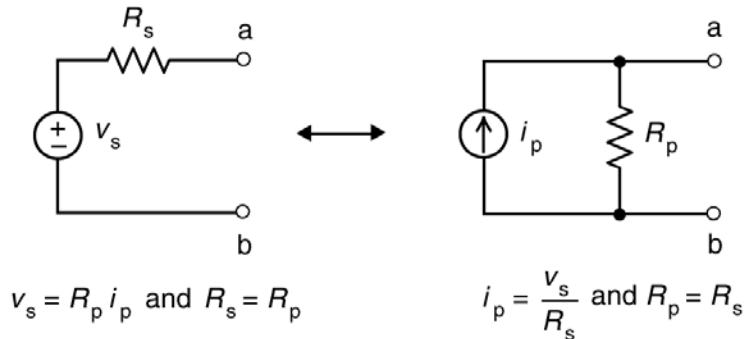


## Equivalent Circuits


### 1. Source Transformations




### 2. Circuit Analysis using Source Transformations and Equivalent Circuits

- a) Reduce the size of the “original circuit”
  - i) using Source Transformations
  - ii) by replacing series or parallel elements with equivalent elements.
- b) Analyze the “equivalent circuit” .
- c) Identify currents or voltages in the “original circuit” that are equal to the corresponding currents or voltages in the “equivalent circuit” .
- d) Analyze the “original circuit” ...
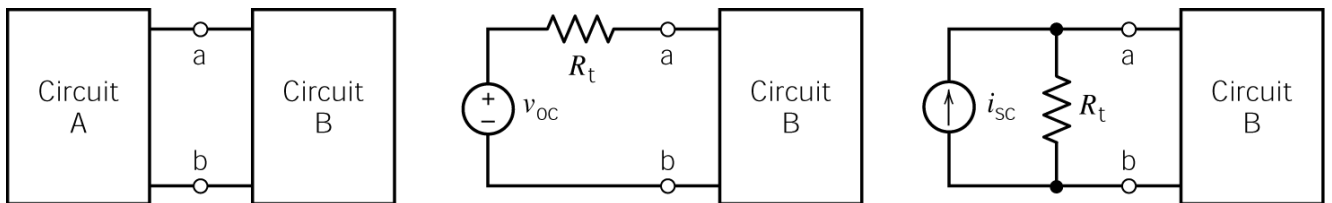
### 3. Thevenin and Norton Equivalent circuits




a)  $v_{oc}$ ,  $i_{sc}$  and  $R_t$ :

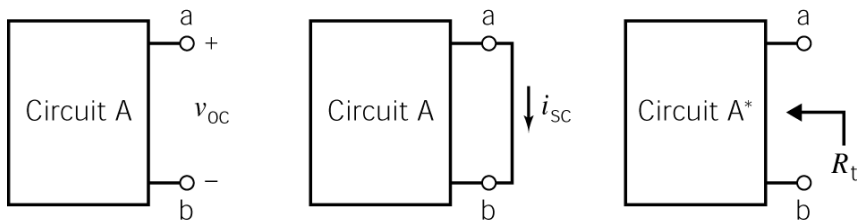


- b) Reducing a circuit to it’s Thevenin and Norton equivalent using Source Transformations and Equivalent Circuits.
- c) Applications of the Thevenin and Norton equivalent circuit
  - i) First-order circuits
  - ii) Maximum power transfer.
  - iii) Many more

## Op Amp Circuits

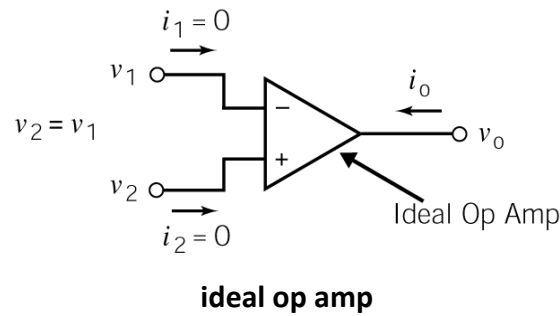

To obtain the node equations representing an op amp circuit:

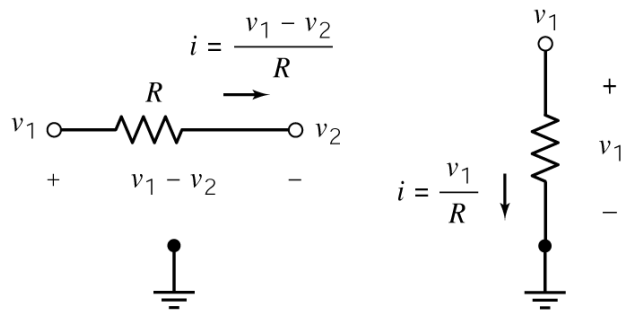1. Express ...
    - a. voltage-source voltages
    - b. ideal op amp voltages and currents**
    - c. resistor currents
- ... in terms of the node voltages



2. Apply KCL at each node except
  - a. the reference node
  - b. the other node of a grounded voltage source
  - c. the output node of an op amp**
  - d. either node of an ungrounded voltage source. Instead, apply KCL to the supernode corresponding to that voltage source.

After writing and solving the node equations, apply KCL at the output node of a op amp to determine the output current of that op amp.


The power supplied by an op amp is the product of the output current directed out of the op amp and node voltage at the output node of the op amp.

## Applications

1. Amplifiers: inverting, noninverting, voltage divider with voltage follower.
2.  $y=mx+b$  (Superposition.)

## Capacitors and Inductors

### 1. Element equations

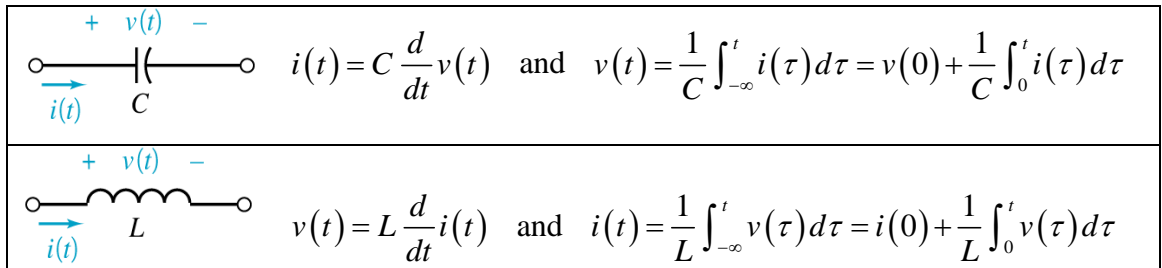

2. In a dc circuit...
3. Capacitor voltages and inductor currents are continuous.
4. Series and parallel capacitors and inductors...

## First-order Circuits


### 1. Identifying features:

- a. Single capacitor or single inductor.
- b. Something happened
  - i. Switch
  - ii. Step function
- c. Constant inputs except at  $t_0$ .

### 2. Find

- a. Initial condition:  $t < t_0$  and steady state.
- b. Thevenin or Norton equivalent of ... after  $t_0$ .
- c.  $L$  or  $C$


### 3.

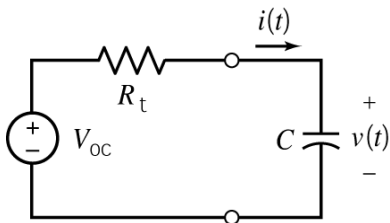

$$v(t) = V_{oc} + (v(0) - V_{oc})e^{-at} \quad \text{for } t \geq 0$$

where

$$a = \frac{1}{R_t C}$$

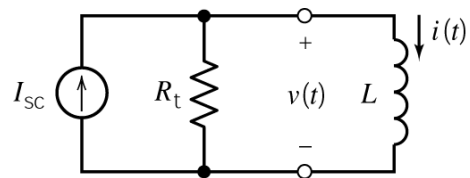

$$i(t) = I_{sc} + (i(0) - I_{sc})e^{-at} \quad \text{for } t \geq 0$$

where

$$a = \frac{R_t}{L}$$

4. Find output current or voltage.