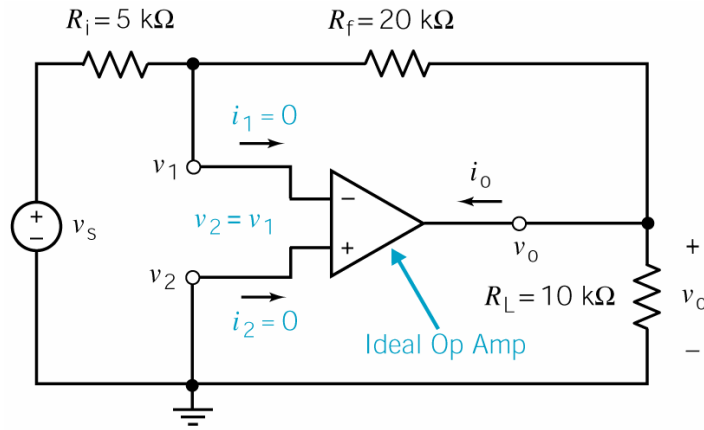


The Inverting Amplifier



v_2 is the node voltage at the reference node (ground), so $v_2 = 0$. The op amp is ideal so $v_1 = v_2$. (All op amps are ideal in this course.) Consequently,

$$v_1 = v_2 = 0$$

Apply KCL at the node connected to the inverting input of the op amp to get

$$\frac{v_s - v_1}{R_i} = i_1 + \frac{v_1 - v_o}{R_f} \Rightarrow \frac{v_s}{R_i} = \frac{-v_o}{R_f} \Rightarrow v_o = -\frac{R_f}{R_i} v_s = -4v_s$$

Beware: Both $\frac{v_o}{v_s} = -\frac{R_f}{R_i}$ and $\left| \frac{v_o}{v_s} \right| = \frac{R_f}{R_i}$ are sometimes called the “gain” of the inverting amplifier.

Apply KCL at the output node of the op amp to get

$$\frac{v_1 - v_o}{R_f} = i_o + \frac{v_o}{R_L} \Rightarrow i_o = -\left(\frac{1}{R_f} + \frac{1}{R_L} \right) v_o = -\frac{R_f + R_L}{R_f R_L} v_o = -\frac{R_f + R_L}{R_f R_L} \left(-\frac{R_f}{R_i} v_s \right)$$

or

$$i_o = \frac{R_f + R_L}{R_i R_L} v_s = \frac{2 \times 10^4 + 10^4}{(2 \times 10^4) 10^4} v_s = (0.6 \times 10^{-3}) v_s$$

The power received by the op amp is

$$v_o i_o = \left(-\frac{R_f}{R_i} v_s \right) \left(\frac{R_f + R_L}{R_i R_L} v_s \right) = -\left(\frac{R_f}{R_i} \right) \left(\frac{R_f + R_L}{R_i R_L} \right) v_s^2 = -2.4 \times 10^{-3} v_s^2$$


The power supplied by the op amp is

$$-v_o i_o = 2.4 \times 10^{-3} v_s^2$$

The input to this circuit is the voltage source voltage, v_s . The output is the voltage, v_o , across R_L . Recall that the input and output voltages of the circuit are related by

$$v_o = -\frac{R_f}{R_i} v_s = -4v_s$$

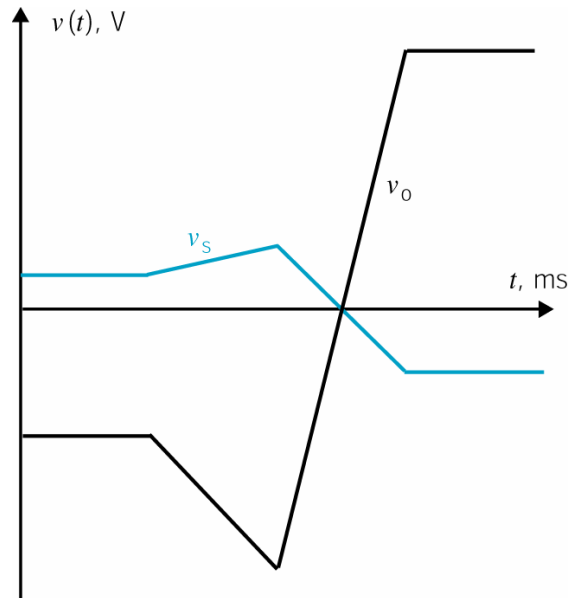Consider this plot of the input and output voltages for a particular input:



The output is seen to be 4 times as large as the input. The output is inverted with respect to the input due to the minus sign. Appropriately, the circuit is called an inverting amplifier.