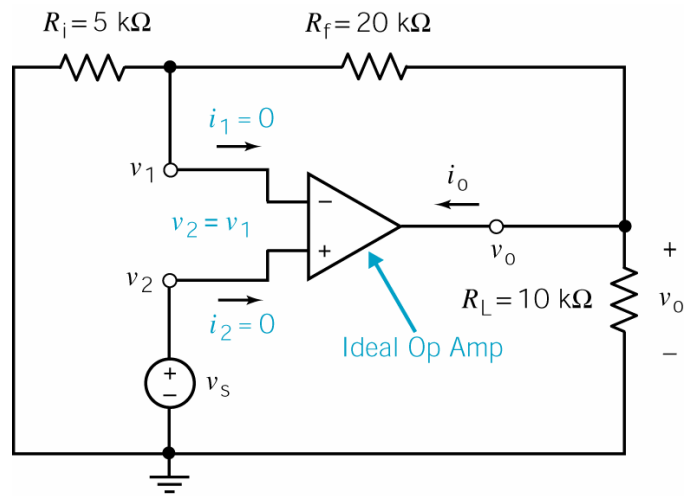


The Noninverting Amplifier



The voltage source causes $v_2 = v_s$. The op amp is ideal so $v_1 = v_2$. (All op amps are ideal in this course.) Consequently,

$$v_1 = v_2 = v_s$$


Apply KCL at the node connected to the inverting input of the op amp to get

$$\frac{0 - v_1}{R_i} = i_1 + \frac{v_1 - v_o}{R_f} \Rightarrow \frac{-v_s}{R_i} = \frac{v_s - v_o}{R_f} \Rightarrow v_o = \left(1 + \frac{R_f}{R_i}\right) v_s = 5v_s$$

Apply KCL at the output node of the op amp to get

$$\begin{aligned} \frac{v_1 - v_o}{R_f} = i_o + \frac{v_o}{R_L} &\Rightarrow i_o = -\left(\frac{1}{R_f} + \frac{1}{R_L}\right)v_o + \frac{1}{R_f}v_s = -\left(\frac{1}{R_f} + \frac{1}{R_L}\right)\left(1 + \frac{R_f}{R_i}\right)v_s + \frac{1}{R_f}v_s \\ &= -\left(\frac{1}{R_i} + \frac{1}{R_L}\left(1 + \frac{R_f}{R_i}\right)\right)v_s \\ &= (0.45 \times 10^{-3})v_s \end{aligned}$$

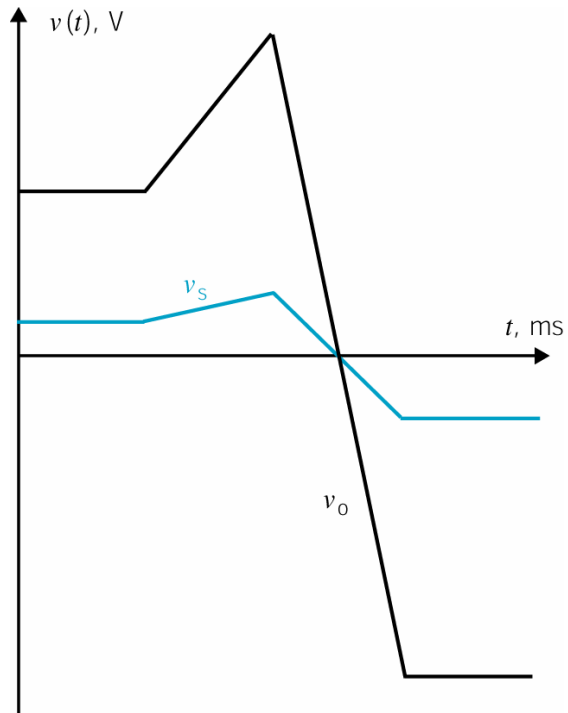The input to this circuit is the voltage source voltage, v_s . The output is the voltage, v_o , across R_L . Consider this plot of the input and output voltages for a particular input:



The output is seen to be 5 times as large as the input. The output is not inverted with respect to the input. Appropriately, the circuit is called a noninverting amplifier.