


## Examples

1. This circuit has three inputs:  $v_1$ ,  $v_2$  and  $v_3$ . The output of the circuit is  $v_o$ . The output is related to the inputs by

$$v_o = a v_1 + b v_2 + c v_3$$

where  $a$ ,  $b$  and  $c$  are constants.

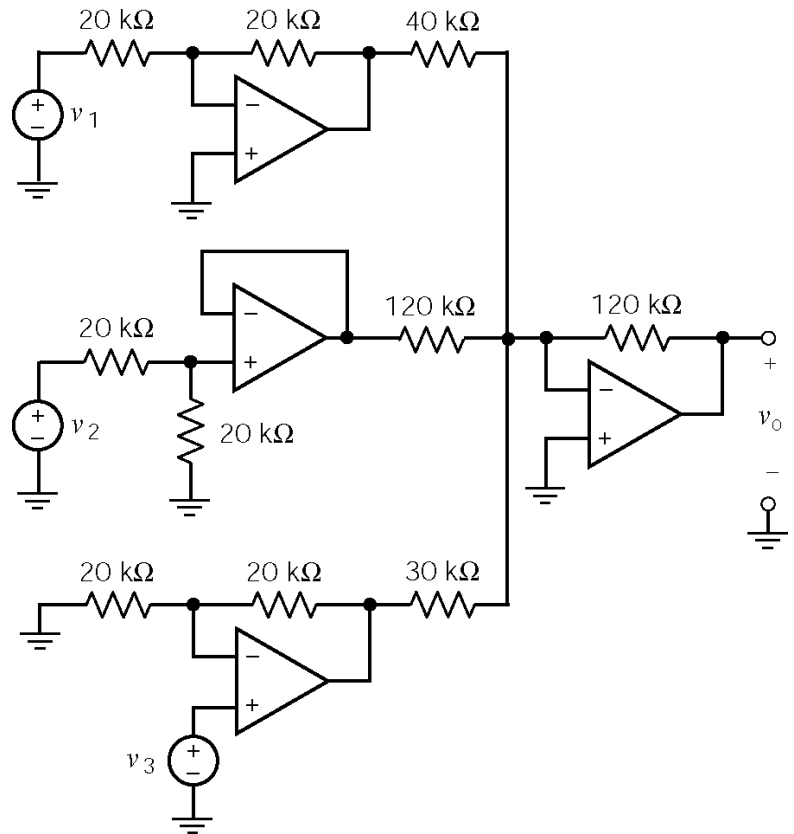Determine the values of  $a$ ,  $b$  and  $c$ .




2. This circuit has two inputs:  $v_1$  and  $v_2$ . The output of the circuit is  $v_o$ . The output is related to the inputs by

$$v_o = a v_1 + b v_2$$

where  $a$  and  $b$  are constants.

Determine the values of  $a$  and  $b$ .

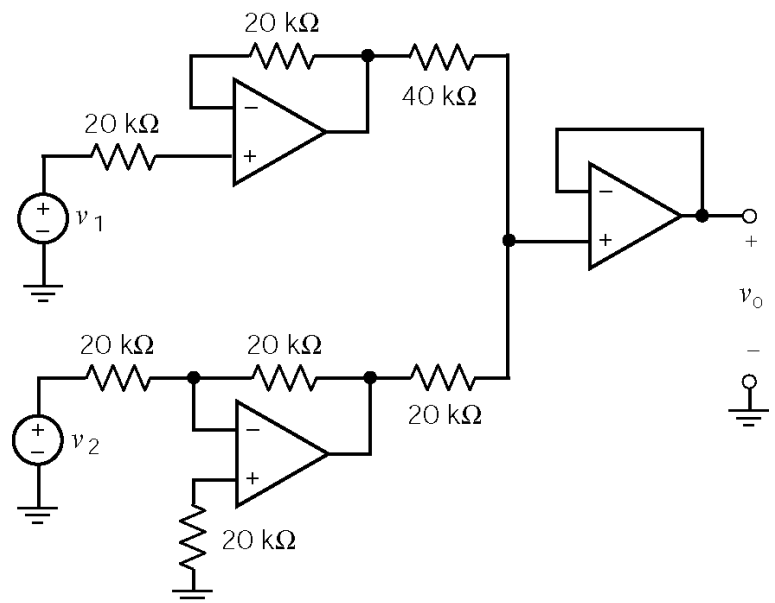

## Solutions


1. Use units of V, mA and k $\Omega$ .

$$v_o = - \left[ \left( \frac{120}{40} \right) \left( -\frac{20}{20} \right) v_1 + \left( \frac{120}{120} \right) \left( \frac{20}{20+20} \right) v_2 + \left( \frac{120}{30} \right) \left( 1 + \frac{20}{20} \right) v_3 \right] = 3 v_1 - 0.5 v_2 - 8 v_3$$

so

$$a = 3, \quad b = -0.5 \text{ and } c = -8$$

2.

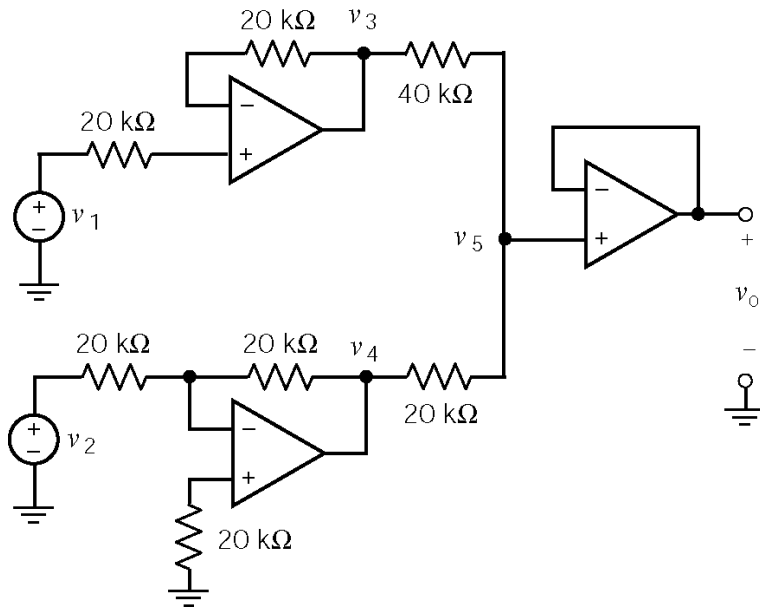

Label the node voltages as shown.  
Use units of V, mA and k $\Omega$ .

$$v_3 = v_1 \quad \text{and} \quad v_4 = -v_2$$

Write a node equation

$$\frac{v_5 - v_3}{40} + \frac{v_5 - v_4}{20} = 0$$

Solving for  $v_5$

$$v_5 = \frac{1}{3}(v_3 + 2v_4) = \frac{1}{3}v_1 - \frac{2}{3}v_2$$

so

$$a = -\frac{1}{3} \quad \text{and} \quad b = -\frac{2}{3}$$