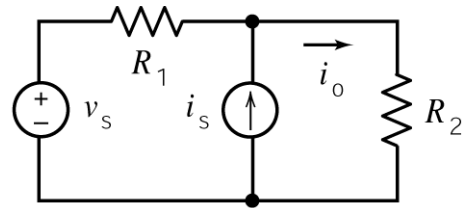


Another Sample ES 250 Final Exam

1. This circuit has two inputs, v_s and i_s , and one output i_o . The output is related to the inputs by the equation

$$i_o = a i_s + b v_s$$



Given the following two facts:

The output is $i_o = 0.45$ A when the inputs are $i_s = 0.25$ A and $v_s = 15$ V.

and

The output is $i_o = 0.30$ A when the inputs are $i_s = 0.50$ A and $v_s = 0$ V.

Determine the following:


The values of the constants a and b are $a = \underline{\hspace{2cm}}$ and $b = \underline{\hspace{2cm}}$ A/V.

The values of the resistances are $R_1 = \underline{\hspace{2cm}}$ Ω and $R_2 = \underline{\hspace{2cm}}$ Ω .

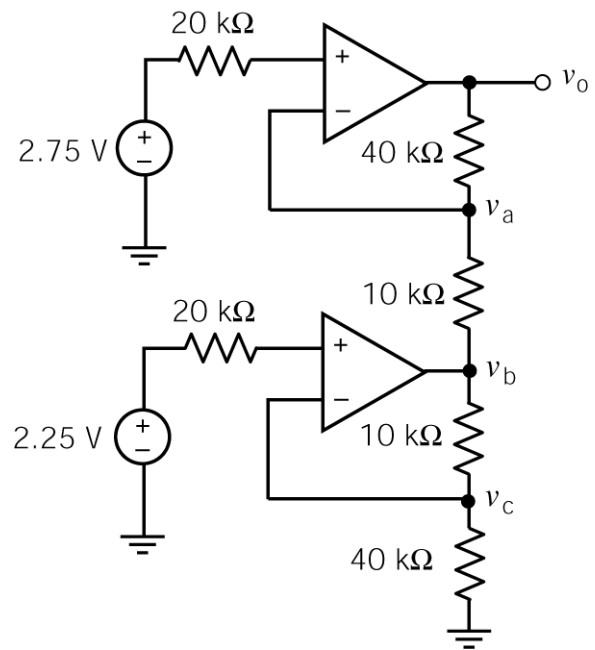
2. Determine the values of the node voltages v_a , v_b , v_c and v_o :

$$v_a = \underline{\hspace{2cm}} \text{ V, } v_b = \underline{\hspace{2cm}} \text{ V,}$$

$$v_c = \underline{\hspace{2cm}} \text{ V, and } v_o = \underline{\hspace{2cm}} \text{ V.}$$



3.

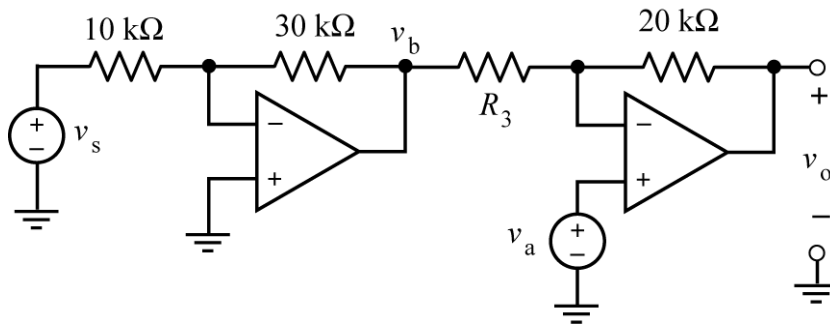

The node voltage v_b is given by
 $v_b = -3v_s$

The input to this circuit is the voltage v_s . The output is the node voltage v_o . The output is related to the input by the equation $v_o = m v_s + b$ where m and b are constants.

(a) Suppose $v_o = 18$ V when $v_s = 1$ V and $v_o = 6$ V when $v_s = -1$ V. Determine the values of m and b :

$$m = \text{_____ V/V and } b = \text{_____ V.}$$

(b) Instead, suppose that $R_3 = 12$ kΩ and $v_a = 3$ V. Determine the values of m and b :

$$m = \text{_____ V/V and } b = \text{_____ V.}$$

(c) Instead, suppose that we require $v_o = 4 v_s + 7$. Determine the required values of R_3 and v_a :

$$R_3 = \text{_____ kΩ and } v_a = \text{_____ V.}$$


4. The input to this circuit is the voltage:

$$v(t) = 4e^{-20t} \text{ V for } t > 0$$


The output is the current: $i(t) = -1.2e^{-20t} - 1.5$ A for $t > 0$

The initial condition is $i_L(0) = -3.5$ A. Determine the values of the resistance and inductance:
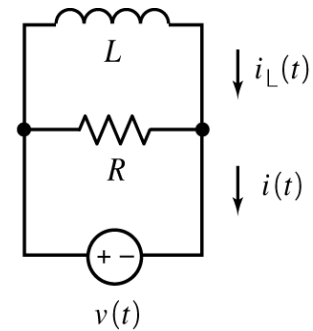
$$R = \text{_____ Ω and } L = \text{_____ H.}$$



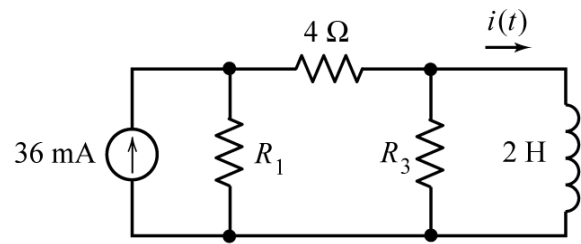5. After time $t = 0$, a given circuit is represented by this circuit diagram.



a. Suppose that the inductor current is

$$i(t) = 21.6 + 28.4e^{-4t} \text{ mA for } t \geq 0$$

Determine the values of R_1 and R_3 : $R_1 = \underline{\hspace{2cm}} \Omega$ and $R_3 = \underline{\hspace{2cm}} \Omega$.

b. Suppose instead that $R_1 = 16 \Omega$, $R_3 = 20 \Omega$, the initial condition is $i(0) = 10 \text{ mA}$, and the inductor current is $i(t) = A + Be^{-at}$ for $t \geq 0$. Determine the values of the constants A , B , and a :


$$A = \underline{\hspace{2cm}} \text{ mA}, \quad B = \underline{\hspace{2cm}} \text{ mA} \quad \text{and} \quad a = \underline{\hspace{2cm}} \text{ s}^{-1}.$$

6. a) Determine the time constant, τ , and the steady state capacitor voltage, $v(\infty)$, when the switch is open:



$$\tau = \underline{\hspace{2cm}} \text{ s} \quad \text{and} \quad v(\infty) = \underline{\hspace{2cm}} \text{ V}$$

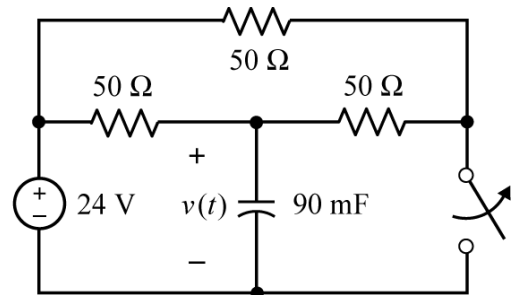b) Determine the time constant, τ , and the steady state capacitor voltage, $v(\infty)$, when the switch is closed:

$$\tau = \underline{\hspace{2cm}} \text{ s} \quad \text{and} \quad v(\infty) = \underline{\hspace{2cm}} \text{ V}$$



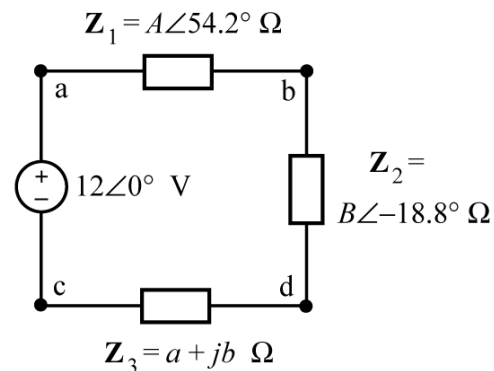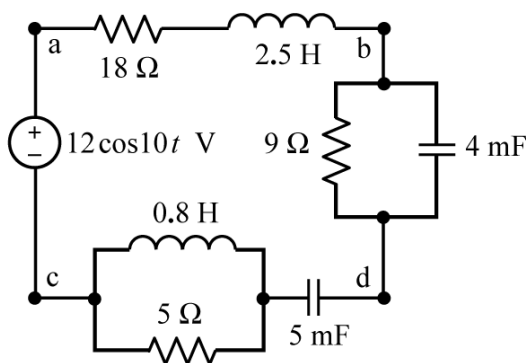
7. Here is an ac circuit represented in both the time domain and the frequency domain:



Determine the values of A , B , a and b .

$$A = \underline{\hspace{2cm}} \text{ V}, \quad B = \underline{\hspace{2cm}} \Omega, \quad a = \underline{\hspace{2cm}} \Omega \quad \text{and} \quad b = \underline{\hspace{2cm}} \Omega.$$

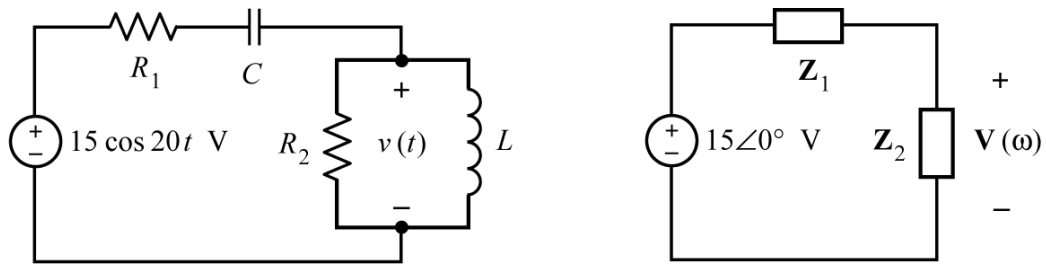8. Here is an ac circuit represented in both the time domain and the frequency domain:



Given that $Z_1 = 15.3 \angle -24.1^\circ \Omega$, $Z_2 = 14.4 \angle 36.9^\circ \Omega$ and $V(\omega) = A \angle 31.5^\circ$ V, determine the values of A , R_1 , R_2 , L and C .

$A =$ _____ V, $R_1 =$ _____ Ω , $R_2 =$ _____ Ω , $L =$ _____ H and $C =$ _____ mF.