

## ES 250 Practice Final Exam

1. Given that


$$v_a = 8 \text{ V},$$

Determine the values of  $R_1$  and  $v_o$ :

$$R_1 = \underline{\quad 10 \quad} \Omega,$$

and
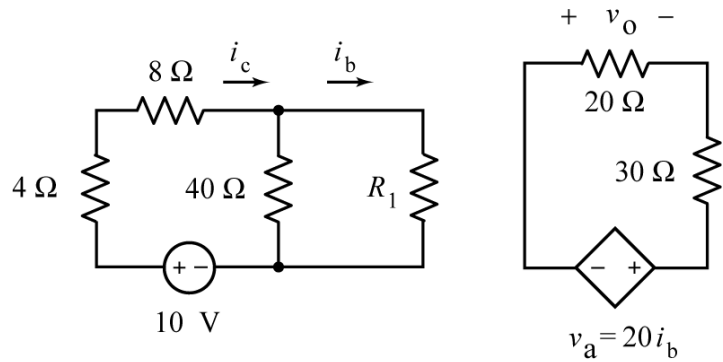
$$v_o = \underline{\quad -3.2 \quad} \text{ V}$$



First,

$$v_o = -\frac{20}{20+30}8 = -3.2 \text{ V}$$

Next,

$$\frac{8}{20} = i_b = \frac{40}{40+R_1} i_c = \frac{40}{40+R_1} \left( \frac{10}{12+40 \parallel R_1} \right) = \frac{40}{40+R_1} \left( \frac{10}{12+\frac{40R_1}{40+R_1}} \right) = \frac{400}{12(40+R_1)+40R_1} = \frac{400}{480+52R_1}$$


$$\text{Then } \frac{8}{20} = \frac{400}{480+52R_1} \Rightarrow 480+52R_1 = \frac{400(20)}{8} = 1000 \Rightarrow \frac{1000-480}{52} = 10 \Omega$$

2. Given that  $0 \leq R \leq \infty$  in this circuit, consider these two observations:

When  $R = 2 \Omega$  then  $v_R = 4 \text{ V}$  and  $i_R = 2 \text{ A}$ .

When  $R = 6 \Omega$  then  $v_R = 6 \text{ V}$  and  $i_R = 1 \text{ A}$ .

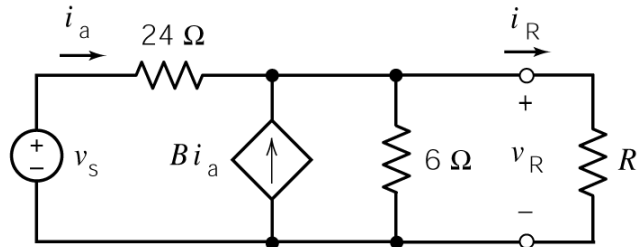Fill in the blanks in the following statements:




- The maximum value of  $i_R$  is 4 A.
- The maximum value of  $v_R$  is 8 V.
- The maximum value of  $p_R = i_R v_R$  occurs when  $R = \underline{\quad 2 \quad} \Omega$ .
- The maximum value of  $p_R = i_R v_R$  is 8 W.

We can replace the part of the circuit to the left of the terminals by its Thevenin equivalent circuit:

Using voltage division  $v_R = \frac{R}{R+R_t} v_{oc}$  and using Ohm's law  $i_R = \frac{v_{oc}}{R+R_t}$ .

By inspection,  $v_R = \frac{R}{R+R_t} v_{oc} = \frac{v_{oc}}{1+\frac{R_t}{R}}$  will be maximum when  $R = \infty$ . The

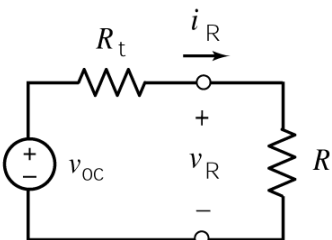maximum value of  $v_R$  will be  $v_{oc}$ . Similarly,  $i_R = \frac{v_{oc}}{R+R_t}$  will be



maximum when  $R = 0$ . The maximum value of  $i_R$  will be  $\frac{v_{oc}}{R_t} = i_{sc}$ .

The maximum power transfer theorem tells us that  $p_R = i_R v_R$  will be maximum when  $R = R_t$ . Then

$$p_R = i_R v_R = \left( \frac{v_{oc}}{R + R_t} \right) \left( \frac{R}{R + R_t} v_{oc} \right) = R \left( \frac{v_{oc}}{R + R_t} \right)^2.$$


Let's substitute the given data into the equation  $i_R = \frac{v_{oc}}{R + R_t}$ .

When  $R = 2 \Omega$  we get  $2 = \frac{v_{oc}}{2 + R_t} \Rightarrow 4 + 2R_t = v_{oc}$ . When  $R = 6 \Omega$  we get  $1 = \frac{v_{oc}}{6 + R_t} \Rightarrow 6 + R_t = v_{oc}$ .

So  $6 + R_t = 4 + 2R_t \Rightarrow R_t = 2 \Omega$  and  $v_{oc} = 4 + 2R_t = 8 \text{ V}$ . Also  $i_{sc} = \frac{v_{oc}}{R_t} = \frac{8}{2} = 4 \text{ A}$ .

Now the blanks can be easily filled-in.

3.

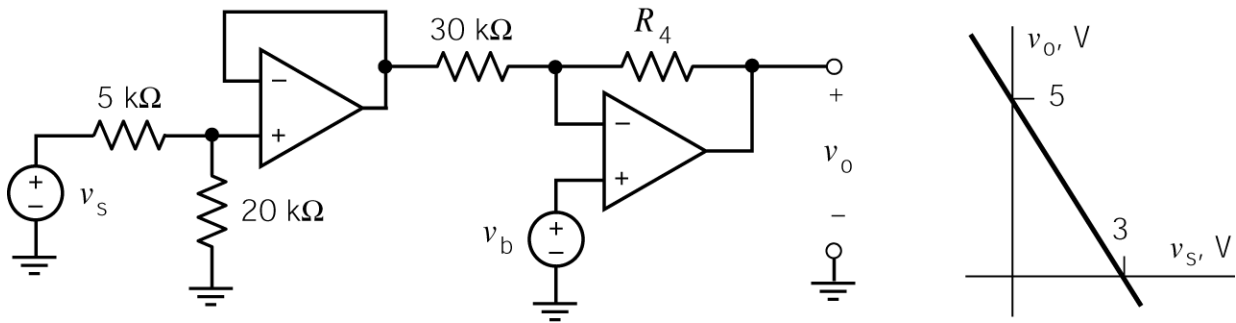

The input to this circuit is the voltage,  $v_s$ . The output is the voltage  $v_o$ . The voltage  $v_b$  is used to adjust the relationship between the input and output. Determine values of  $R_4$  and  $v_b$  that cause the circuit input and output have the relationship specified by the graph

$$v_b = \underline{1.62} \text{ V and } R_4 = \underline{62.5} \text{ k}\Omega.$$

Recognize the voltage divider, voltage follower and noninverting amplifier to write

$$v_o = \left( \frac{20 \times 10^3}{20 \times 10^3 + 5 \times 10^3} \right) \left( -\frac{R_4}{30 \times 10^3} \right) v_s + \left( 1 + \frac{R_4}{30 \times 10^3} \right) v_b = \left( -\frac{2R_4}{75 \times 10^3} \right) v_s + \left( 1 + \frac{R_4}{30 \times 10^3} \right) v_b$$

(Alternately, this equation can be obtained by writing two node equations: one at the noninverting node of the left op amp and the other at the inverting node of the right op amp.)

The equation of the straight line is  $v_o = -\frac{5}{3}v_s + 5$

Comparing coefficients gives


$$-\frac{2R_4}{75 \times 10^3} = -\frac{5}{3} \Rightarrow R_4 = \frac{5}{3} \times \frac{75 \times 10^3}{2} = 62.5 \times 10^3 = 62.5 \text{ k}\Omega$$

and

$$5 = \left(1 + \frac{R_4}{30 \times 10^3}\right) v_b = \left(1 + \frac{62.5 \times 10^3}{30 \times 10^3}\right) v_b = 3.08333 v_b \Rightarrow v_b = \frac{5}{3.08333} = 1.62 \text{ V}$$

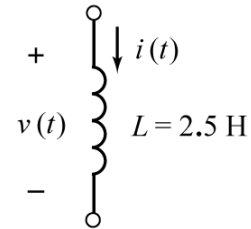4. Consider this inductor. The current and voltage are given by

$$i(t) = \begin{cases} 5t - 4.6 & 0 \leq t \leq 0.2 \\ at + b & 0.2 \leq t \leq 0.5 \\ c & t \geq 0.5 \end{cases} \quad \text{and} \quad v(t) = \begin{cases} 12.5 & 0 < t < 0.2 \\ 25 & 0.2 < t < 0.5 \\ 0 & t > 0.5 \end{cases}$$



where a, b and c are real constants. (The current is given in Amps, the voltage in Volts and the time in seconds.) Determine the values of the constants:

$$a = \underline{\quad 10 \quad} \text{ A/s}, \quad b = \underline{\quad -5.6 \quad} \text{ A} \quad \text{and} \quad c = \underline{\quad -0.6 \quad} \text{ A}$$

At  $t = 0.2$  s

$$i(0.2) = 5(0.2) - 4.6 = -3.6 \text{ A}$$

For  $0.2 \leq t \leq 0.5$

$$i(t) = \frac{1}{2.5} \int_{0.2}^t 25 d\tau - 3.6 = 10\tau \Big|_{0.2}^t - 3.6 = 10(t - 0.2) - 3.6 = 10t - 5.6 \text{ A}$$

At  $t = 0.5$  s

$$i(0.5) = 10(0.5) - 5.6 = -0.6 \text{ A}$$

For  $t \geq 0.5$

$$i(t) = \frac{1}{2.5} \int_{0.5}^t 0 d\tau - 0.6 = -0.6$$


Checks:

$$\text{At } t = 0.2 \text{ s} \quad i(0.2) = 10(0.2) - 5.6 = -3.6 \text{ A} \quad \checkmark$$

$$\text{For } 0.2 \leq t \leq 0.5 \quad v(t) = 2.5 \frac{d}{dt} i(t) = 2.5 \frac{d}{dt} (10t - 5.6) = 2.5(10) = 25 \text{ V} \quad \checkmark$$

$$-0.6 - (-3.6) = i(0.5) - i(0.2) = \frac{1}{2.5} \int_{0.2}^{0.5} 25 d\tau = 10(0.5 - 0.2) = 3 \text{ A} \quad \checkmark$$

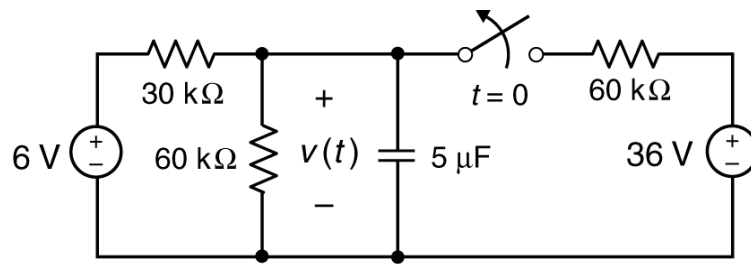5. This circuit is at steady state when the switch opens at time  $t = 0$ .




The capacitor voltage is  $v(t) = A + B e^{-at}$  for  $t \geq 0$ . Determine the values of the constants  $A$ ,  $B$ , and  $a$ :

$$A = \underline{\quad 4 \quad} \text{ V}, \quad B = \underline{\quad 8 \quad} \text{ V} \quad \text{and} \quad a = \underline{\quad 10 \quad} \text{ s}.$$

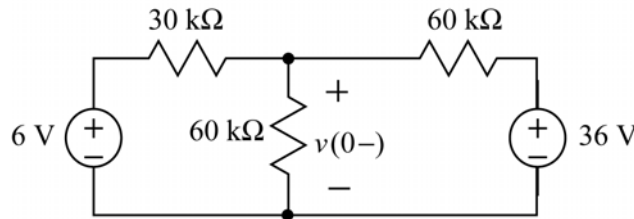**Solution:**

Before  $t = 0$ , with the switch closed and the circuit at the steady state, the capacitor acts like an open circuit so we have




Using superposition

$$v(0-) = \frac{60 \parallel 60}{30 + (60 \parallel 60)} 6 + \frac{60 \parallel 30}{60 + (60 \parallel 30)} 36 = \left(\frac{1}{2}\right) 6 + \left(\frac{1}{4}\right) 36 = 12 \text{ V}$$

The capacitor voltage is continuous so  $v(0+) = v(0-) = 12 \text{ V}$ .

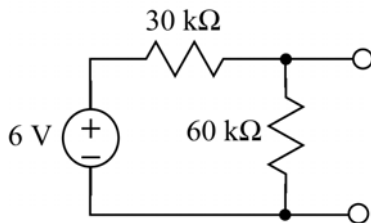After  $t = 0$  the switch is open. Determine the Thevenin equivalent circuit for the part of the circuit connected to the capacitor:



$$v_{oc} = \frac{60}{60 + 30} 6 = 4 \text{ V}$$

$$R_t = 30 \parallel 60 = 20 \text{ k}\Omega$$

The time constant is  $\tau = R_t C = (20 \times 10^3)(5 \times 10^{-6}) = 0.1 \text{ s}$  so  $\frac{1}{\tau} = 10 \frac{1}{\text{s}}$ .

The capacitor voltage is given by

$$v(t) = (v(0+) - v_{oc}) e^{-t/\tau} + v_{oc} = (12 - 4) e^{-10t} + 4 = 4 + 8 e^{-10t} \text{ V} \quad \text{for } t \geq 0$$

6. This circuit is at steady state before the switch closes at time  $t = 0$ . After the switch closes, the inductor current is given by


$$i(t) = 0.6 - 0.2e^{-5t} \text{ A for } t \geq 0$$

Determine the values of  $R_1$ ,  $R_2$  and  $L$ :

$$R_1 = \underline{20} \ \Omega, \quad R_2 = \underline{10} \ \Omega$$

and

$$L = \underline{4} \ \text{H}$$

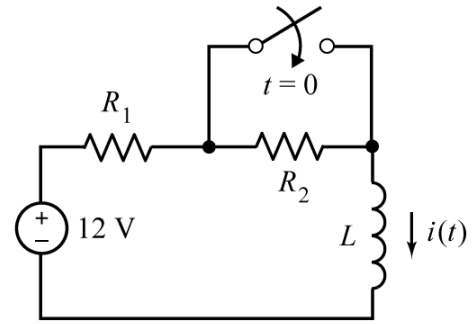


**Solution:**

The steady state current before the switch closes is equal to

$$i(0) = 0.6 - 0.2e^{-5(0)} = 0.4 \text{ A.}$$

The inductor will act like a short circuit when this circuit is at steady state so
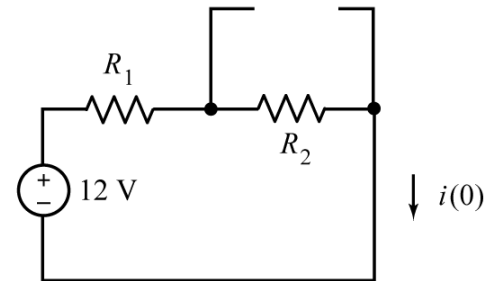
$$0.4 = i(0) = \frac{12}{R_1 + R_2} \Rightarrow R_1 + R_2 = 30 \ \Omega$$




After the switch has been open for a long time, the circuit will again be at steady state. The steady state inductor current will be

$$i(\infty) = 0.6 - 0.2e^{-5(\infty)} = 0.6 \text{ A}$$

The inductor will act like a short circuit when this circuit is at steady state so
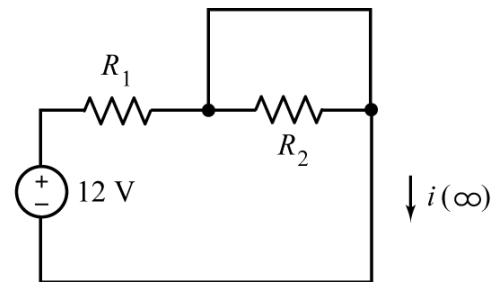
$$0.6 = i(\infty) = \frac{12}{R_1} \Rightarrow R_1 = 20 \ \Omega$$



Then  $R_2 = 10 \ \Omega$ .

After the switch is closed, the Thevenin resistance of the part of the circuit connected to the inductor is  $R_t = R_1$ .

Then


$$5 = \frac{1}{\tau} = \frac{R_t}{L} = \frac{R_1}{L} = \frac{20}{L} \Rightarrow L = 4 \ \text{H}$$

7. The voltage and current for this circuit are given by

$$v(t) = 20 \cos(20t + 15^\circ) \text{ V and } i(t) = 1.49 \cos(20t + 63^\circ) \text{ A}$$

Determine the values of the resistance,  $R$ , and capacitance,  $C$ :
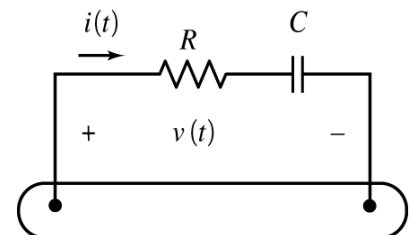
$$R = \underline{9} \ \Omega \text{ and } C = \underline{5} \ \text{mF.}$$




**Solution:**

In the frequency domain we have:

$$R - j\frac{1}{20C} = \mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{20\angle 15^\circ}{1.49\angle 63^\circ} = \frac{20}{1.49} \angle (15^\circ - 63^\circ) = 13.42 \angle -48^\circ = 8.98 - j9.97 \Omega$$

Equating real and imaginary parts gives  $R = 9 \Omega$  and  $C = \frac{1}{20 \times 9.97} = 5 \text{ mF}$ .

8.

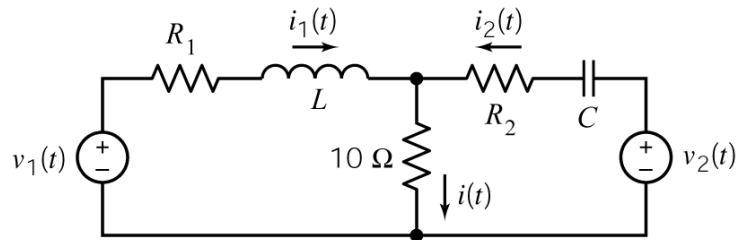

This circuit is at steady state. The voltage source voltages are given by

$$v_1(t) = 12 \cos(2t - 90^\circ) \text{ V} \quad \text{and} \quad v_2(t) = 5 \cos(2t + 90^\circ) \text{ V}$$

The currents are given by


$$i_1(t) = 744 \cos(2t - 118^\circ) \text{ mA}, \quad i_2(t) = 540.5 \cos(2t + 100^\circ) \text{ mA} \quad \text{and} \quad i(t) = A \cos(2t - 164^\circ) \text{ mA}$$

Determine the values of  $A$ ,  $R_1$ ,  $R_2$ ,  $L$  and  $C$ :

$$A = \underline{460} \text{ mA}, \quad R_1 = \underline{10} \Omega, \quad R_2 = \underline{10} \Omega, \quad L = \underline{6} \text{ H} \quad \text{and} \quad C = \underline{50} \text{ mF}.$$

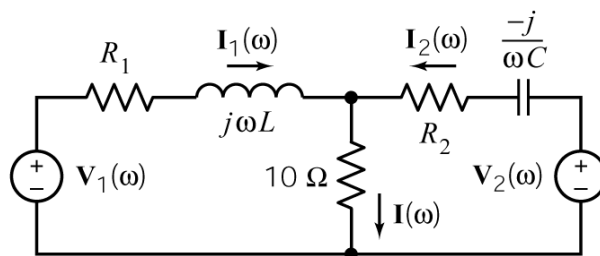**Solution:**


Represent the circuit in the frequency domain using impedances and phasors:



$$\begin{aligned} \mathbf{I} &= \mathbf{I}_1 + \mathbf{I}_2 = 0.744 \angle -118^\circ + 0.5405 \angle 100^\circ = (-0.349 - j0.657) + (-0.094 + j0.532) \\ &= (-0.349 - 0.094) + j(-0.657 + 0.532) \\ &= -0.443 - j0.125 \\ &= 0.460 \angle -164^\circ \end{aligned}$$

$$i(t) = 460 \cos(2t - 164^\circ) \text{ mA}$$

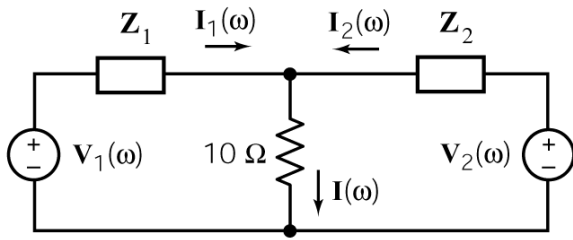Replacing series impedances by equivalent impedances gives



$$\mathbf{Z}_1 = R_1 + j\omega L$$

and

$$\mathbf{Z}_2 = R_2 - j\frac{1}{\omega C}$$

From KVL

$$\begin{aligned} \mathbf{Z}_1 \mathbf{I}_1 + 10\mathbf{I} - \mathbf{V}_1 &= 0 \Rightarrow \mathbf{Z}_1 = \frac{\mathbf{V}_1 - 10\mathbf{I}}{\mathbf{I}_1} = \frac{12\angle -90^\circ - 10(0.460\angle -164^\circ)}{0.744\angle -118^\circ} \\ &= \frac{-j12 - 10(-0.443 - j0.125)}{0.744\angle -118^\circ} \\ &= \frac{4.43 - j10.75}{0.744\angle -118^\circ} = \frac{11.63\angle -67.6^\circ}{0.744\angle -118^\circ} \\ &= 15.63\angle 50.4^\circ \\ &= 10 + j12 \Omega \end{aligned}$$

and

$$\begin{aligned} -\mathbf{Z}_2 \mathbf{I}_2 + \mathbf{V}_2 - 10\mathbf{I} &= 0 \Rightarrow \mathbf{Z}_2 = \frac{\mathbf{V}_2 - 10\mathbf{I}}{\mathbf{I}_2} = \frac{5\angle 90^\circ - 10(0.460\angle -164^\circ)}{0.5405\angle 100^\circ} \\ &= \frac{j5 - 10(-0.443 - j0.125)}{0.5405\angle 100^\circ} \\ &= \frac{4.43 + j6.25}{0.5405\angle 100^\circ} = \frac{7.66\angle 54.7^\circ}{0.5405\angle 100^\circ} \\ &= 14.14\angle -55.3^\circ \\ &= 10 - j10 \Omega \end{aligned}$$

Next

$$10 + j12 = R_1 + j\omega L = R_1 + j2L \Rightarrow R_1 = 10 \Omega \text{ and } L = \frac{12}{2} = 6 \text{ H}$$

and

$$10 - j10 = R_2 - j\frac{1}{\omega C} = R_2 - j\frac{1}{2C} \Rightarrow R_2 = 10 \Omega \text{ and } C = \frac{1}{2(10)} = 0.05 \text{ F}$$

9. The input this circuit is the current

$$i_s(t) = 2 \cos(5t + 15^\circ) \text{ A}.$$


In the frequency domain, this circuit is represented by the node equation

$$\begin{bmatrix} d + j0.5 & -j0.5 \\ -j0.5 & 0.25 + je \end{bmatrix} \begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \end{bmatrix} = \begin{bmatrix} 2\angle 15^\circ \\ 0 \end{bmatrix}$$

where  $\mathbf{V}_a$  and  $\mathbf{V}_b$  are the phasor node voltages and  $d$  and  $e$  are real numbers. Determine the values of  $d$  and  $e$ .

$$d = \underline{\quad 0.125 \quad} \Omega \quad \text{and} \quad e = \underline{\quad -3.5 \quad} \Omega$$

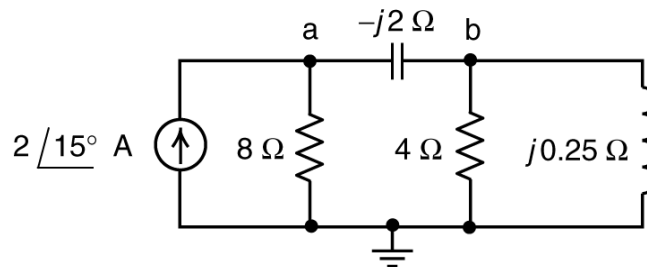**Solution:** Represent the circuit in the frequency domain using impedances and phasors:



Apply KCL at node a to get

$$2\angle 15^\circ = \frac{\mathbf{V}_a}{8} + \frac{\mathbf{V}_a - \mathbf{V}_b}{-j2} = (0.125 + j0.5)\mathbf{V}_a - (j0.5)\mathbf{V}_b$$

Apply KCL at node b to get

$$\begin{aligned} \frac{\mathbf{V}_a - \mathbf{V}_b}{-j2} &= \frac{\mathbf{V}_b}{4} + \frac{\mathbf{V}_b}{j0.25} \Rightarrow j0.5(\mathbf{V}_a - \mathbf{V}_b) = (0.25 - j4)\mathbf{V}_b \\ &\Rightarrow 0 = -j0.5\mathbf{V}_a + (0.25 - j3.5)\mathbf{V}_b \end{aligned}$$

Organize these equations into matrix form to get

$$\begin{bmatrix} 0.125 + j0.5 & -j0.5 \\ -j0.5 & 0.25 - j3.5 \end{bmatrix} \begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \end{bmatrix} = \begin{bmatrix} 2\angle 15^\circ \\ 0 \end{bmatrix}$$

Compare this equation to the given node equation to see that  $d = 0.125 \Omega$  and  $e = -3.5 \Omega$ .