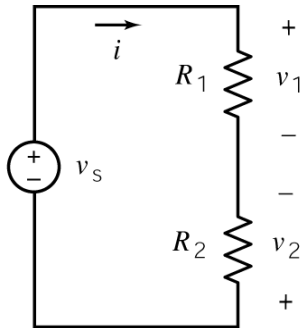


## Reference Directions in Voltage and Current Division




### Voltage Division


Here are two drawings of the same circuit. The bottom circuit is a mirror image of the top circuit.

In both circuits:
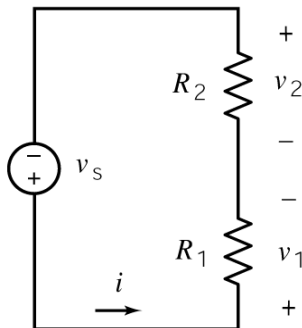
$$i = \frac{v_s}{R_1 + R_2}, \quad v_1 = \left( \frac{R_1}{R_1 + R_2} \right) v_s \quad \text{and} \quad v_2 = - \left( \frac{R_2}{R_1 + R_2} \right) v_s$$



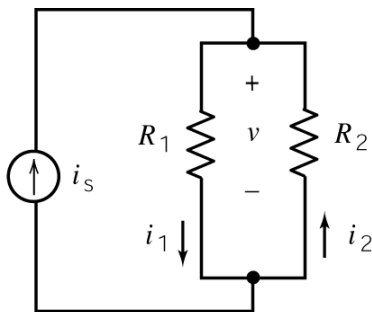There are two possible reference directions for source voltage: + on top or + on bottom. Similarly, there are two possible reference directions for the resistor voltage: + on top or + on bottom. Taken together, there are four possibilities for the source and resistor voltage reference directions. All four are illustrated by these two circuits.




### Current Division

Here are two drawings of the same circuit. The bottom circuit is a mirror image of the top circuit.

In both circuits:

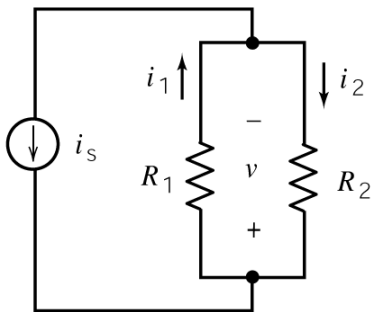
$$v = \left( \frac{R_1 R_2}{R_1 + R_2} \right) i_s, \quad i_1 = \left( \frac{R_2}{R_1 + R_2} \right) i_s \quad \text{and} \quad i_2 = - \left( \frac{R_1}{R_1 + R_2} \right) i_s$$



There are two possible reference directions for the source current: downward or upward. Similarly, there are two possible reference directions for the resistor current: downward or upward. Taken together, there are four possibilities for the source and resistor current reference directions. All four are illustrated by these two circuits.

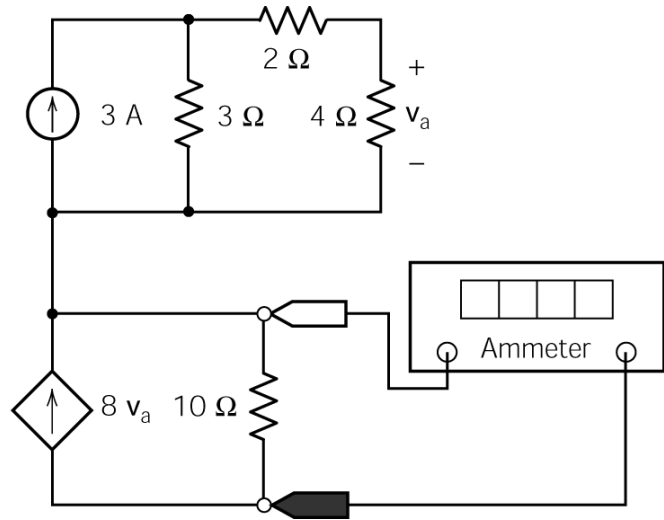
### Problem 4

Determine the value of the current measured by the meter.


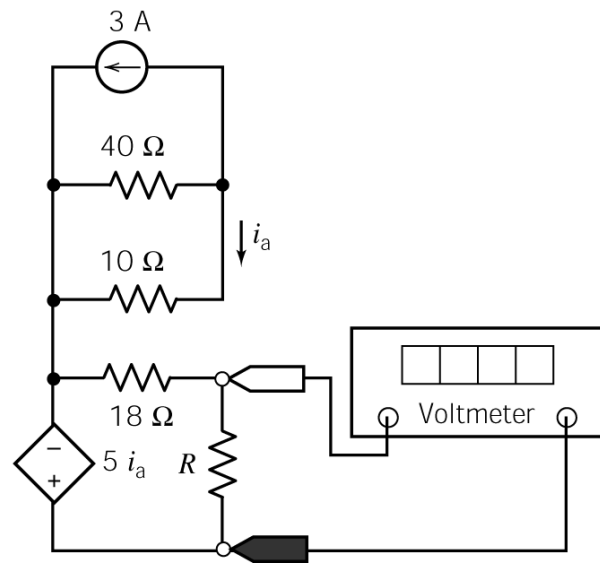
### Problem 5

Determine the value of the resistance  $R$  required to cause the value of the voltage measured by the voltmeter to be 4 V.



### Problem 6

The input to this circuit is the voltage of the independent voltage source,  $v_s$ . The output is the current measured by the meter,  $i_m$ .

(a) Suppose  $v_s = 15$  V. Determine the value of the resistance  $R$  that causes the value of the current measured by the ammeter to be  $i_m = 5$  A.

(b) Suppose  $v_s = 15$  V and  $R = 24$  Ω.

Determine the value of the current measured by the ammeter.

(c) Suppose  $R = 24$  Ω. Determine the value of the input voltage,  $v_s$ , that causes the value of the current measured by the ammeter to be  $i_m = 3$  A.

